

# Lecture #2


# Basic Electronics

# Developer Platform


Android Things 2020

# Signals

Analog

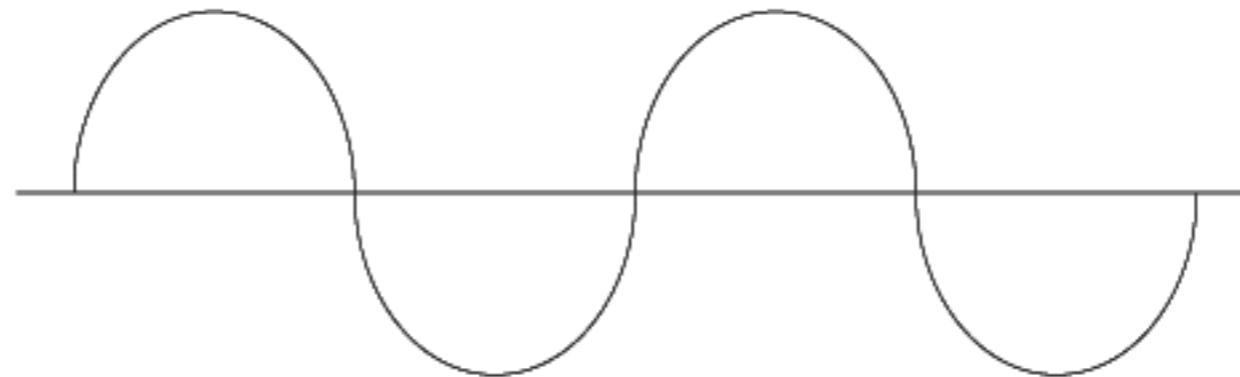

Digital

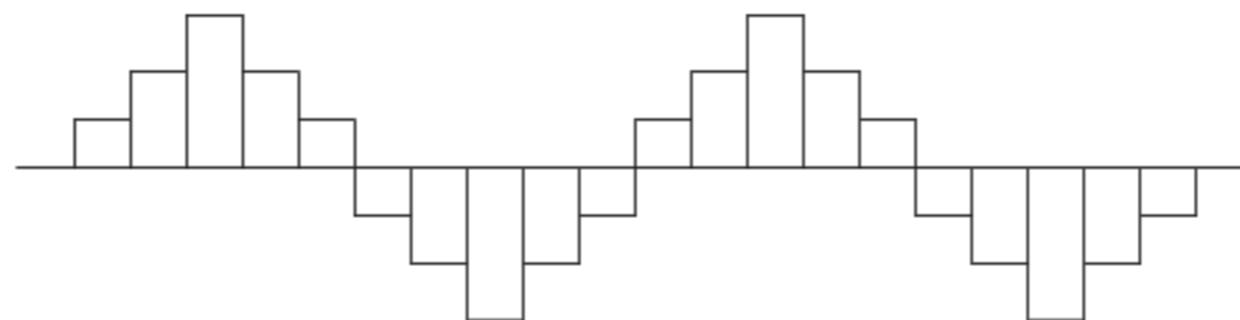

# Analog and Digital

- We can store only digital signal.
  - We will convert everything that is analog to digital.
  - When reading or writing digital signals we need to establish values for:
    - Bits per sample.
    - Sampling rate.


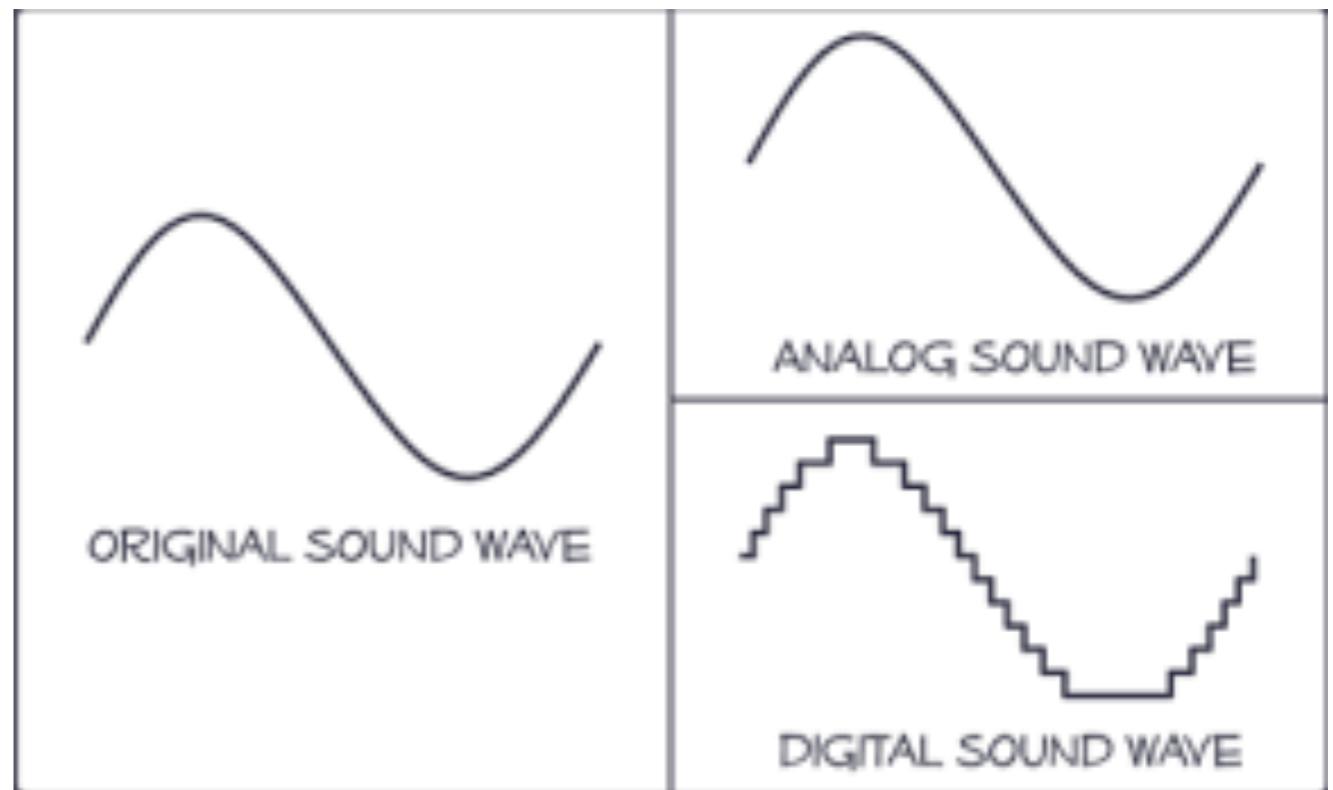



Image source: [www.electronicproducts.com](http://www.electronicproducts.com)
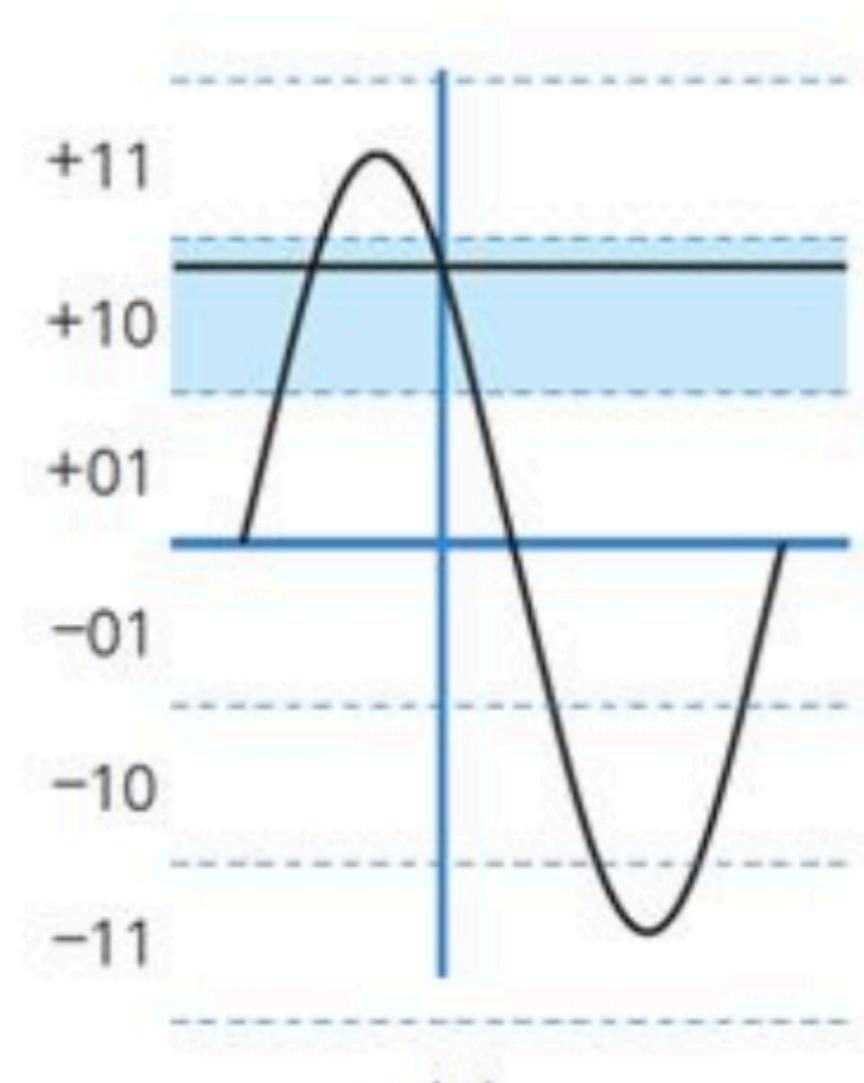
# Bits per sample

- How many bits are used to represent a value.



(a)

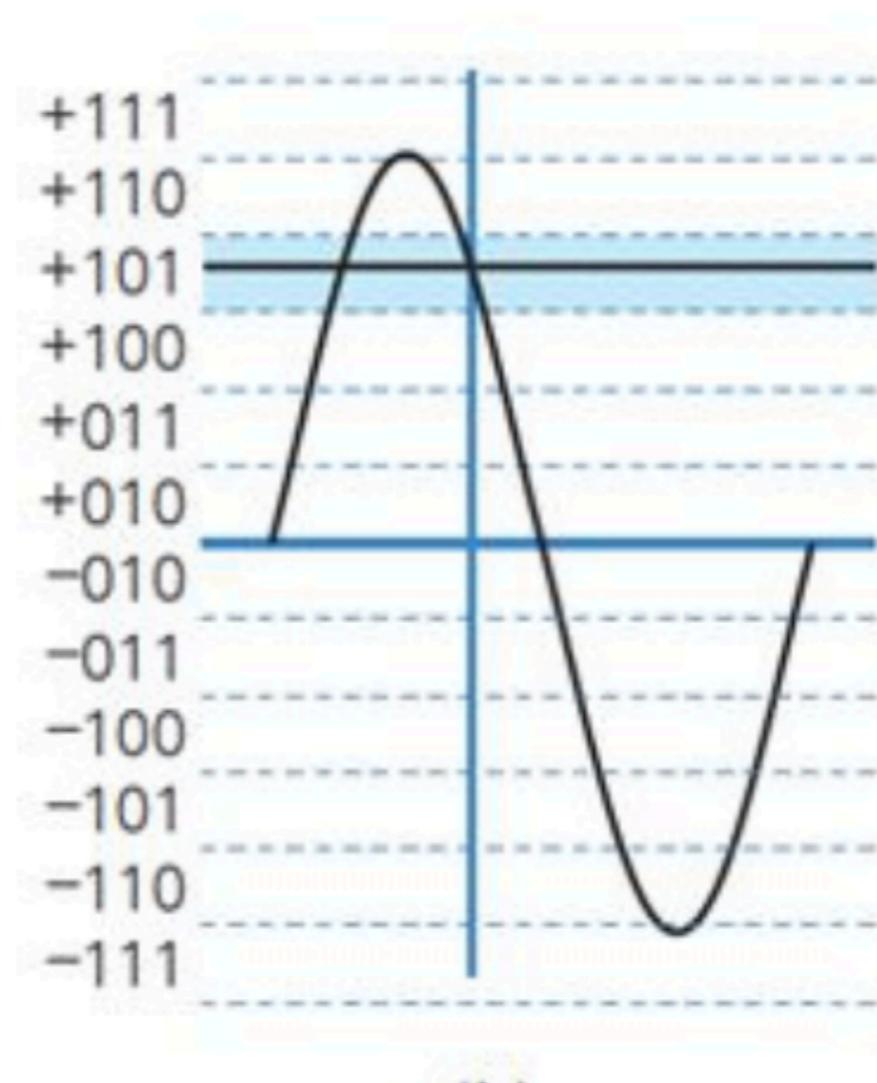

(b)

# Bits per sample


- For **n** bits:
  - Values will range between 0 and  $2^n - 1$ .
  - Eg. for 3 bits we will have:

- 000 - 0
- 001 - 1
- 010 - 2
- 011 - 3
- 100 - 4
- 101 - 5
- 110 - 6
- 111 - 7




Source: etowns

# Bits per sample

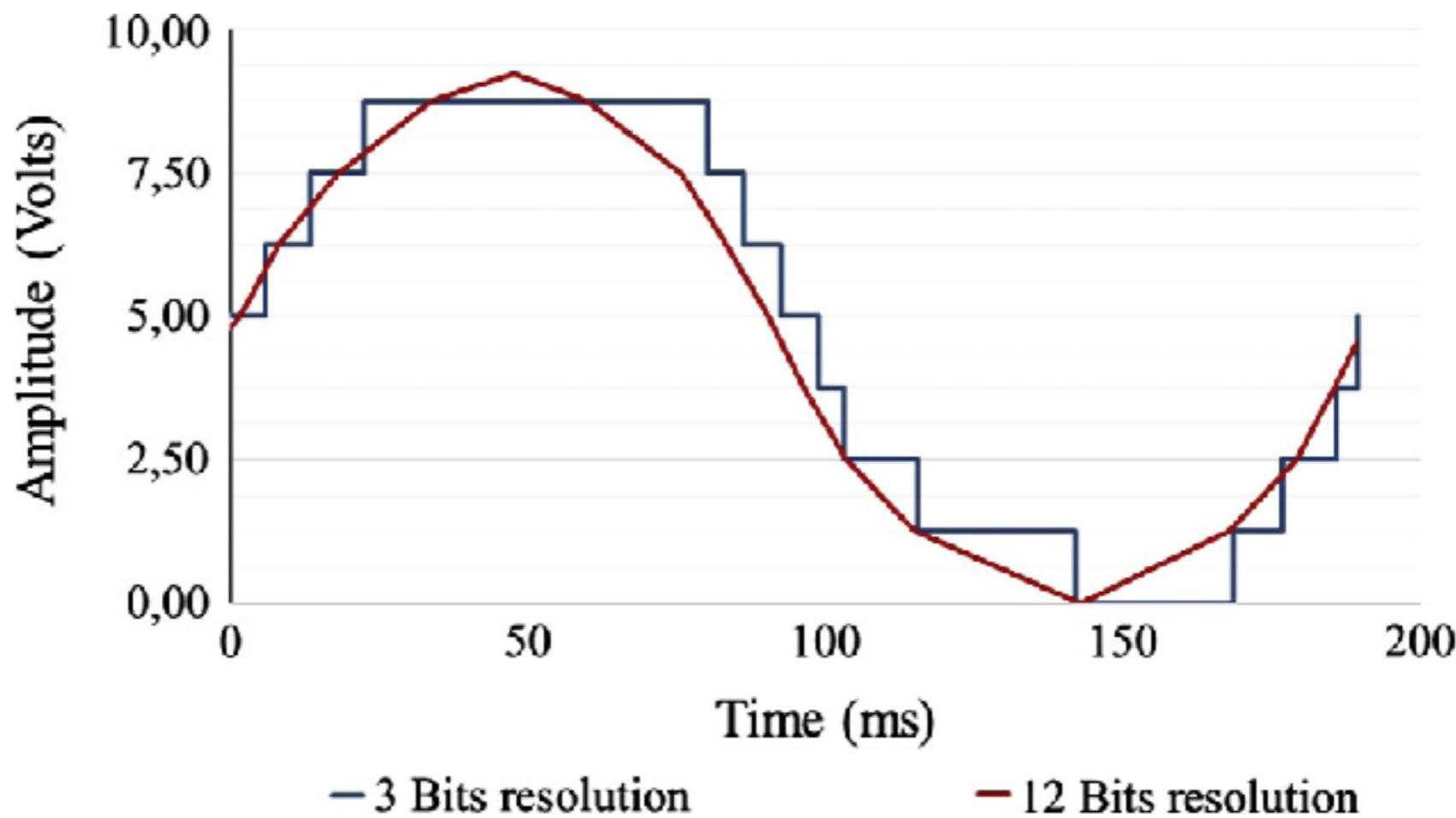


# Sampling


- Make measurements

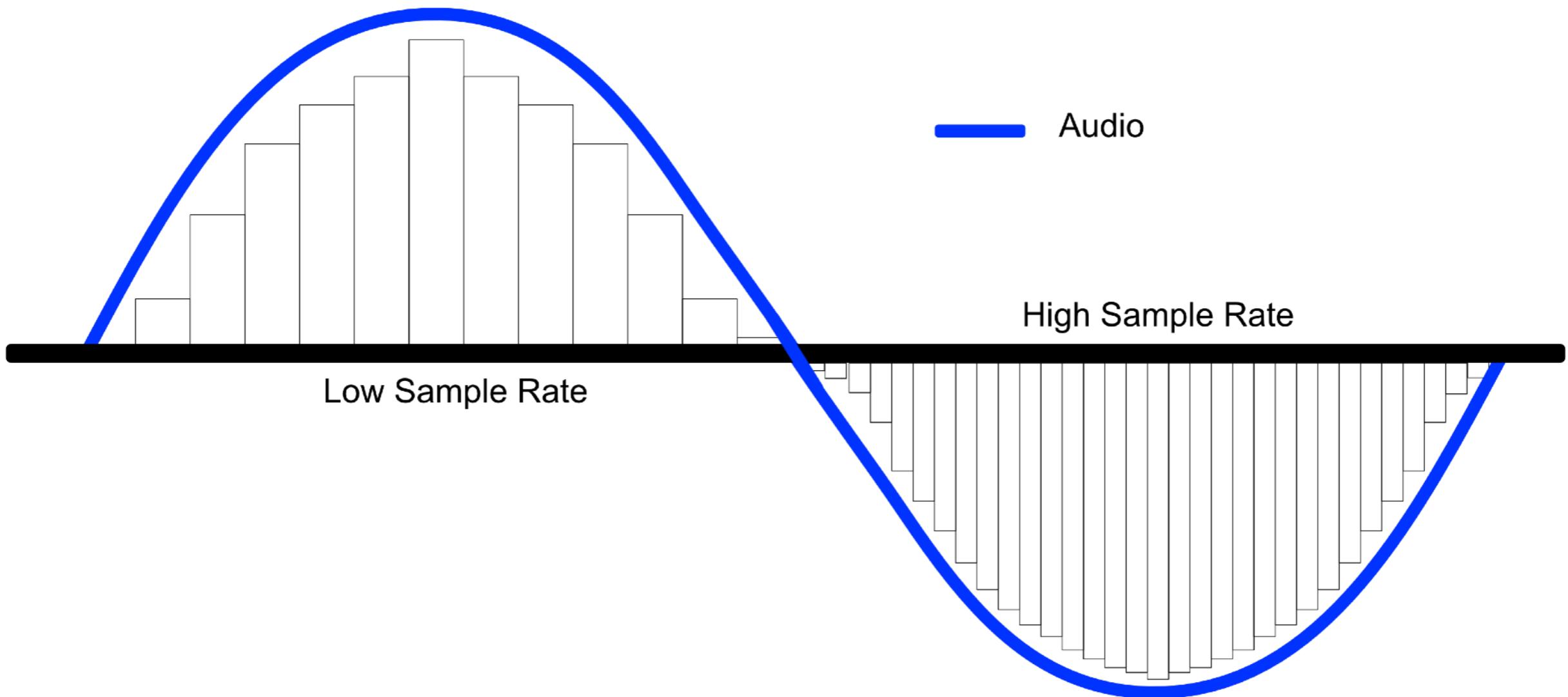

# Sampling

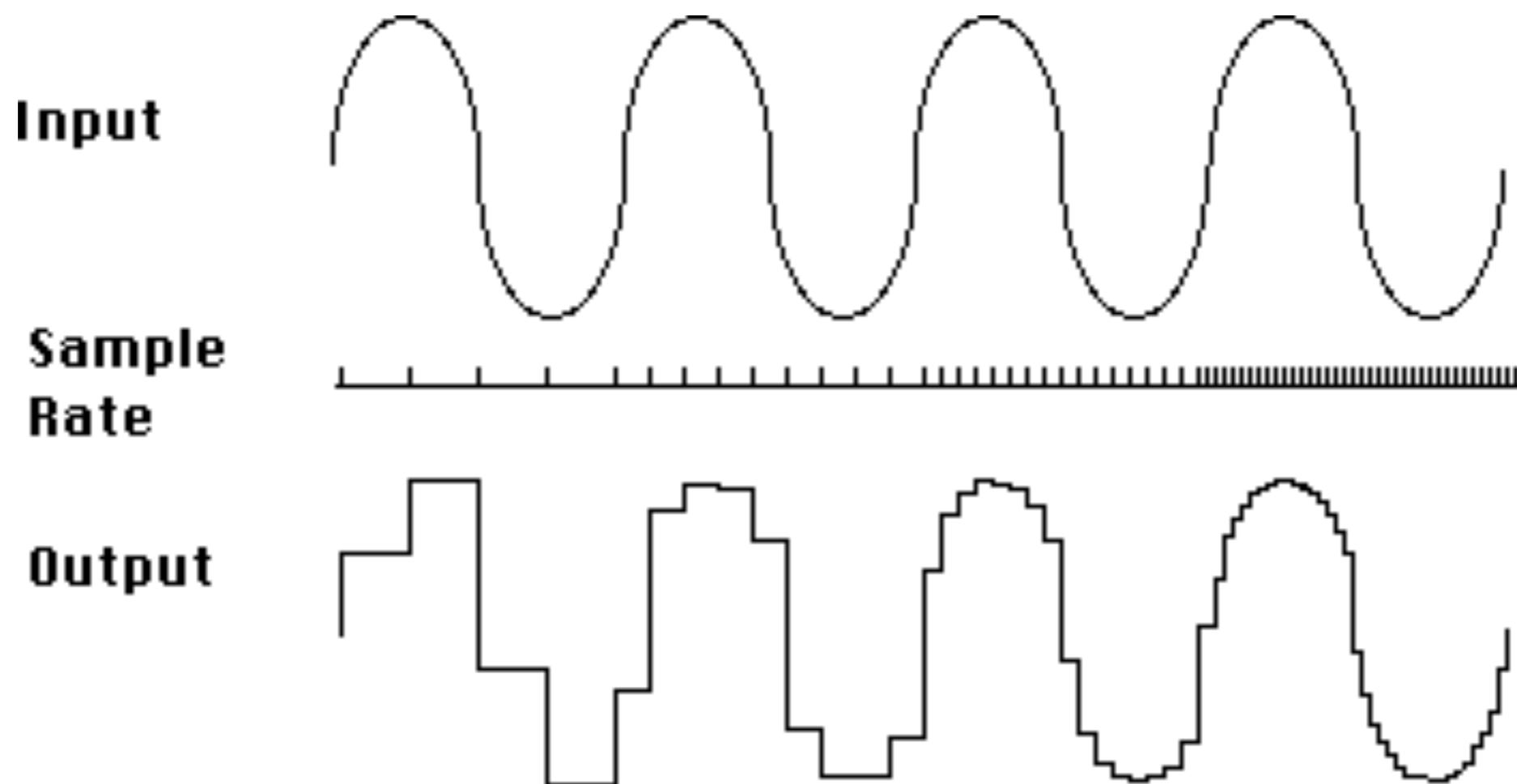

# Sampling

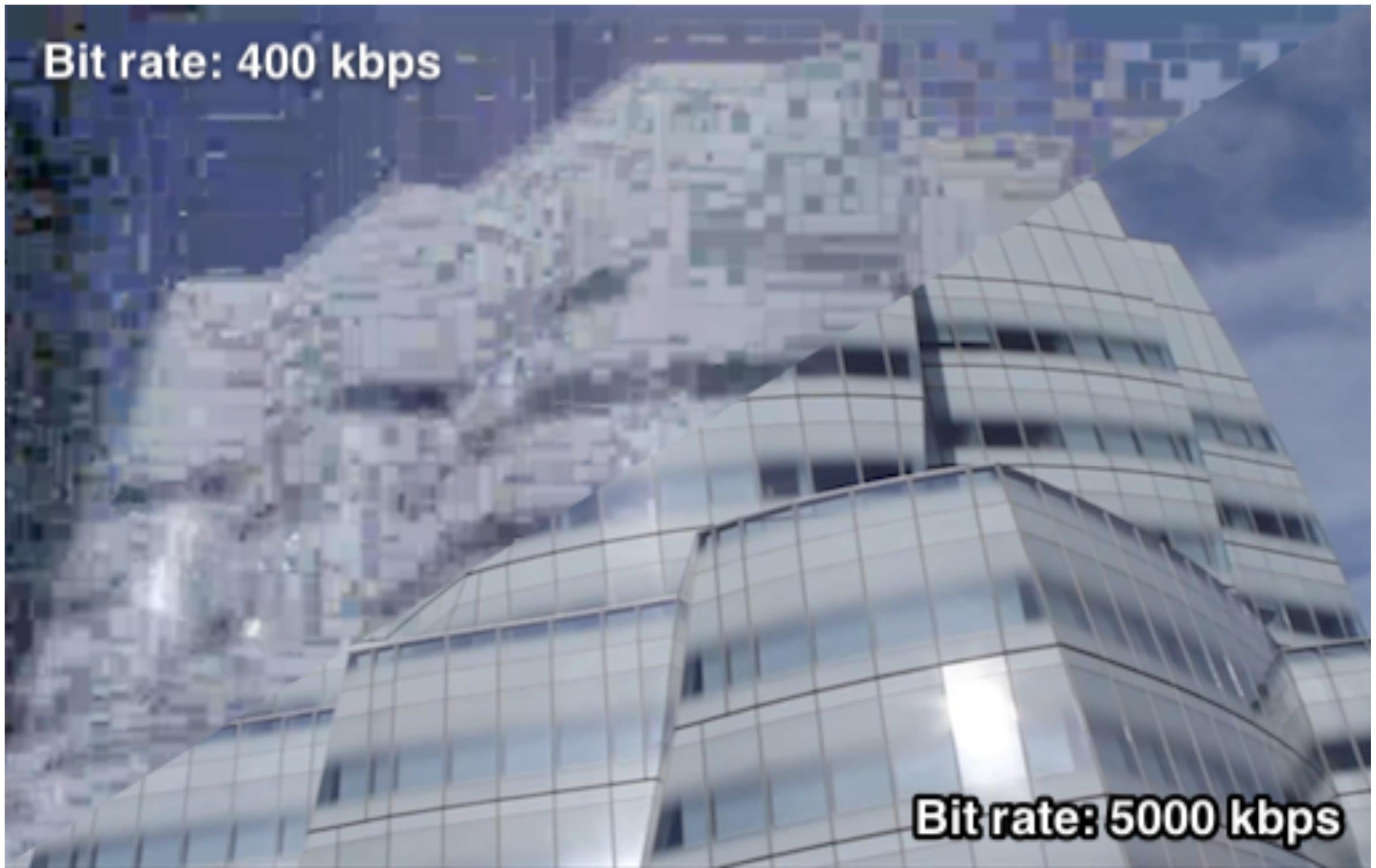

# Frequency

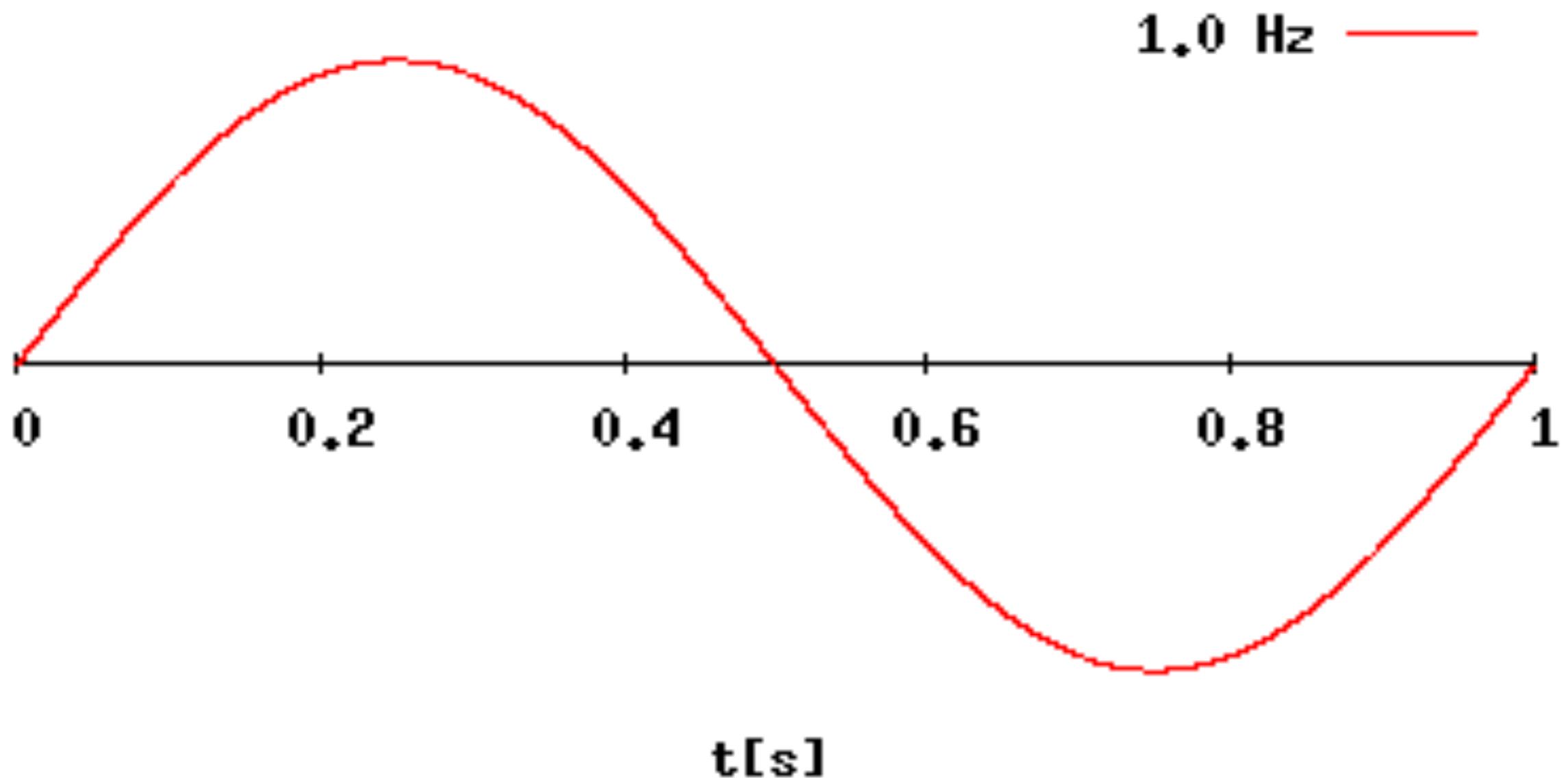


Image source: [https://commons.wikimedia.org/wiki/File:Wave\\_frequency.gif](https://commons.wikimedia.org/wiki/File:Wave_frequency.gif)

# Frequency


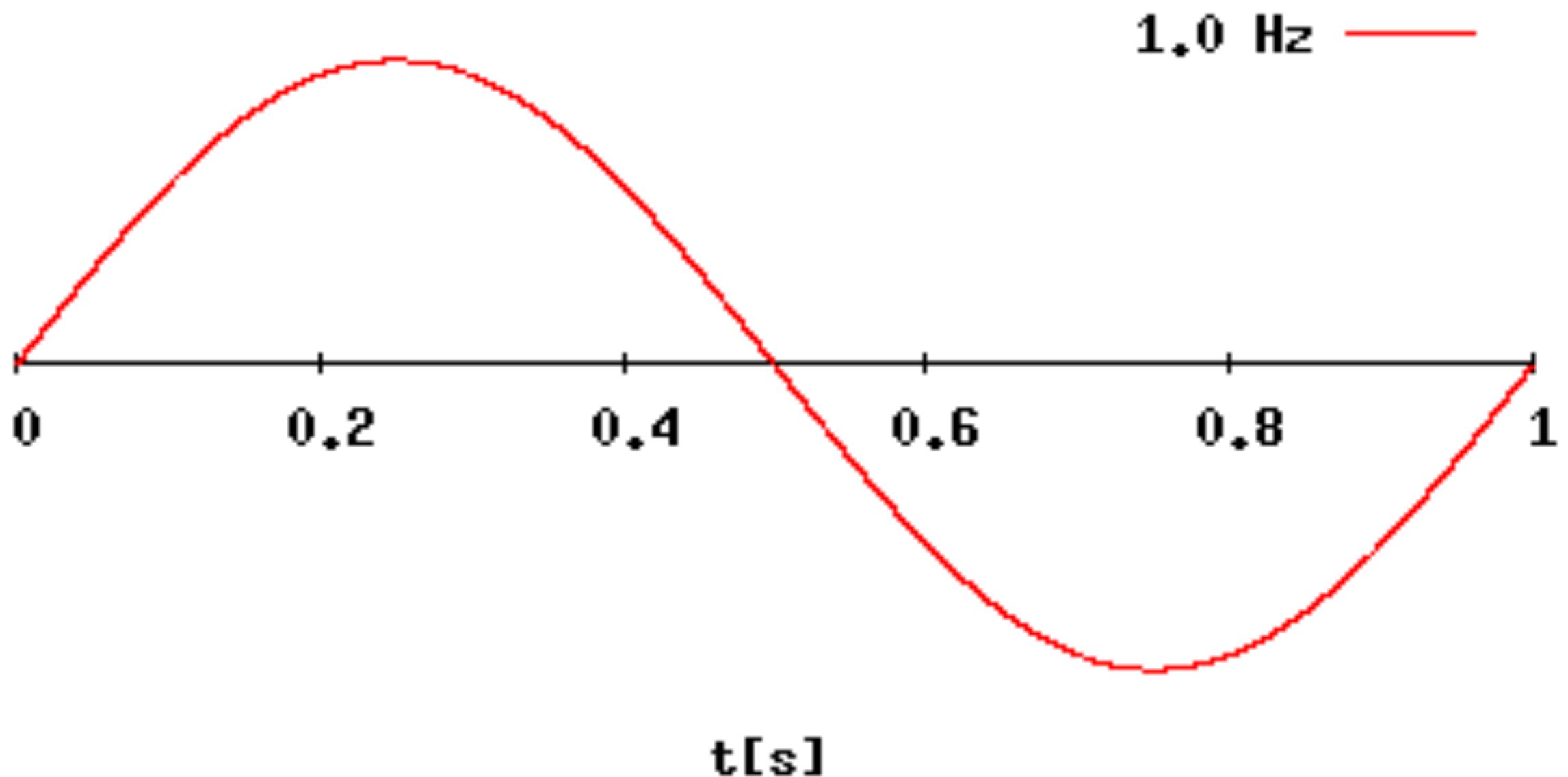


Image source: [https://commons.wikimedia.org/wiki/File:Wave\\_frequency.gif](https://commons.wikimedia.org/wiki/File:Wave_frequency.gif)

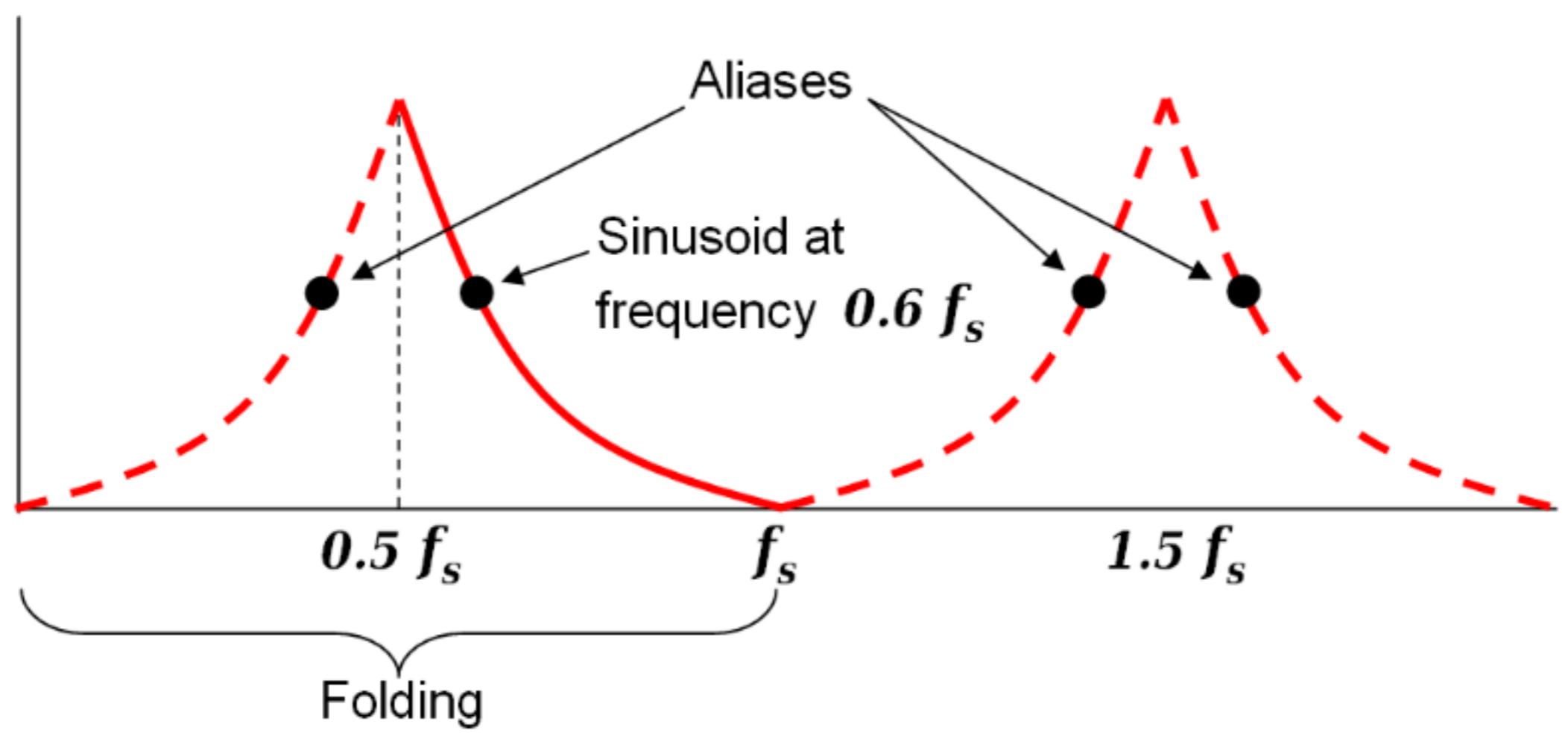
# Sampling Rate

- Nyquist Theorem: Sampling rate  $\geq 2 \times \text{max frequency}$



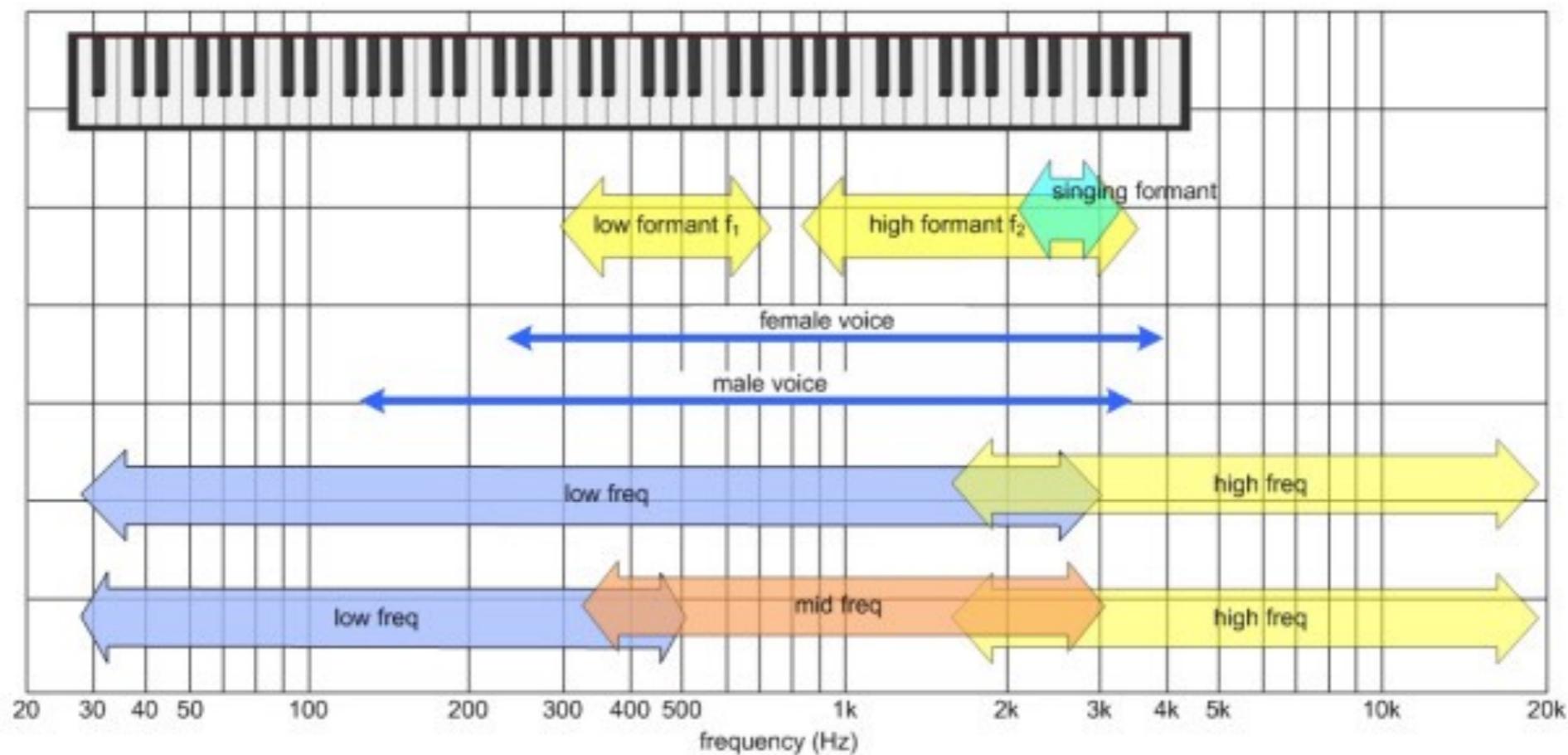
# Voice Frequency

- Human audible range:
  - 20 Hz to 20KHz.





# Voice Frequency

- Human audible range:
- 20 Hz to 20KHz.

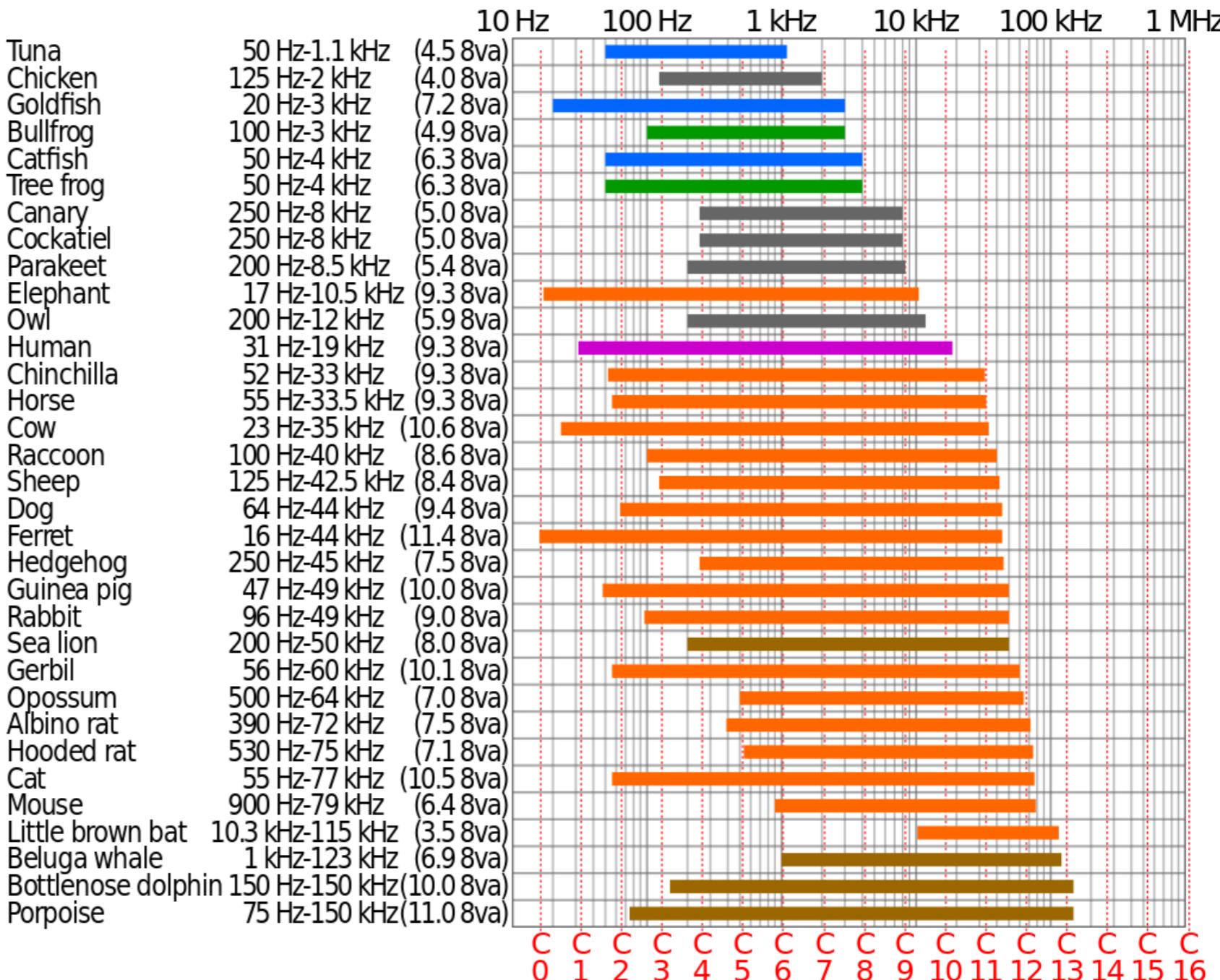

# Voice Frequency

- Human audible range:
- 20 Hz to 20KHz.

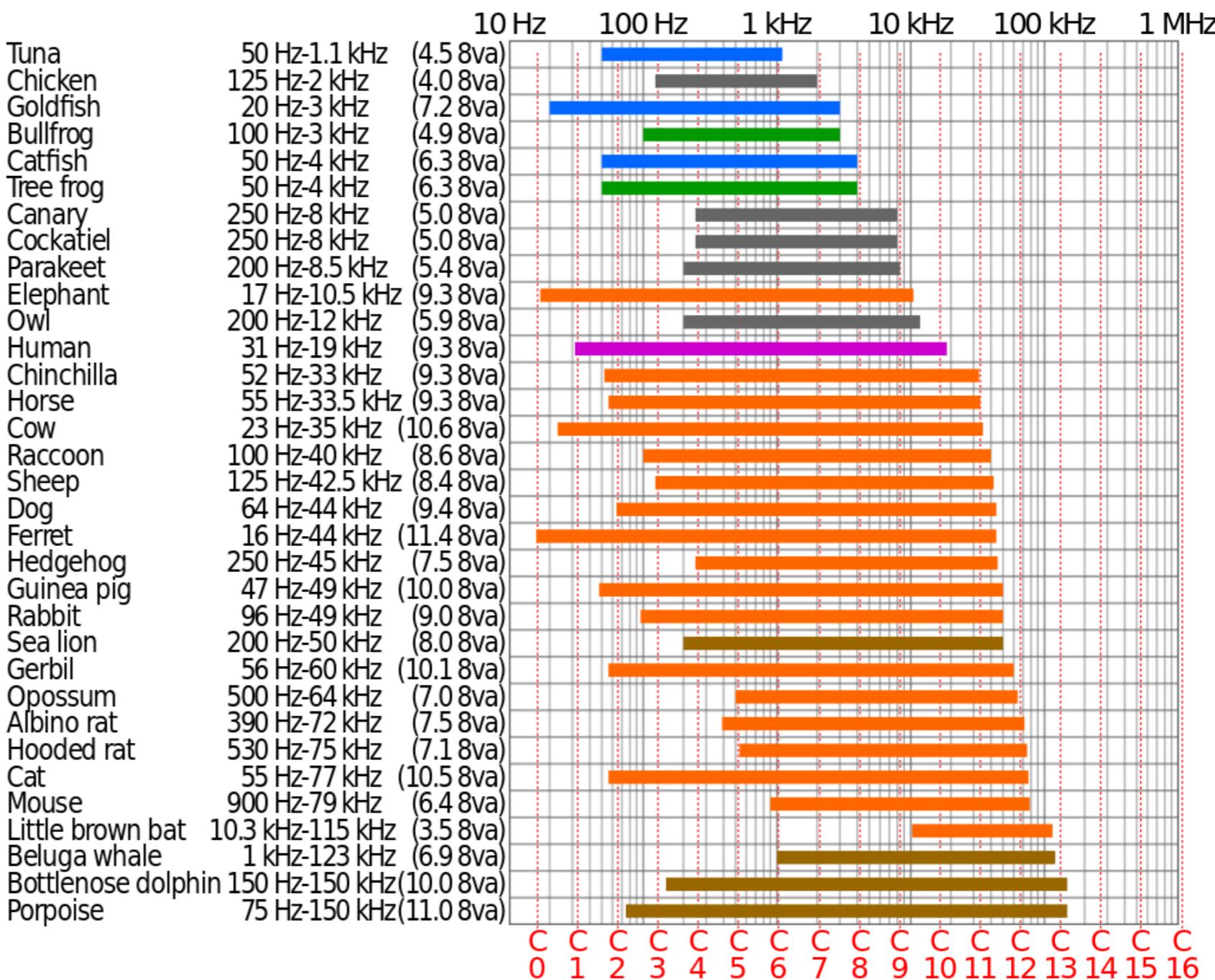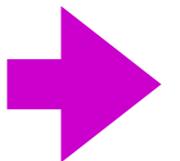

# Voice Frequency

Image source: [www.proav.de/audio/speech-level.html](http://www.proav.de/audio/speech-level.html)

# Voice Frequency

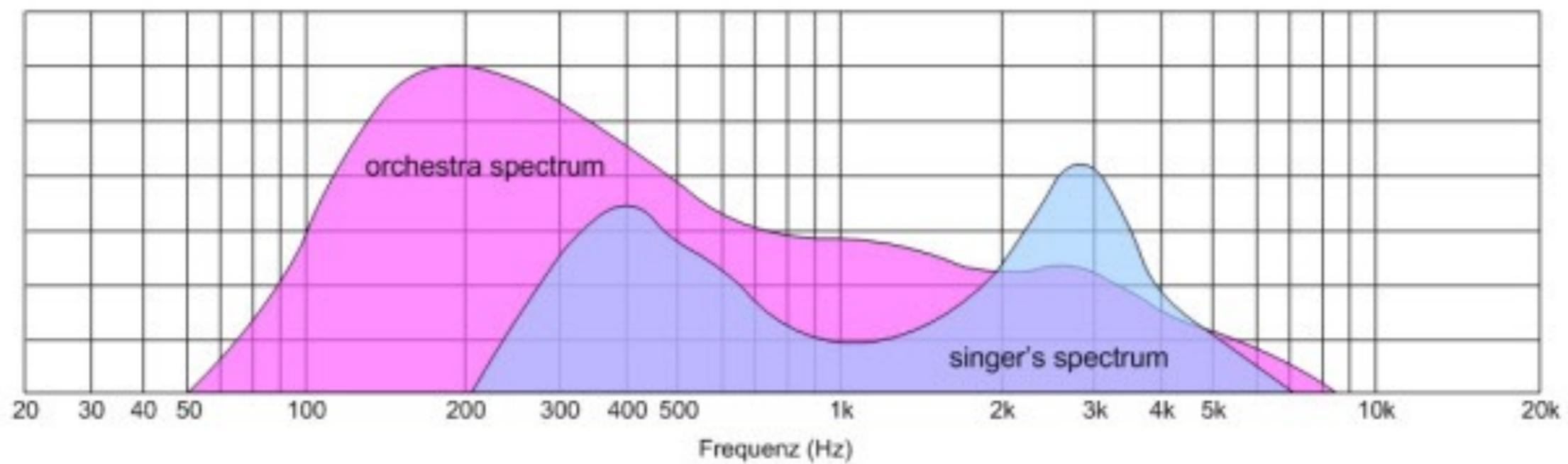


Image source: [www.proav.de/audio/speech-level.html](http://www.proav.de/audio/speech-level.html)



**This record has been made**



**This record has been made**

# Voice Frequency

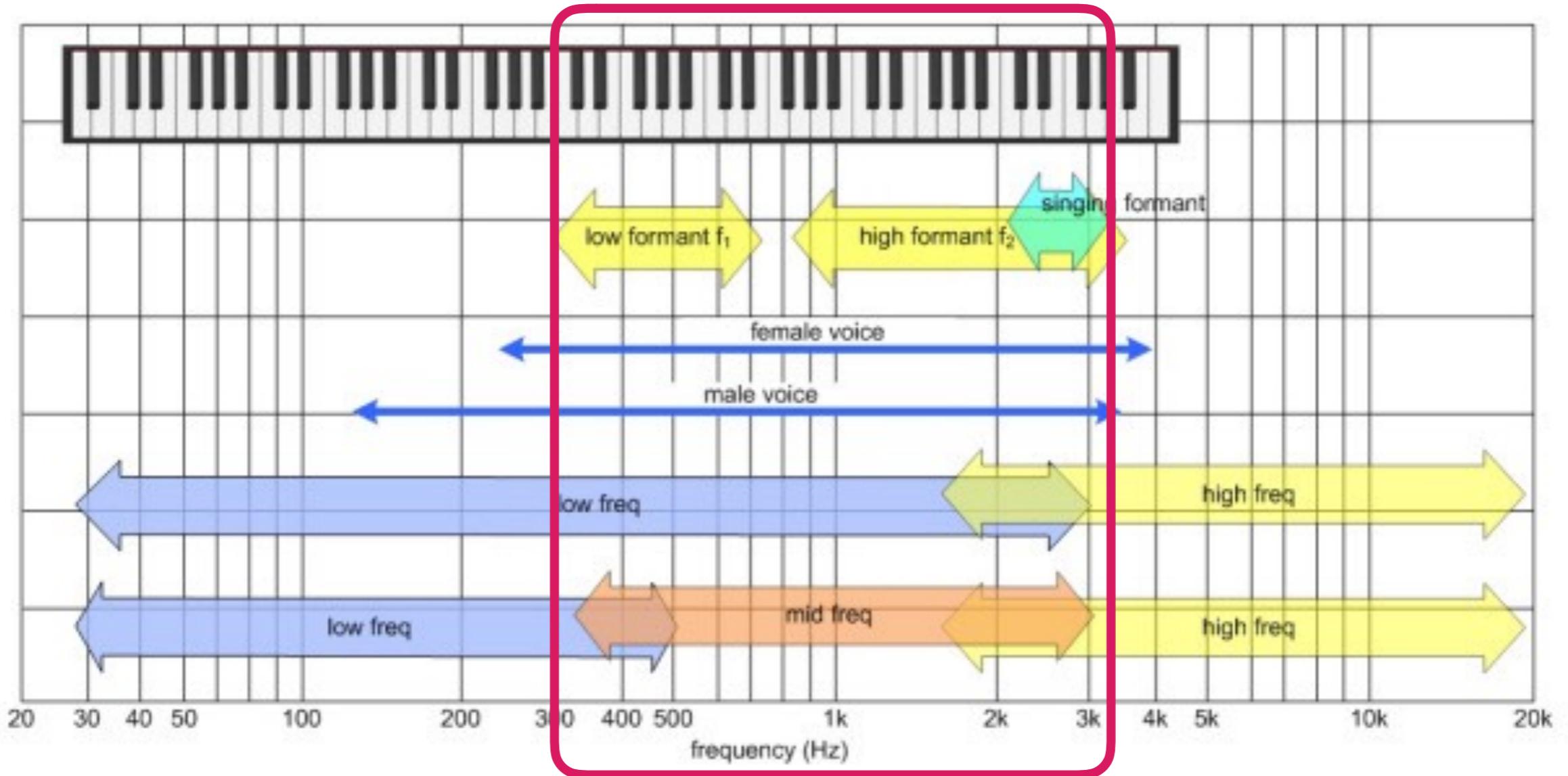


Image source: [www.proav.de/audio/speech-level.html](http://www.proav.de/audio/speech-level.html)

**Telephony, voice frequency range: 300Hz to 3400Hz.**

# Ohm Law

$$I = \frac{V}{R}$$



Image source: <http://stat.case.edu/~pillar/genealogy/ohm.gif>

# Ohm Law

## Ohm's Law Calculator

Voltage (V) = Current (I) \* Resistance (R)

Power (P) = Voltage (V) \* Current (I)

Enter any two known values and press "Calculate" to solve for the others.

Voltage (V)

3.3

Volts (V)

Current (I)

16.5

millamps (mA)

Resistance (R)

200

ohms ( $\Omega$ )

Power (P)

0.05445

Watts (W)

Calculate

Click "Calculate" to update the fields with orange borders.

<http://www.ohmslawcalculator.com/ohms-law-calculator>

# Ohm Law

## Ohm's Law Calculator

Voltage (V) = Current (I) \* Resistance (R)

Power (P) = Voltage (V) \* Current (I)

Enter any two known values and press "Calculate" to solve for the others.

Voltage (V)

3.3

Volts (V)

Current (I)

16.5

millamps (mA)

Resistance (R)

200

ohms ( $\Omega$ )

Power (P)


0.05445

Watts (W)


Calculate

Click "Calculate" to update the fields with orange borders.

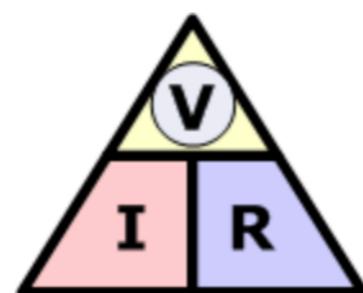
<http://www.ohmslawcalculator.com/ohms-law-calculator>



$$\textcircled{V} = I \times R$$

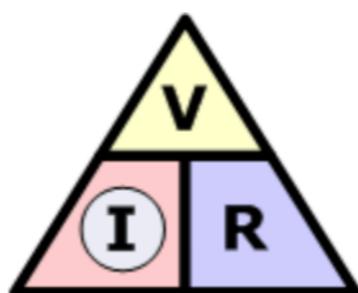

$$\textcircled{I} = \frac{V}{R}$$

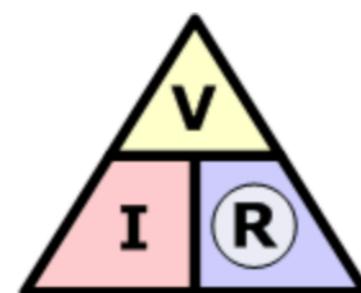


$$\textcircled{R} = \frac{V}{I}$$

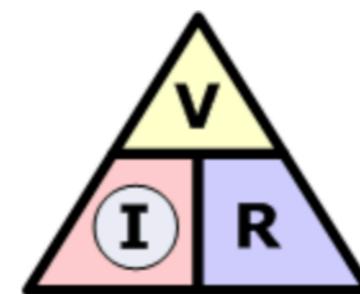
# Ohm Law




$$\textcircled{\textbf{V}} = I \times R$$



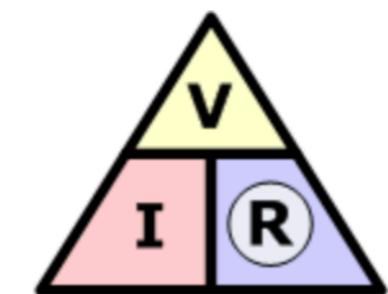
$$\textcircled{\textbf{I}} = \frac{V}{R}$$



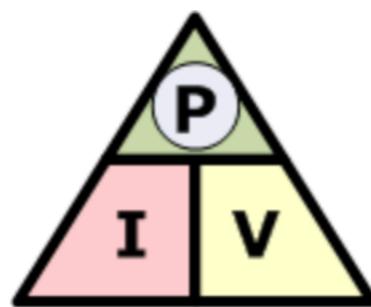
$$\textcircled{\textbf{R}} = \frac{V}{I}$$


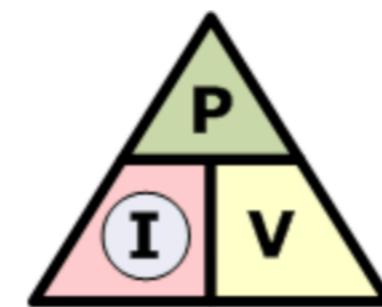
$$\textcircled{\textbf{P}} = I \times V$$



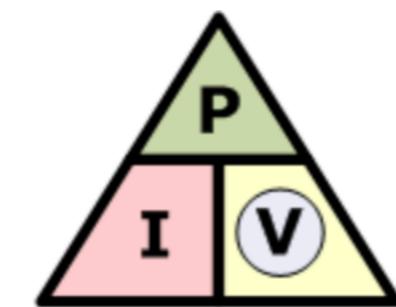
$$\textcircled{\textbf{I}} = \frac{P}{V}$$



$$\textcircled{\textbf{V}} = \frac{P}{I}$$


# Resistors in Series

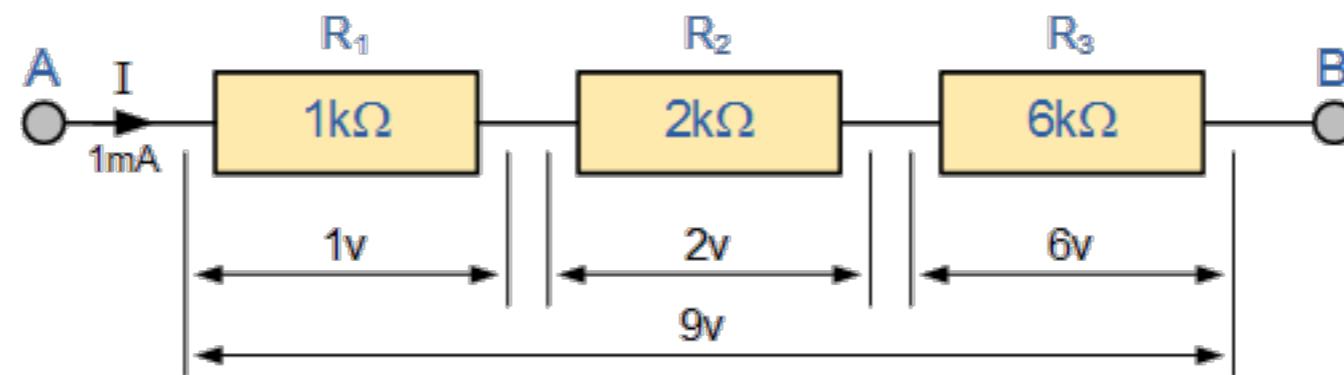

$$R_T = R_1 + R_2 + R_3$$

$$R_{EQ} = R_1 + R_2 + R_3 = 1\text{k}\Omega + 2\text{k}\Omega + 6\text{k}\Omega = 9\text{k}\Omega$$

# Resistors in Parallel

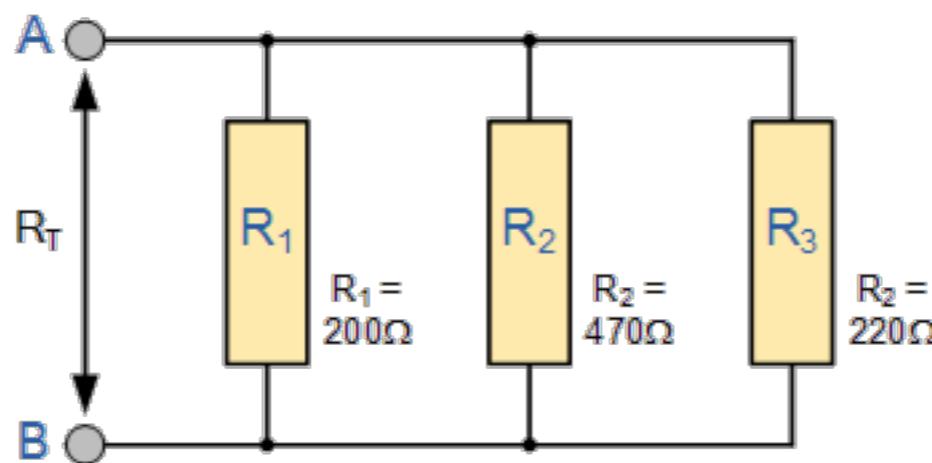

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots + \frac{1}{R_n} \text{ etc}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$= \frac{1}{200} + \frac{1}{470} + \frac{1}{220} = 0.0117$$

$$\text{therefore: } R_T = \frac{1}{0.0117} = 85.67\Omega$$

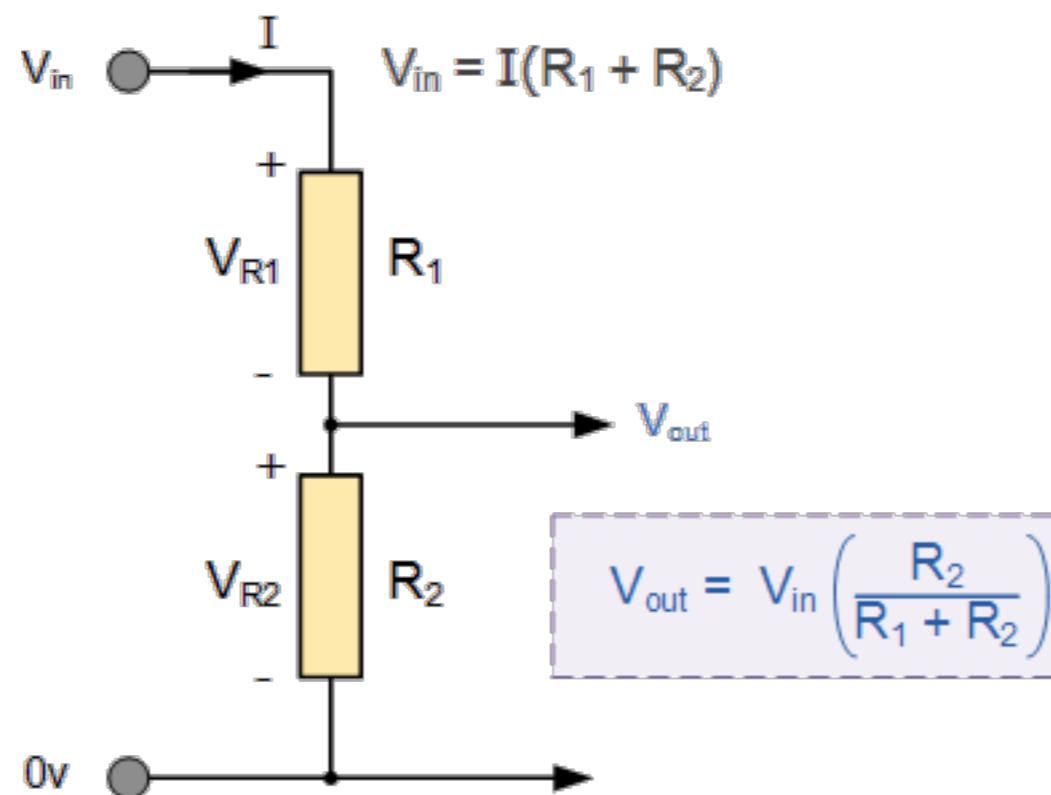
# Voltage Divider Network

Kirchhoff's Voltage Law:

“the supply voltage in a closed circuit is equal to the sum of all the voltage drops ( $I \cdot R$ ) around the circuit”




# Voltage Divider Network

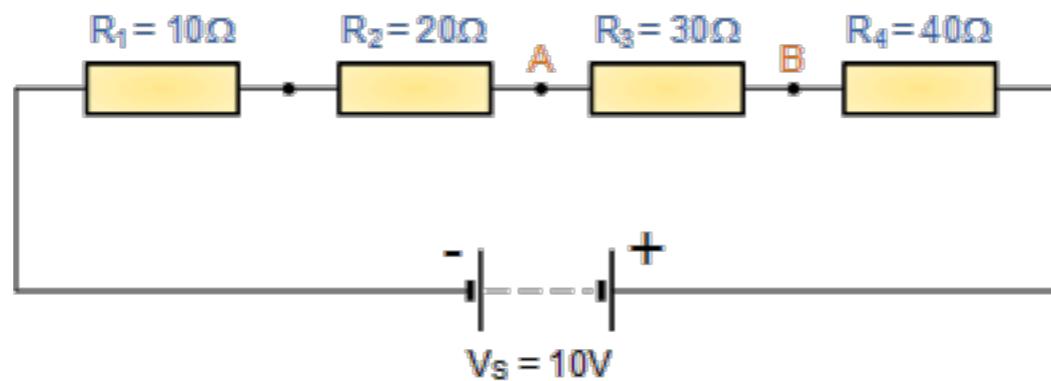


$$V_{AB} = V_{R3} = V_s \times \frac{R3}{R1+R2+R3+R4}$$

$$V_{AB} = 10 \times \frac{30}{10+20+30+40} = 10 \times 0.3 = 3V$$

# Voltage Divider Network

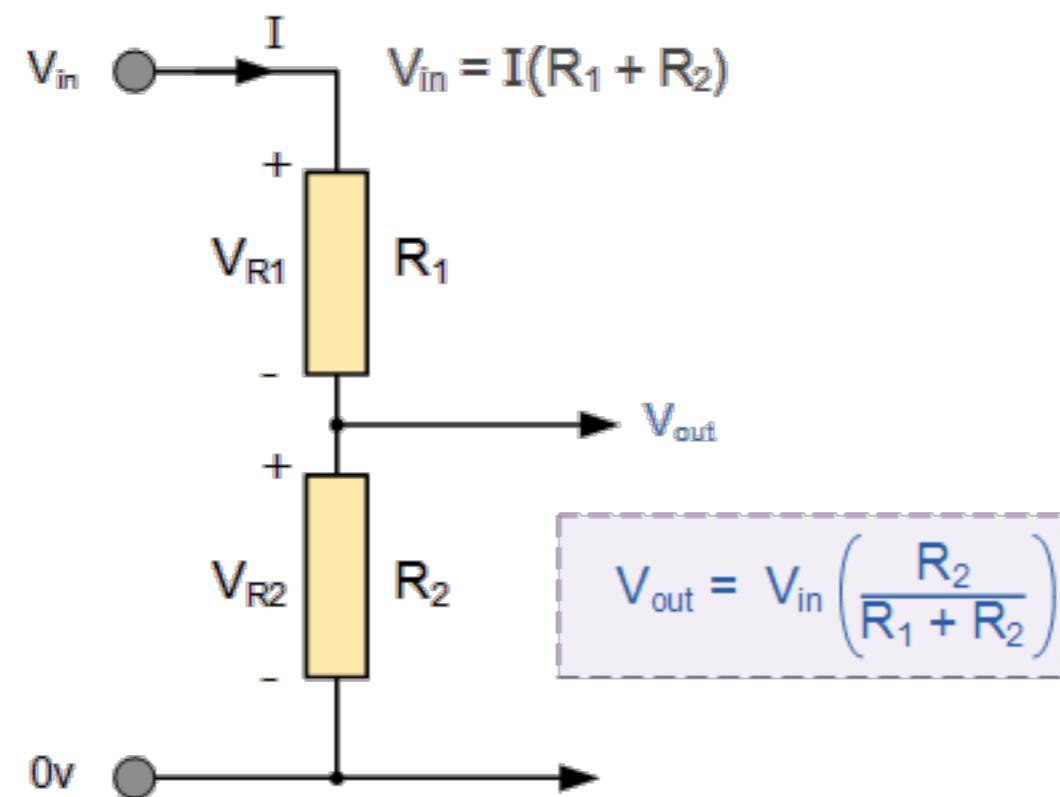


# Voltage Divider Network

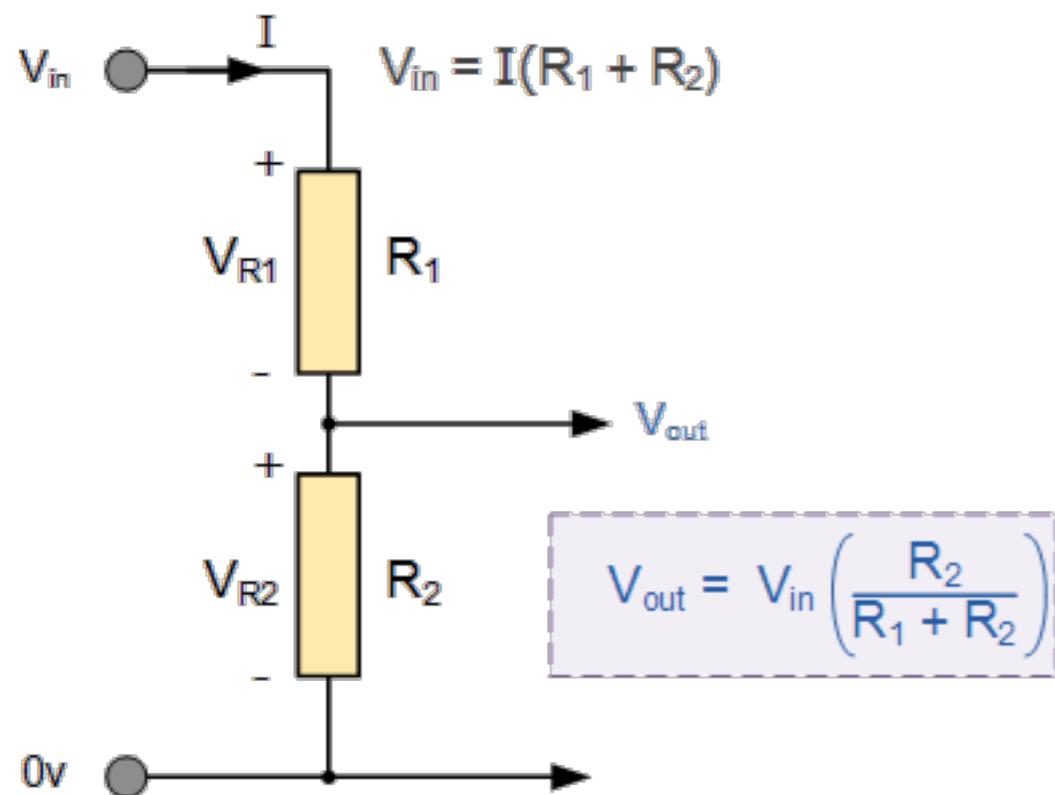

$$R_1 = 0$$
$$V_{out} = ?$$

# Voltage Divider Network

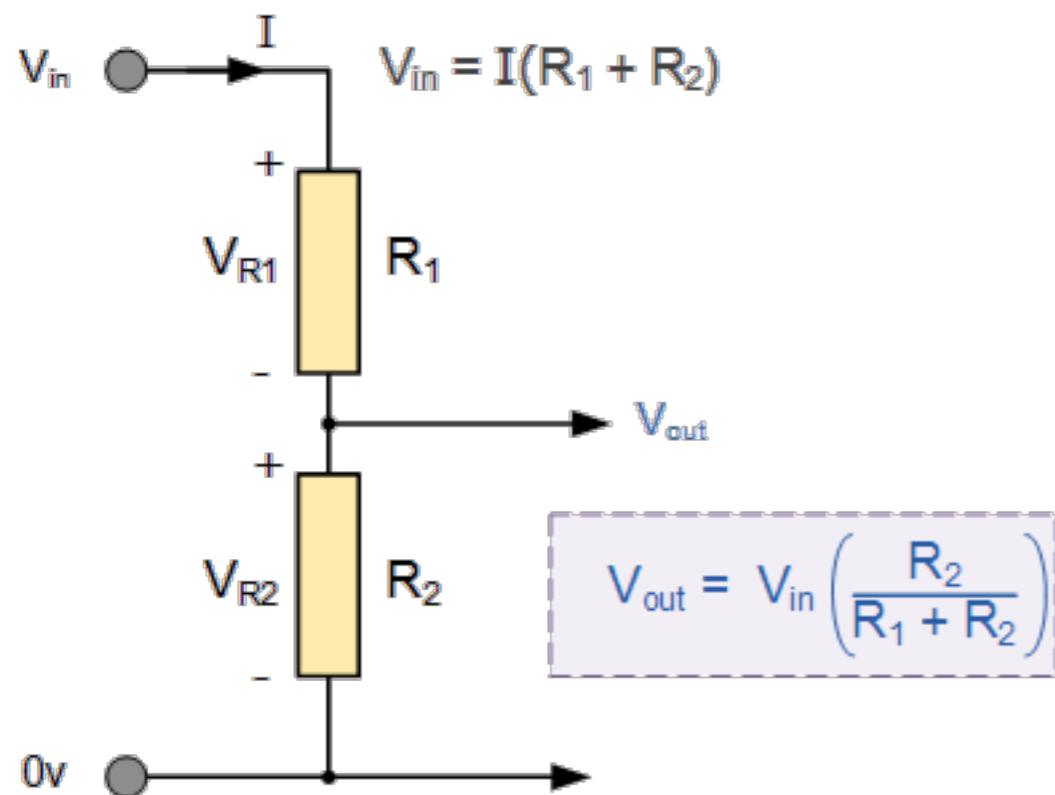


$$V_{in} = I(R_1 + R_2)$$

**$R_1 = 0$**   
 **$V_{out} = V_{in}$**

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

# Voltage Divider Network

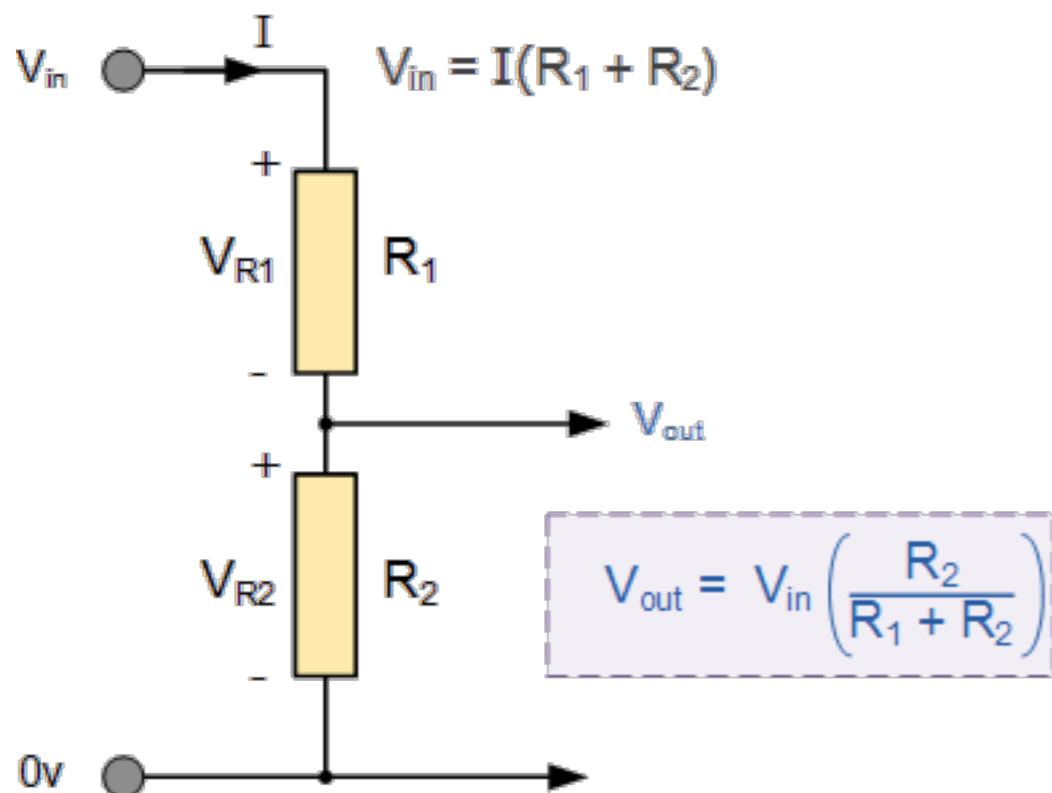

$$V_{in} = I(R_1 + R_2)$$

$R_1$


$R_2$

$$\begin{aligned} R_1 &= 0 \\ V_{out} &= V_{in} \end{aligned}$$

$$\begin{aligned} R_2 &= 0 \\ V_{out} &= ? \end{aligned}$$

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

# Voltage Divider Network

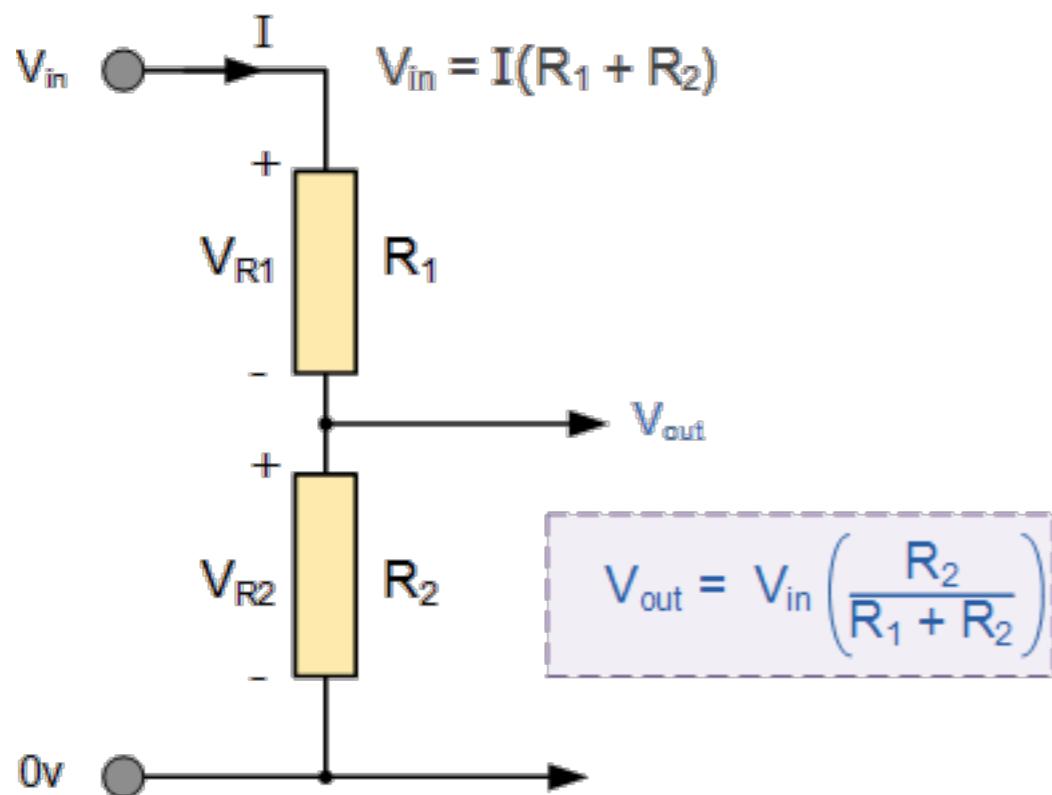

$$R_1 = 0$$


**V<sub>out</sub> = V<sub>in</sub>**

$$R_2 = 0$$

**V<sub>out</sub> = 0**

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

# Voltage Divider Network

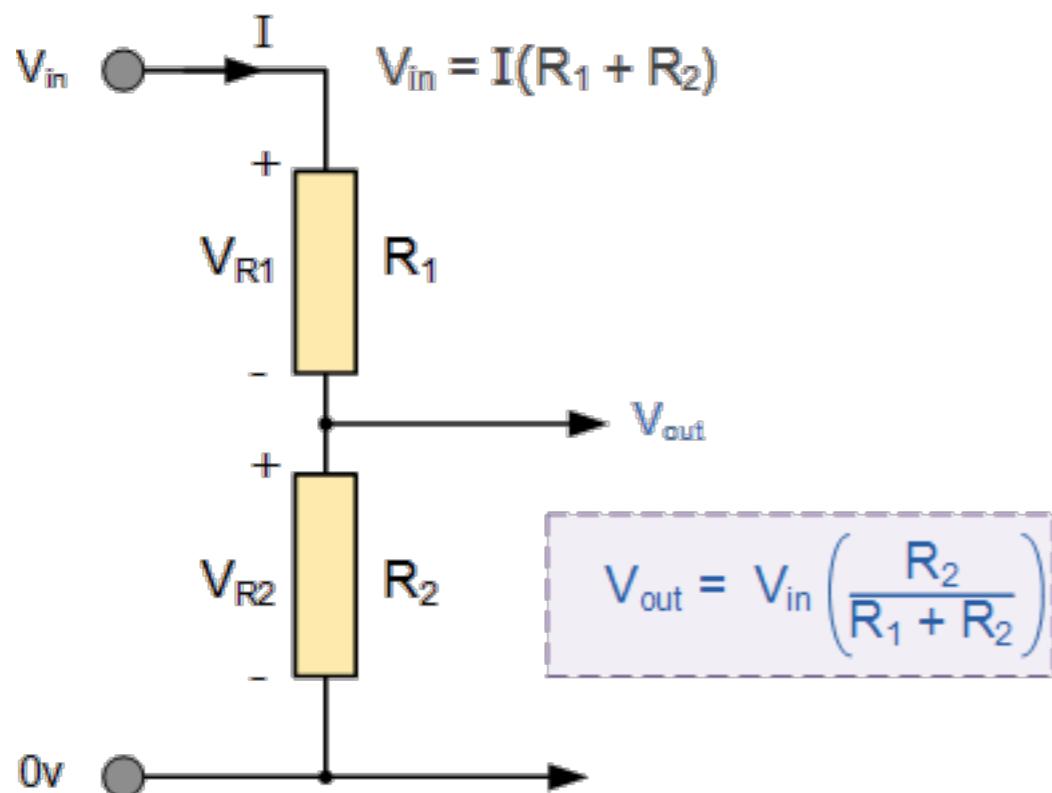


**R1 = 0**  
**Vout = Vin**

**R2 = 0**  
**Vout = 0**

**R2 = infinit**  
**Vout = ?**

# Voltage Divider Network

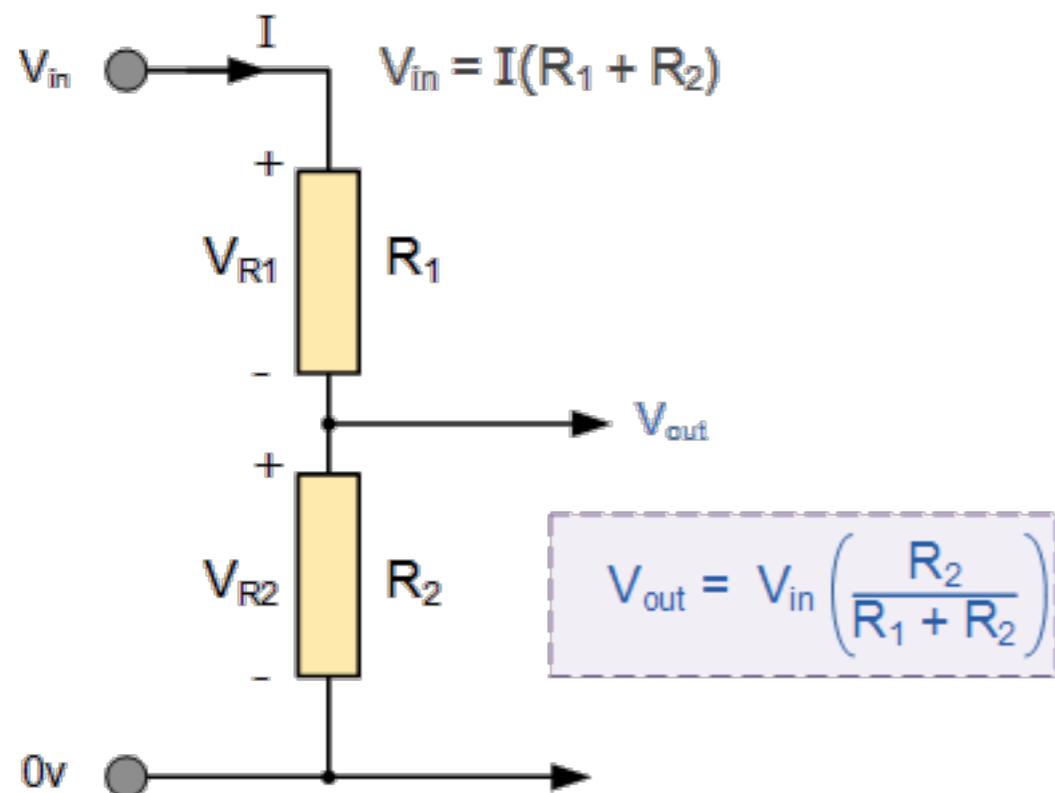

$$V_{in} = I(R_1 + R_2)$$

$$R_1 = 0$$

$$V_{out} = V_{in}$$

$$R_2 = 0$$

$$V_{out} = 0$$

$$R_1 = 0$$


$$R_2 = \infty$$

$$V_{out} = ?$$

$$R_2 = \infty$$

$$V_{out} = V_{in}$$

# Voltage Divider Network

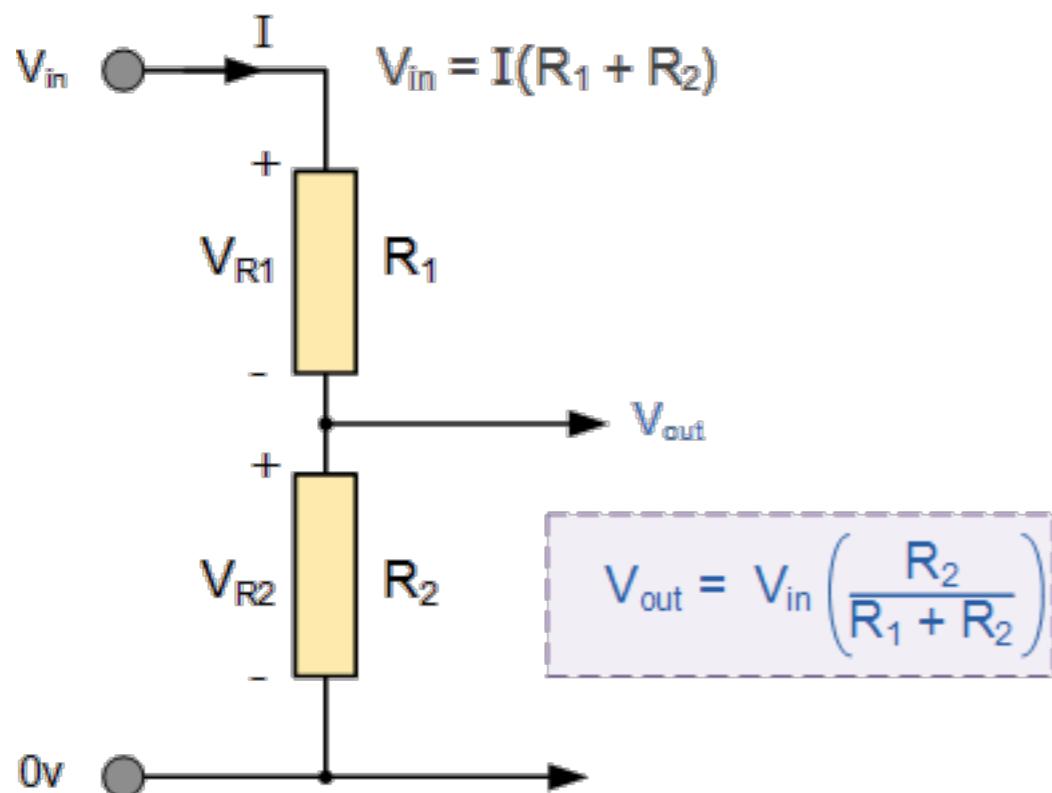

$$V_{in} = I(R_1 + R_2)$$

$$R_1 = 0$$

$$V_{out} = V_{in}$$

$$R_2 = 0$$

$$V_{out} = 0$$

$$R_1 = 0$$

$$R_2 > 0$$

$$V_{out} = ?$$

*Short circuit*


$$R_2 = \text{infinity}$$

$$V_{out} = V_{in}$$

# Peripheral I/O


- General Purpose Input/Output (GPIO)
- Pulse Width Modulation (PWM)
- Serial Communication

# Raspberry Pi 3 Model B

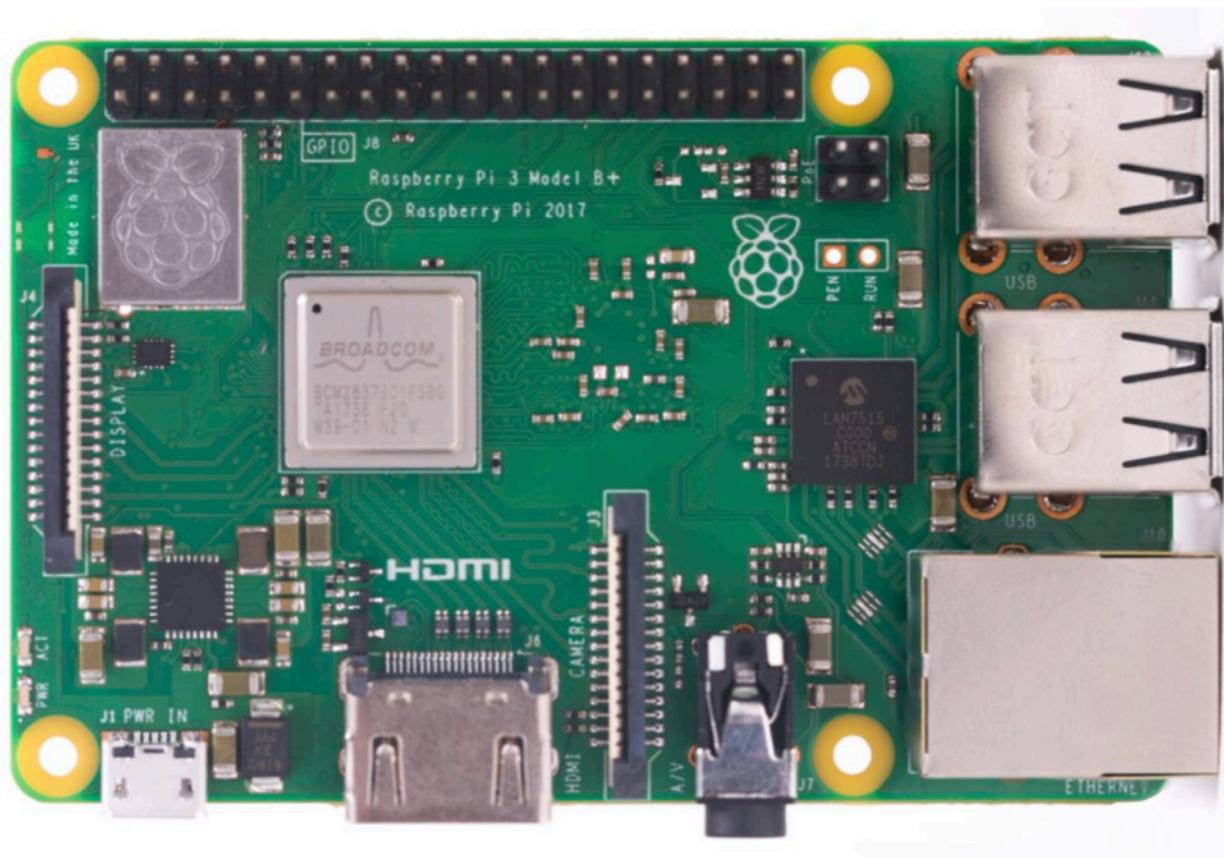

<https://developer.android.com/things/hardware/raspberrypi.html>


# Raspberry Pi 3 Model B

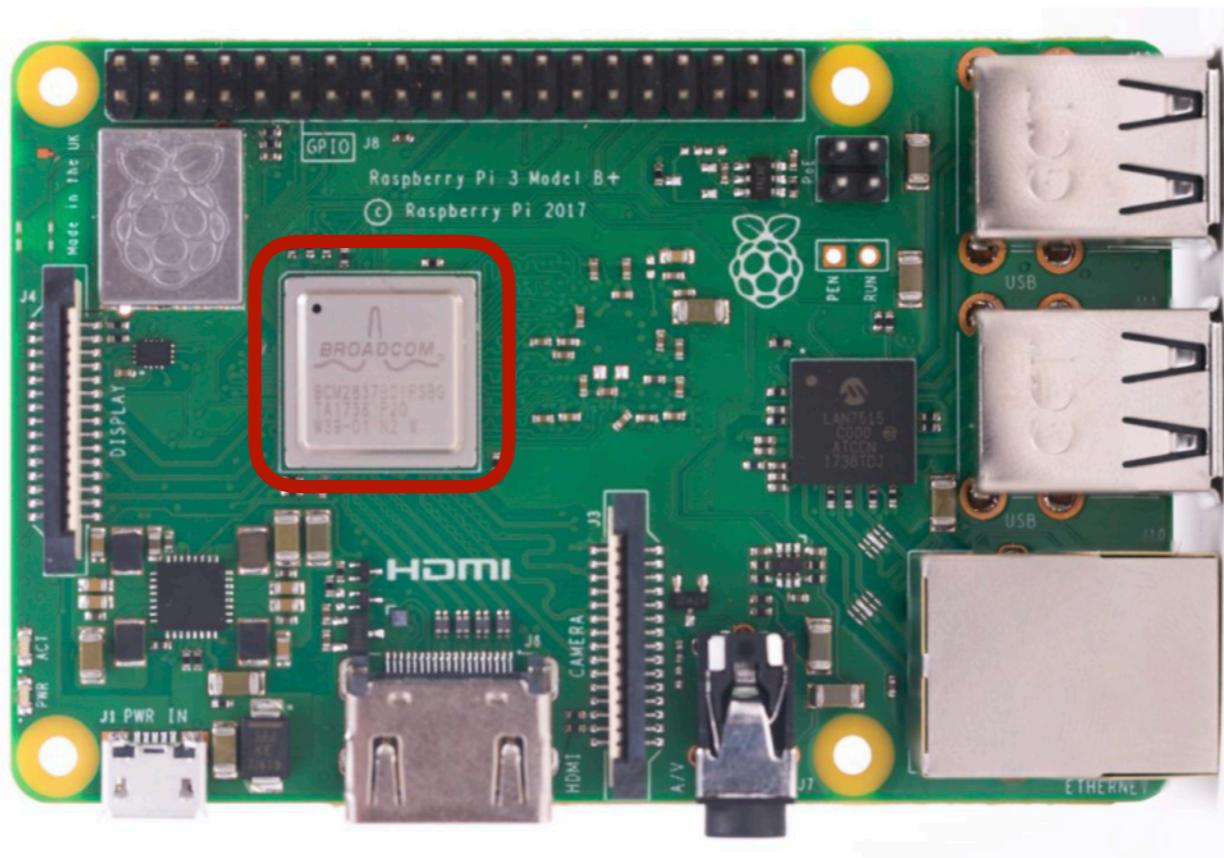

Quad-core 64-bit ARM Cortex-A53

1.2GHz


# Raspberry Pi 3 Model B

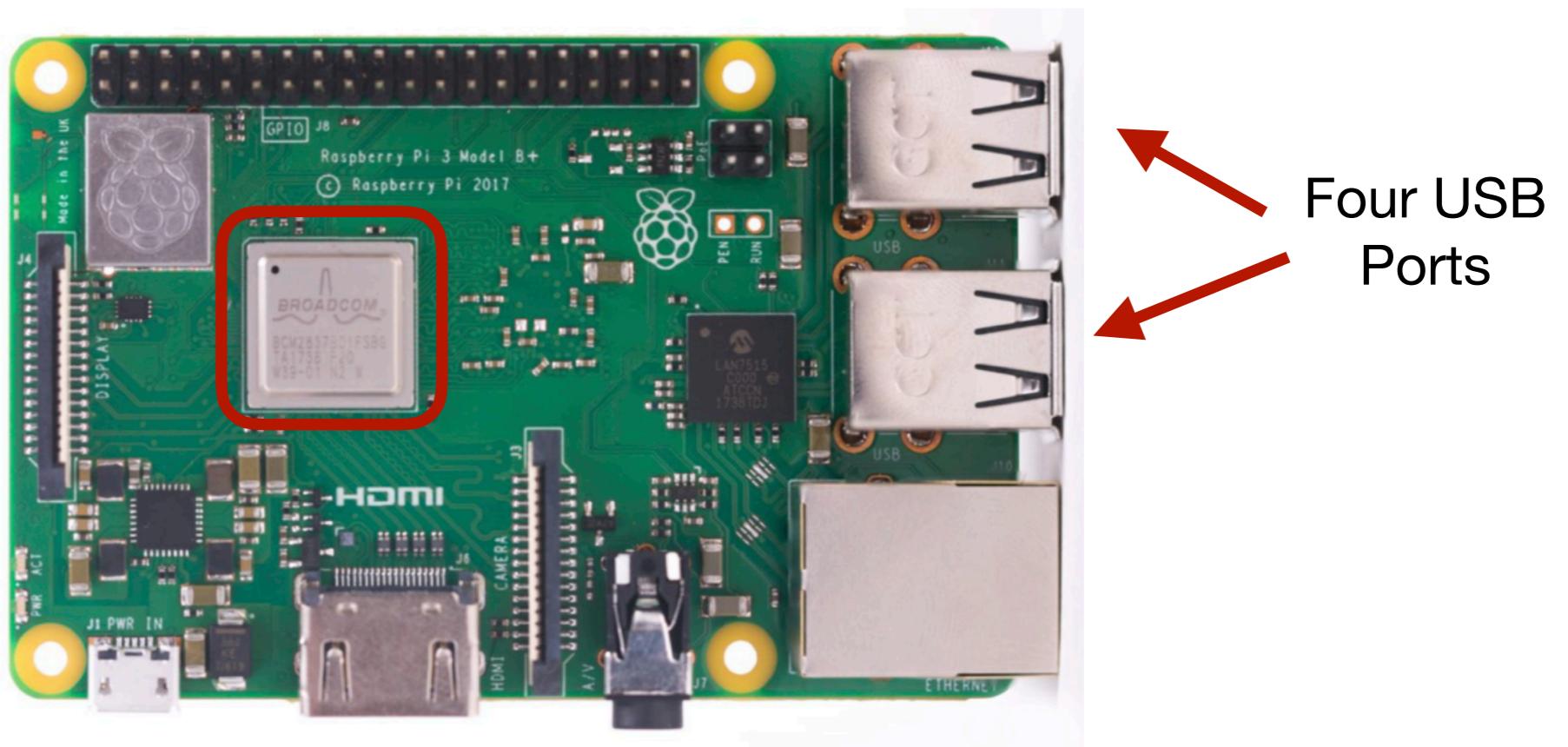

Quad-core 64-bit ARM Cortex-A53

1.2GHz


# Raspberry Pi 3 Model B

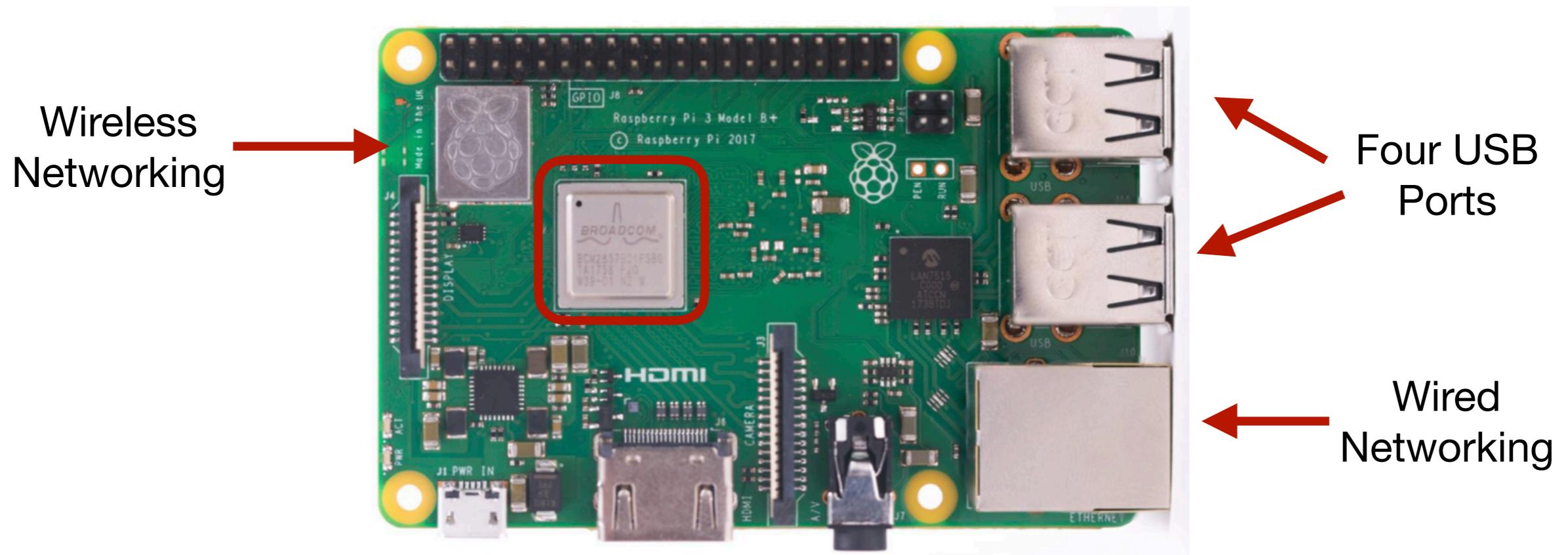


Quad-core 64-bit ARM Cortex-A53

1.2GHz


# Raspberry Pi 3 Model B

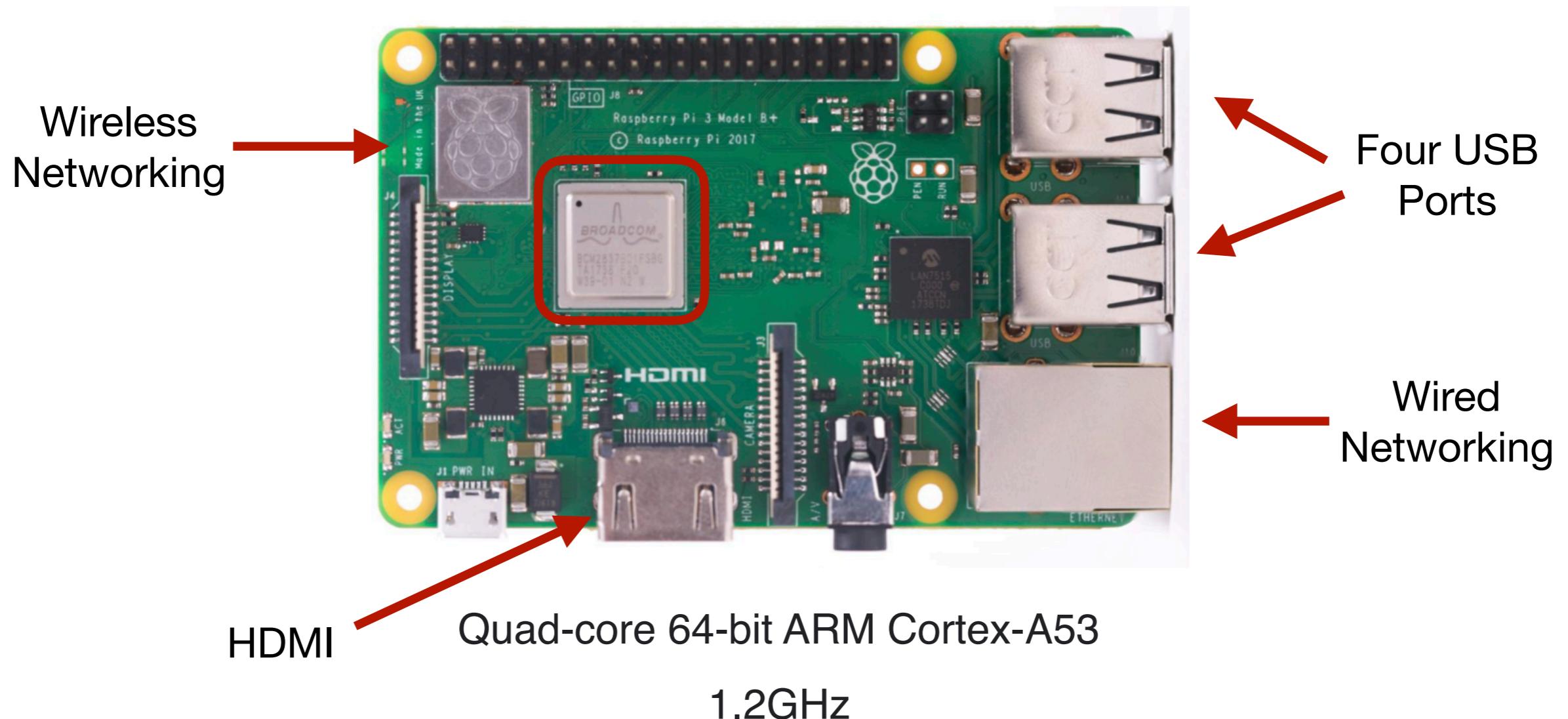


# Raspberry Pi 3 Model B

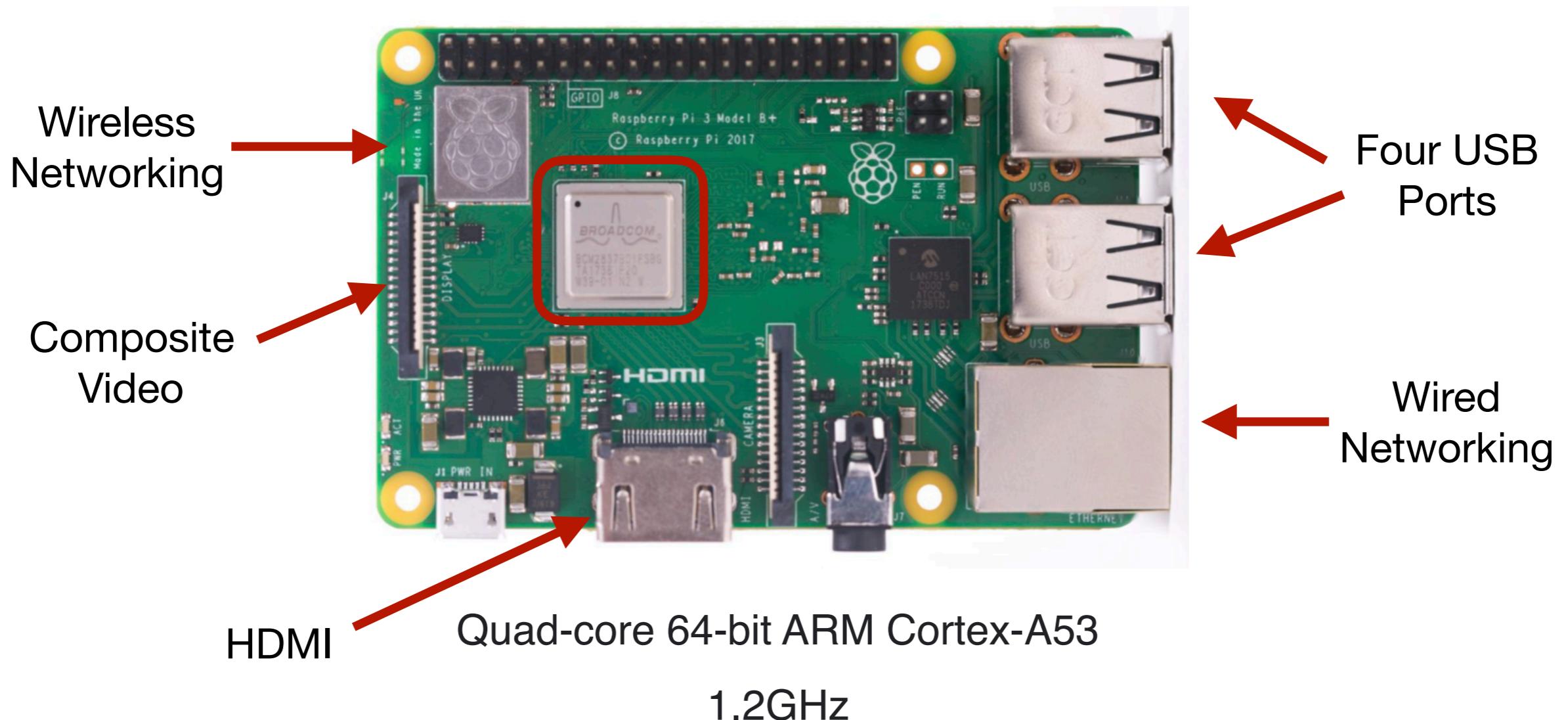


# Raspberry Pi 3 Model B

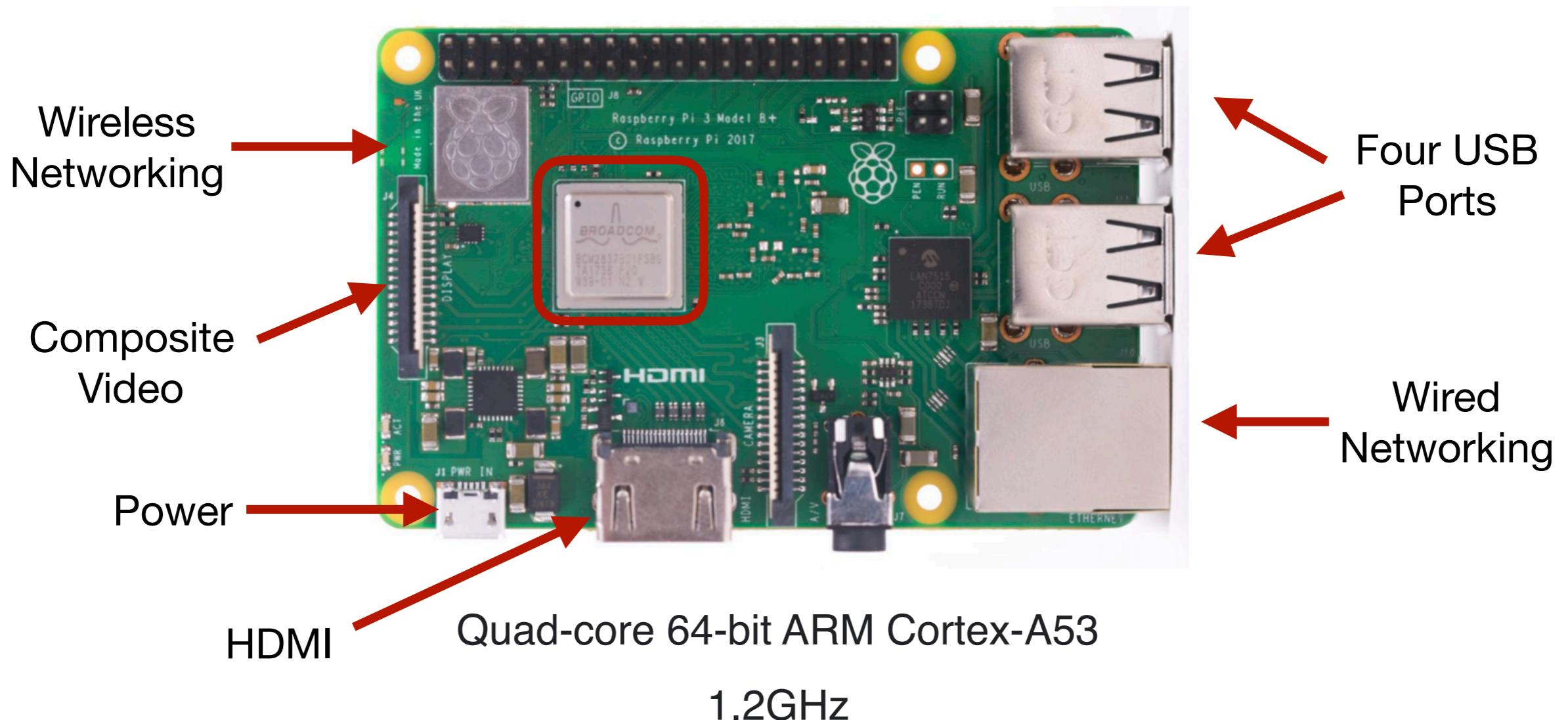


# Raspberry Pi 3 Model B

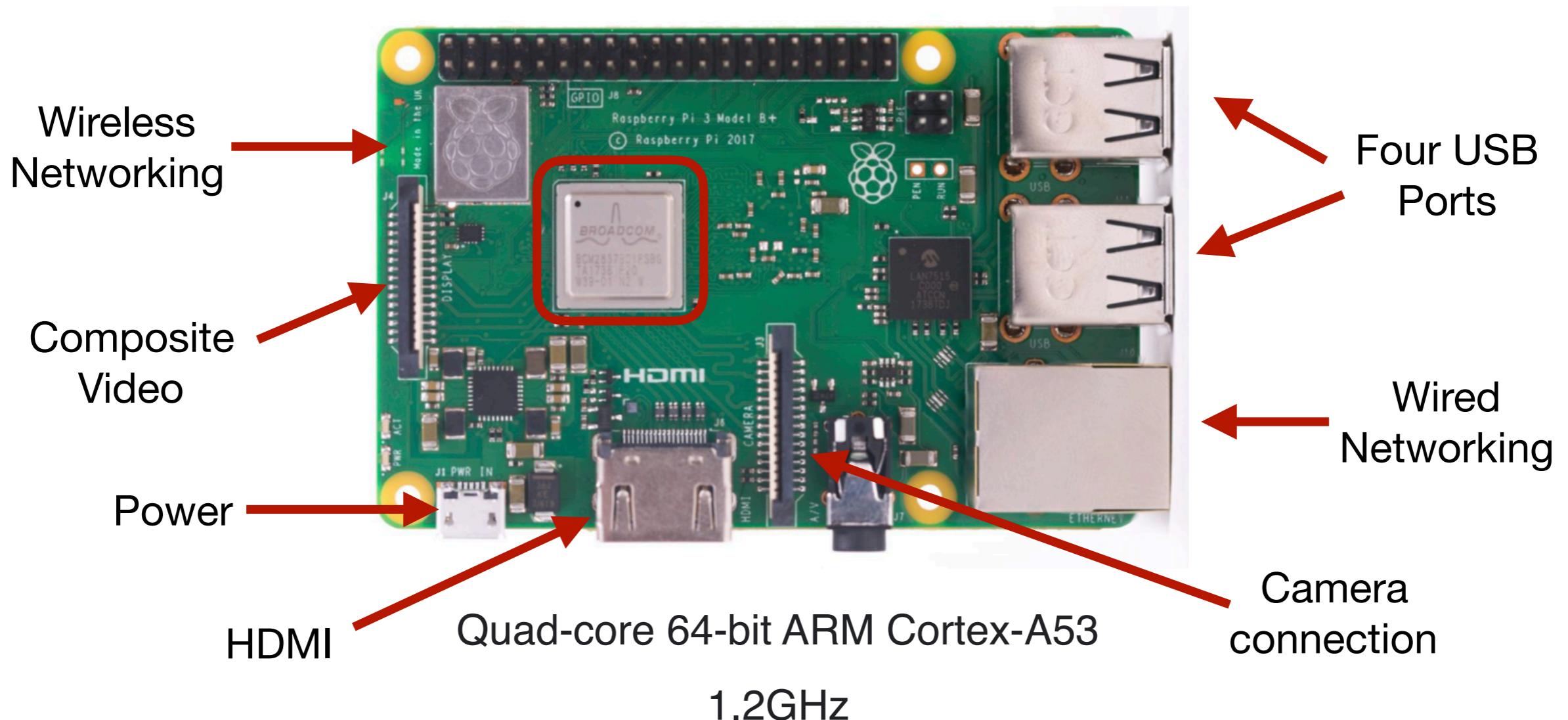

# Raspberry Pi 3 Model B

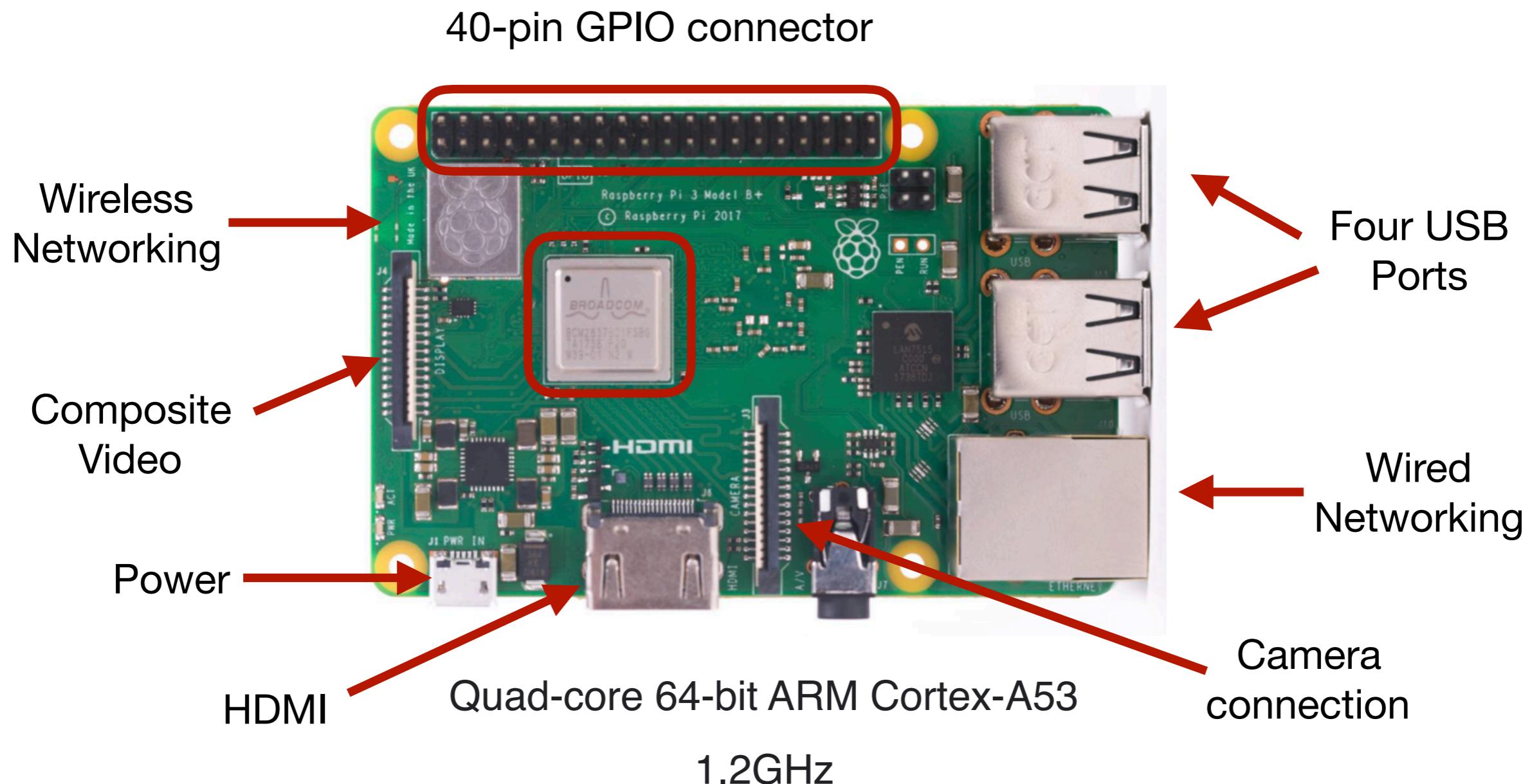


# Raspberry Pi 3 Model B

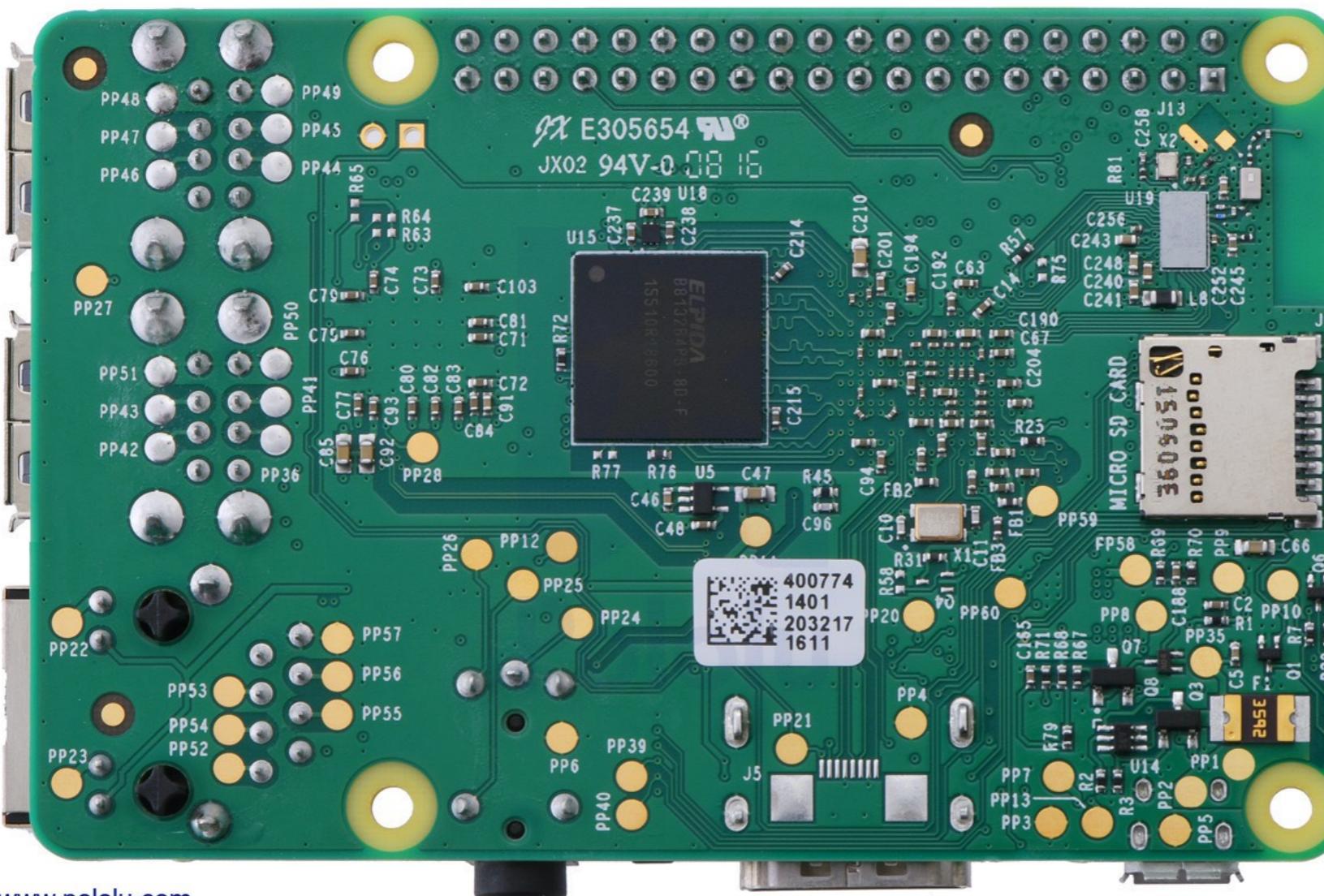

[www.pololu.com](http://www.pololu.com)

<https://developer.android.com/things/hardware/raspberrypi.html>

# Raspberry Pi 3 Model B

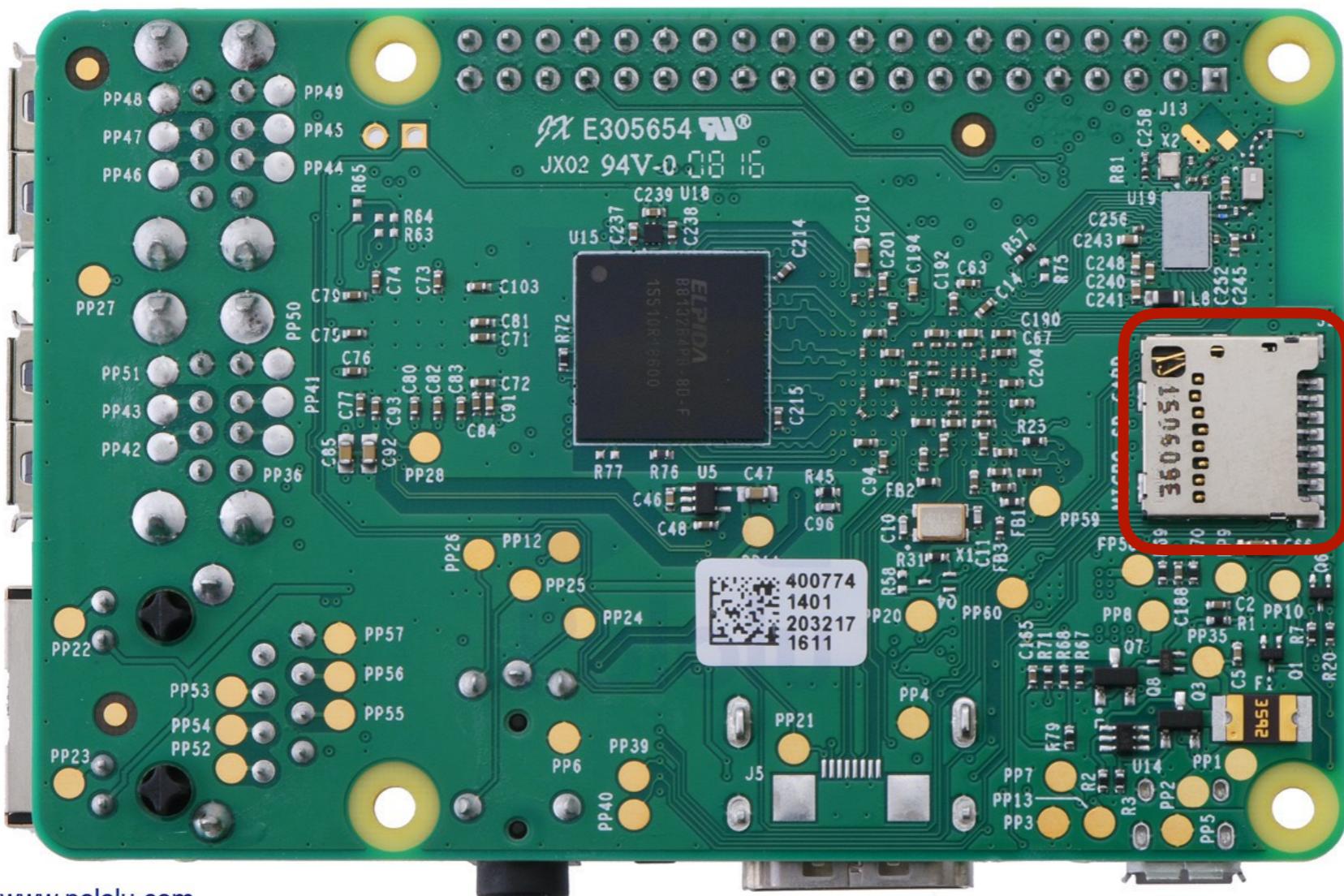




Micro SD  
card reader


[www.pololu.com](http://www.pololu.com)

<https://developer.android.com/things/hardware/raspberrypi.html>

# I/O Pinouts

GPIO Signal	Alternate Functions	
BCM2	I2C1 (SDA)	
BCM3	I2C1 (SCL)	
BCM7	SPI0 (SS1)	
BCM8	SPI0 (SS0)	
BCM9	SPI0 (MISO)	
BCM10	SPI0 (MOSI)	
BCM11	SPI0 (SCLK)	
BCM13	PWM1	
BCM14	UART0 (TXD)	MINIUART (TXD)
BCM15	UART0 (RXD)	MINIUART (RXD)
BCM18	I2S1 (BCLK)	PWM0
BCM19	I2S1 (LRCLK)	
BCM20	I2S1 (SDIN)	
BCM21	I2S1 (SDOUT)	

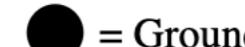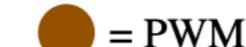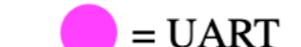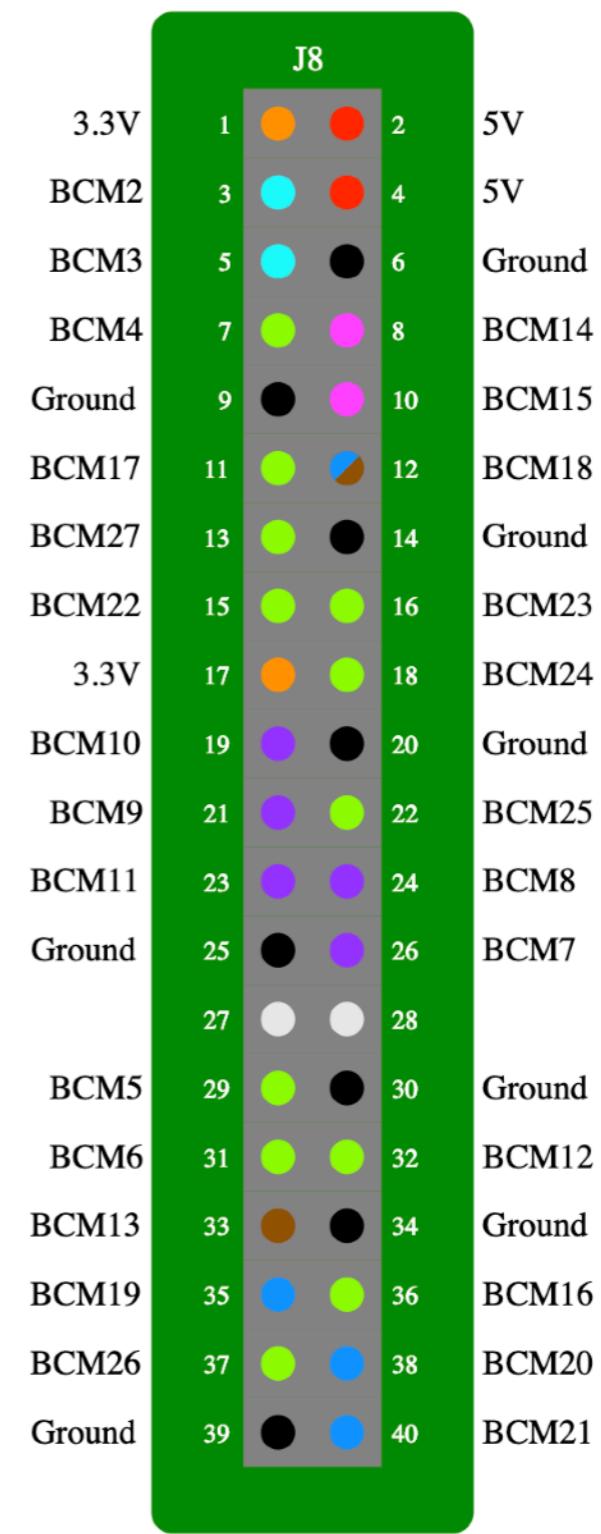 = 5V       = 1.8V       = GPIO       = I2C       = SPI  
 = 3.3V       = Ground       = PWM       = I2S       = UART



# Output and Input

- Digital Pins
  - Two values:
    - Low (0)
    - High (1)
  - Acts either:
    - Battery (OUTPUT)
    - Voltage meter (INPUT)


J8		
3.3V	1	2
BCM2	3	4
BCM3	5	6
BCM4	7	8
Ground	9	10
BCM17	11	12
BCM27	13	14
BCM22	15	16
3.3V	17	18
BCM10	19	20
BCM9	21	22
BCM11	23	24
Ground	25	26
	27	28
BCM5	29	30
BCM6	31	32
BCM13	33	34
BCM19	35	36
BCM26	37	38
Ground	39	40

# Output

J8			
3.3V	1	2	5V
BCM2	3	4	5V
BCM3	5	6	Ground
BCM4	7	8	BCM14
Ground	9	10	BCM15
BCM17	11	12	BCM18
BCM27	13	14	Ground
BCM22	15	16	BCM23
3.3V	17	18	BCM24
BCM10	19	20	Ground
BCM9	21	22	BCM25
BCM11	23	24	BCM8
Ground	25	26	BCM7
	27	28	
BCM5	29	30	Ground
BCM6	31	32	BCM12
BCM13	33	34	Ground
BCM19	35	36	BCM16
BCM26	37	38	BCM20
Ground	39	40	BCM21


- Pin 12 can act like a battery (OUTPUT)
  - LOW - 0V
  - HIGH - 5V, 3.3V or 1.8V

# Output

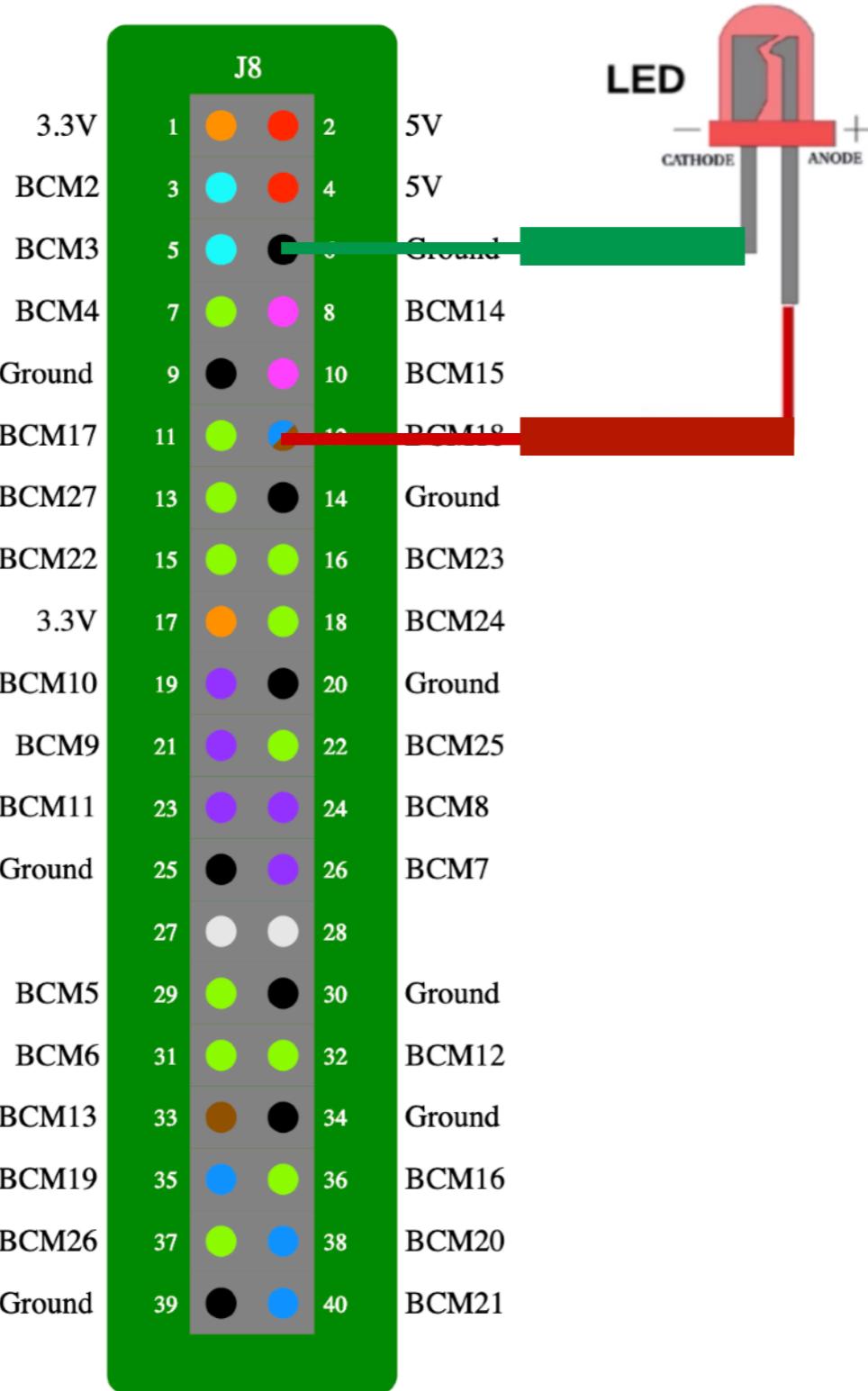

- Pin 12 can act like a battery (OUTPUT)
  - LOW - 0V
  - HIGH - 5V, 3.3V or 1.8V


# Output

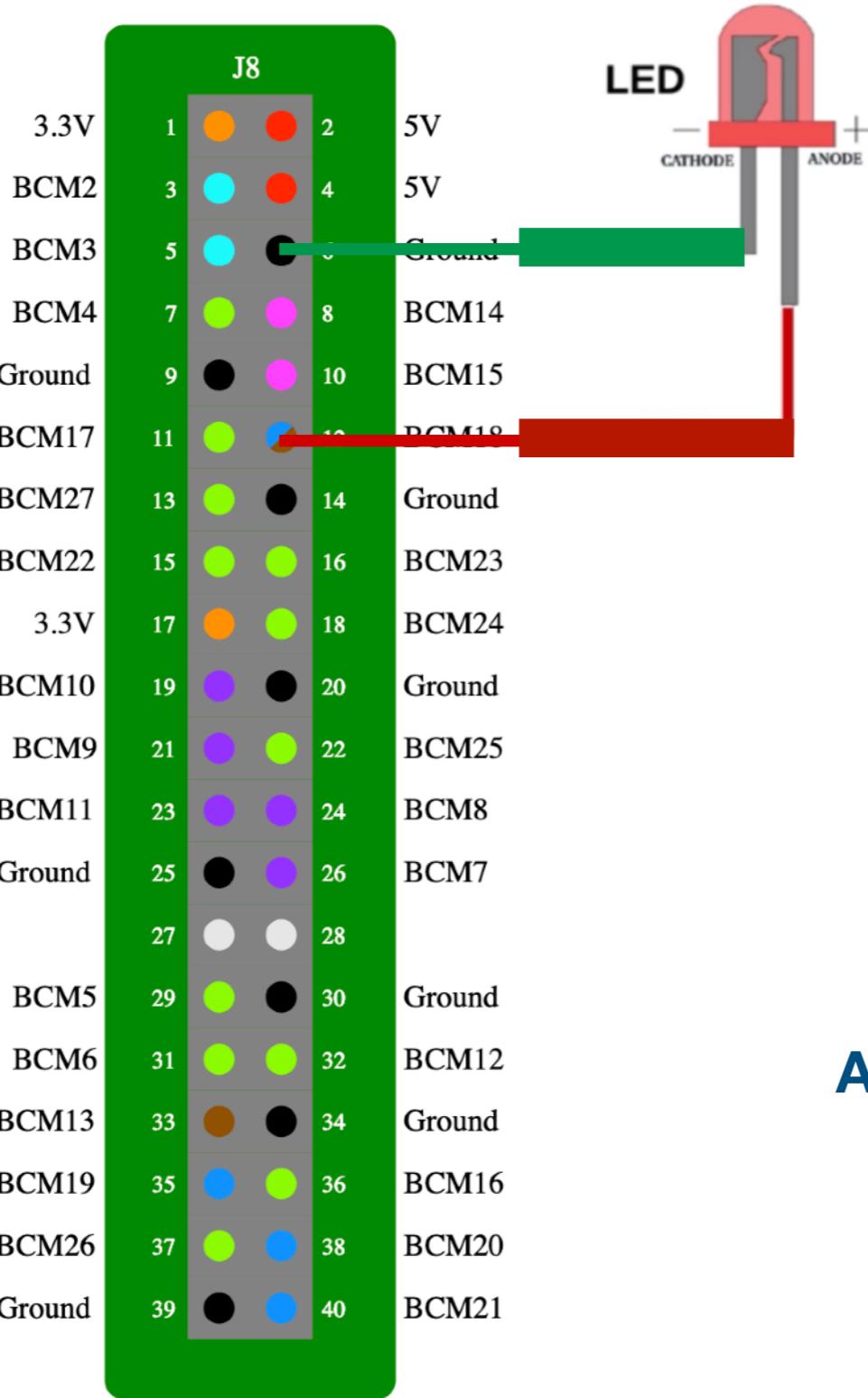

- Pin 12 can act like a battery (OUTPUT)
  - LOW - 0V
  - HIGH - 5V, 3.3V or 1.8V

Arduino

# Output

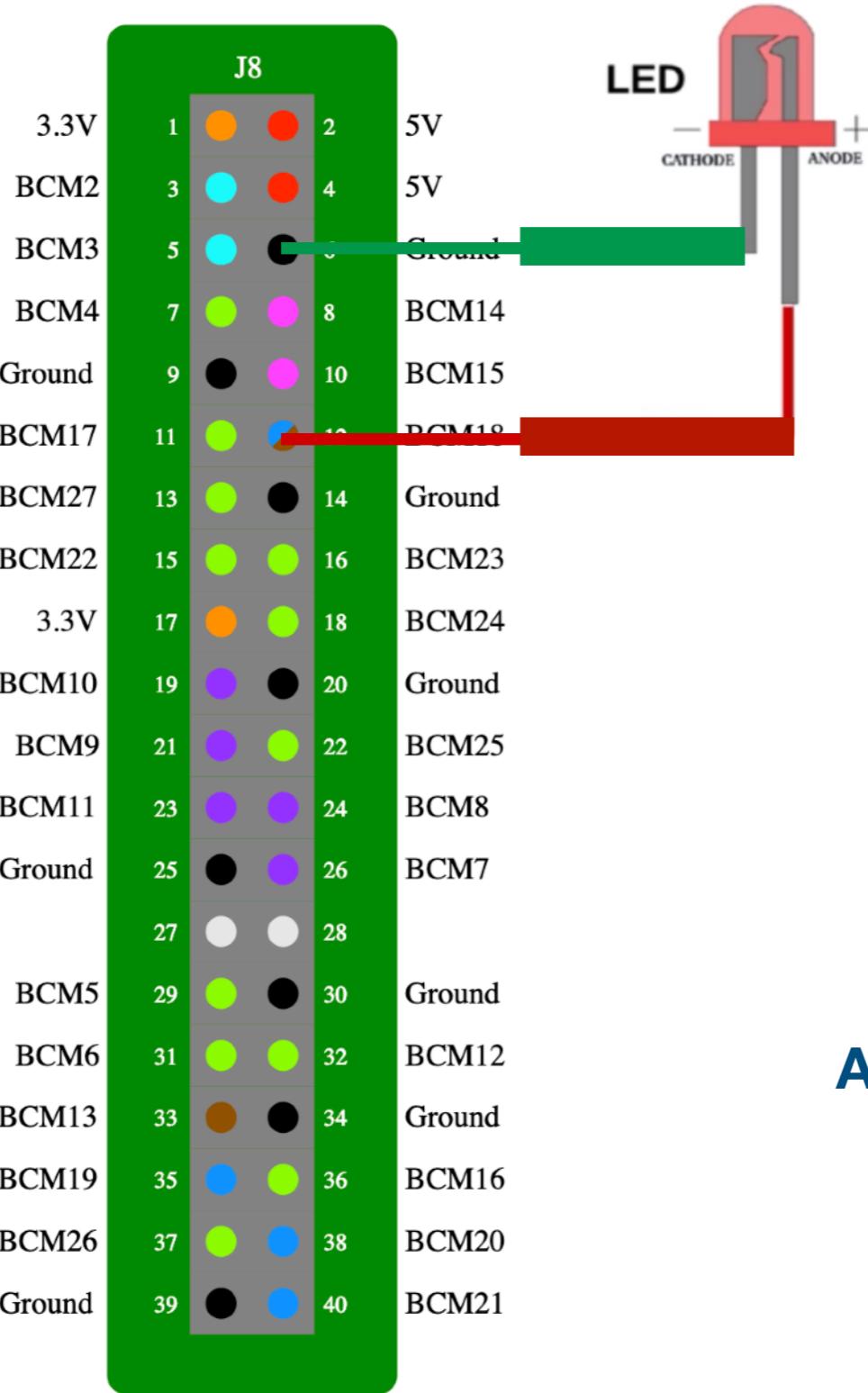


- Pin 12 can act like a battery (OUTPUT)
  - LOW - 0V
  - HIGH - 5V, 3.3V or 1.8V

Arduino


Raspberry Pi

# Output

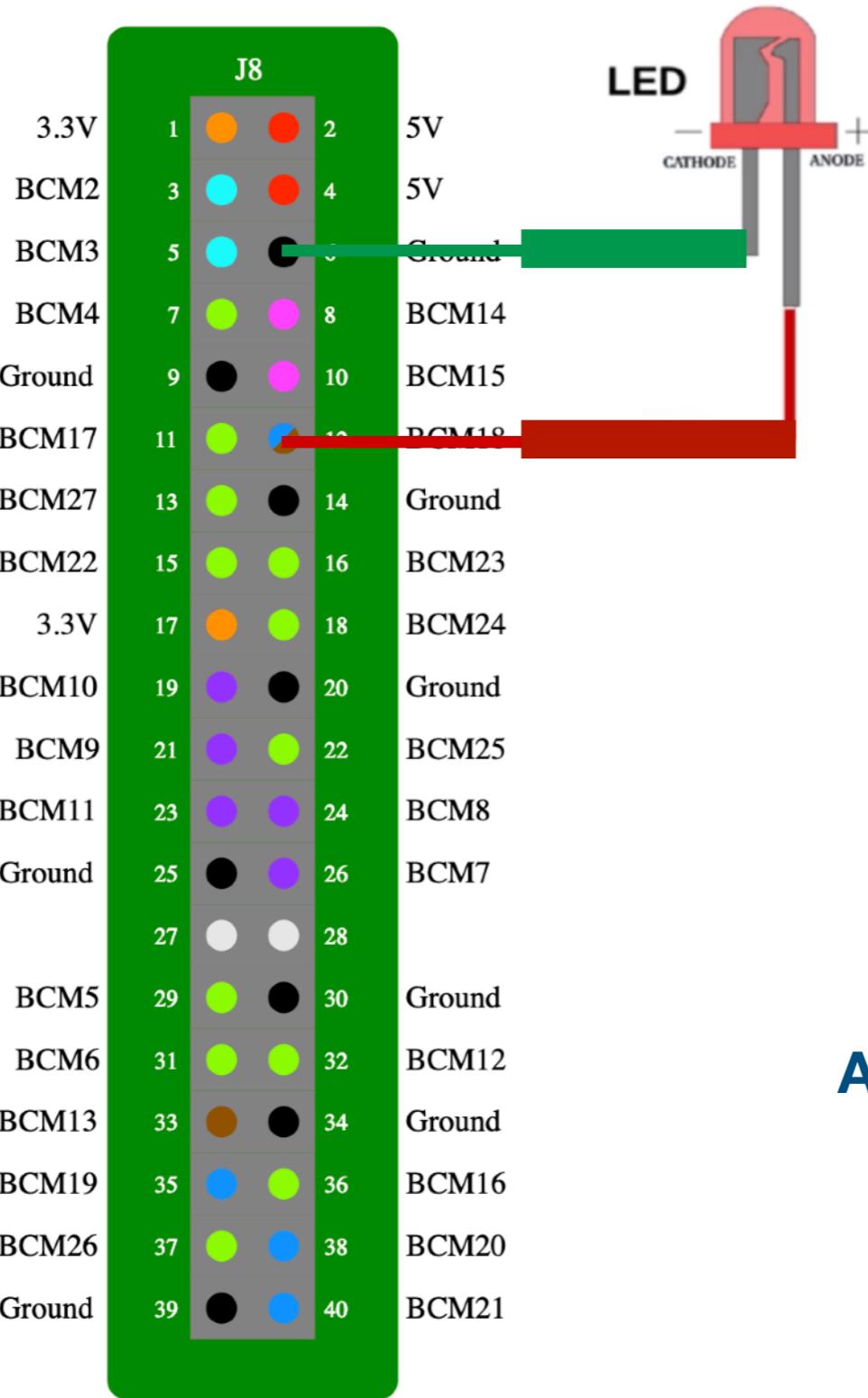

- Pin 12 can act like a battery (OUTPUT)
    - LOW - 0V
    - HIGH - 5V, 3.3V or 1.8V
- Arduino   
Raspberry Pi   
Others

# Output

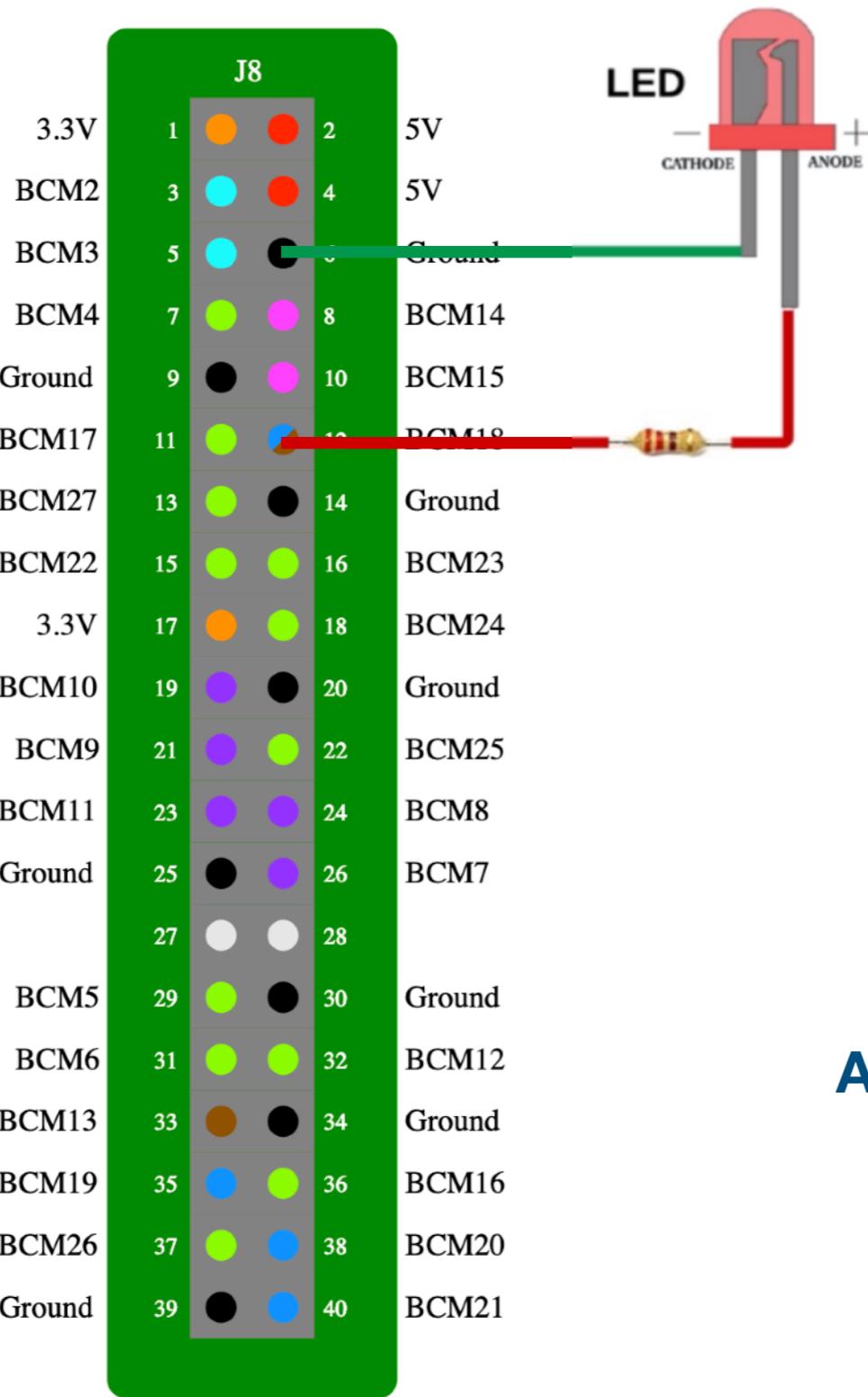




- Pin 12 can act like a battery (OUTPUT)
  - LOW - 0V
  - HIGH - 5V, 3.3V or 1.8V

Arduino





Raspberry Pi

Others





# What resistor to use?

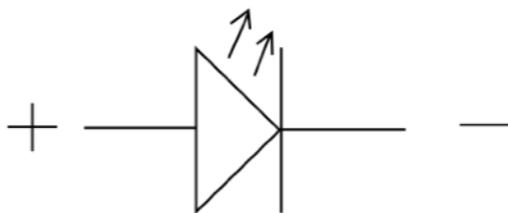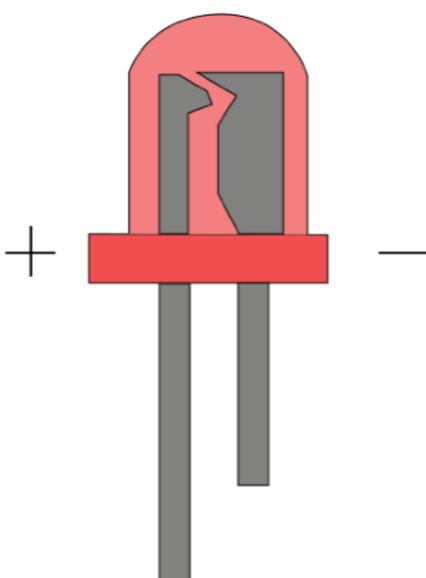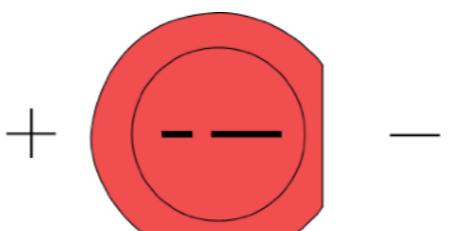





# What resistor to use?

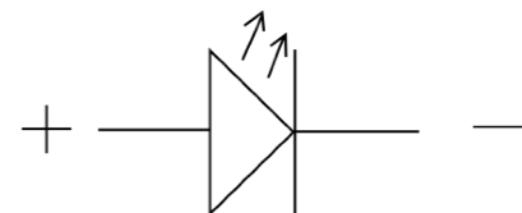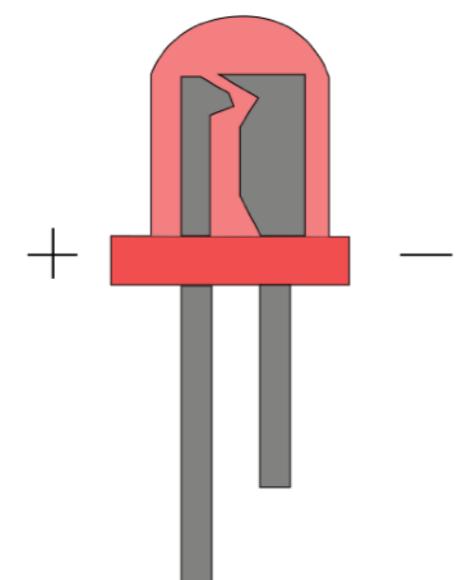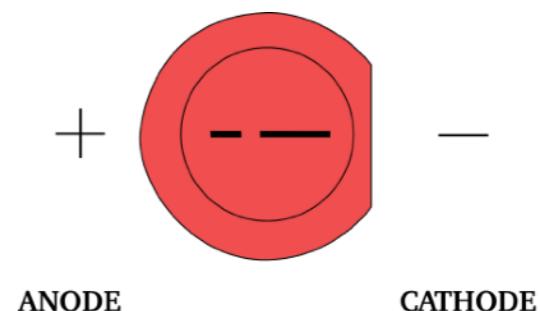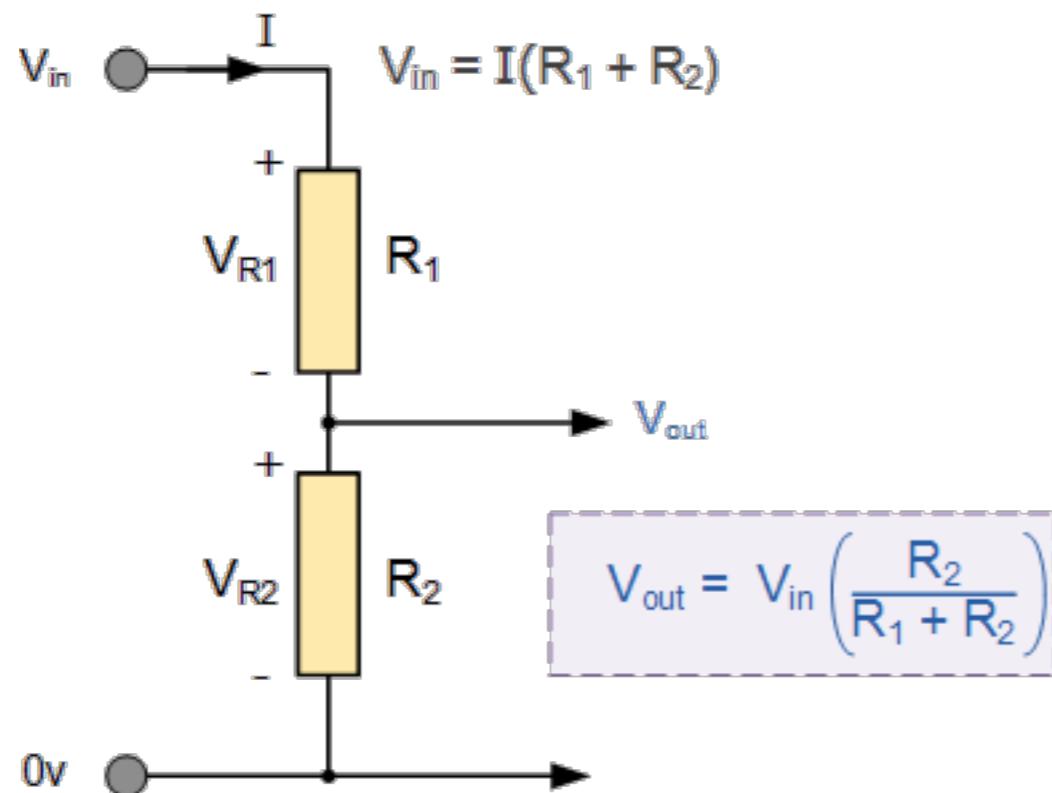



# What resistor to use?

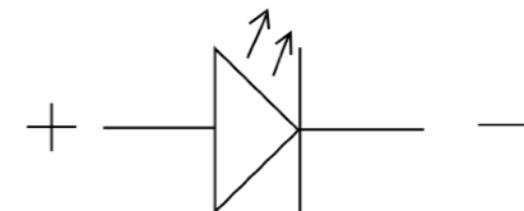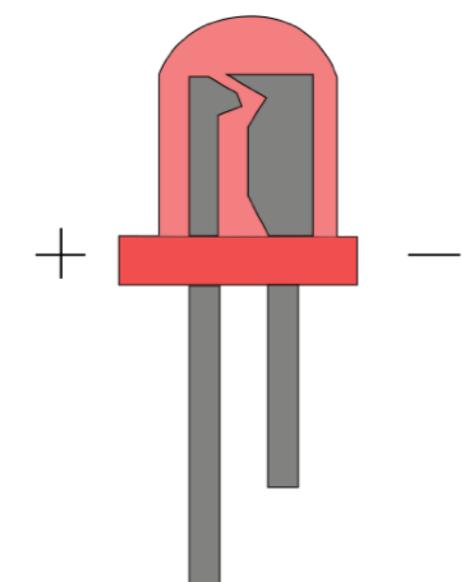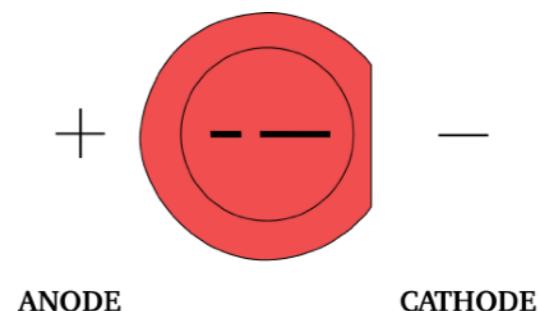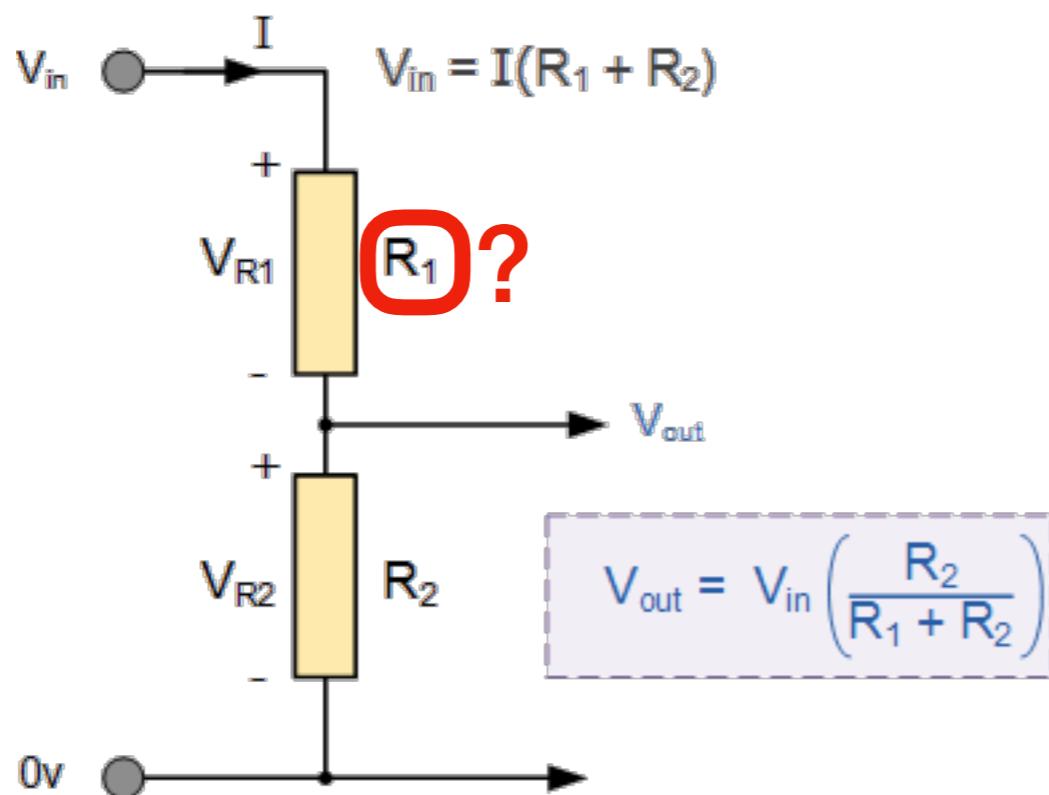



# What resistor to use?

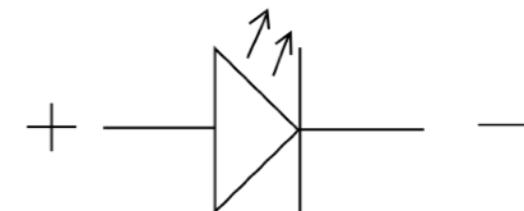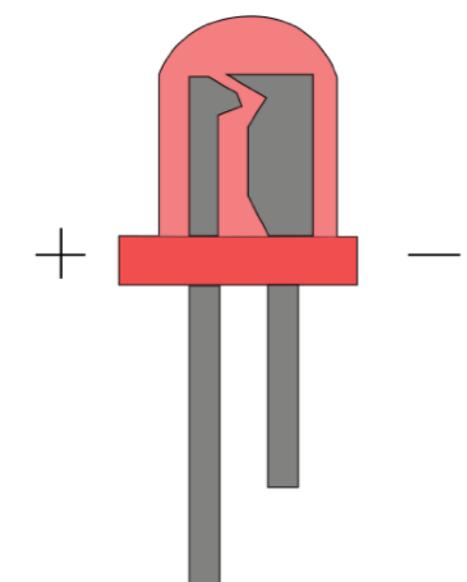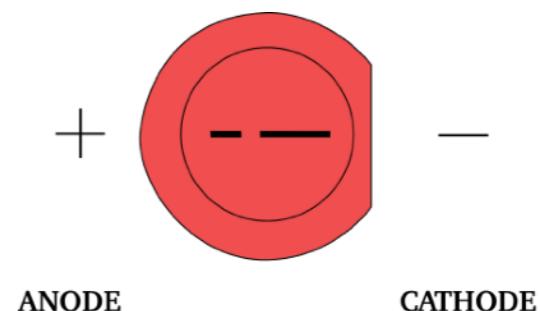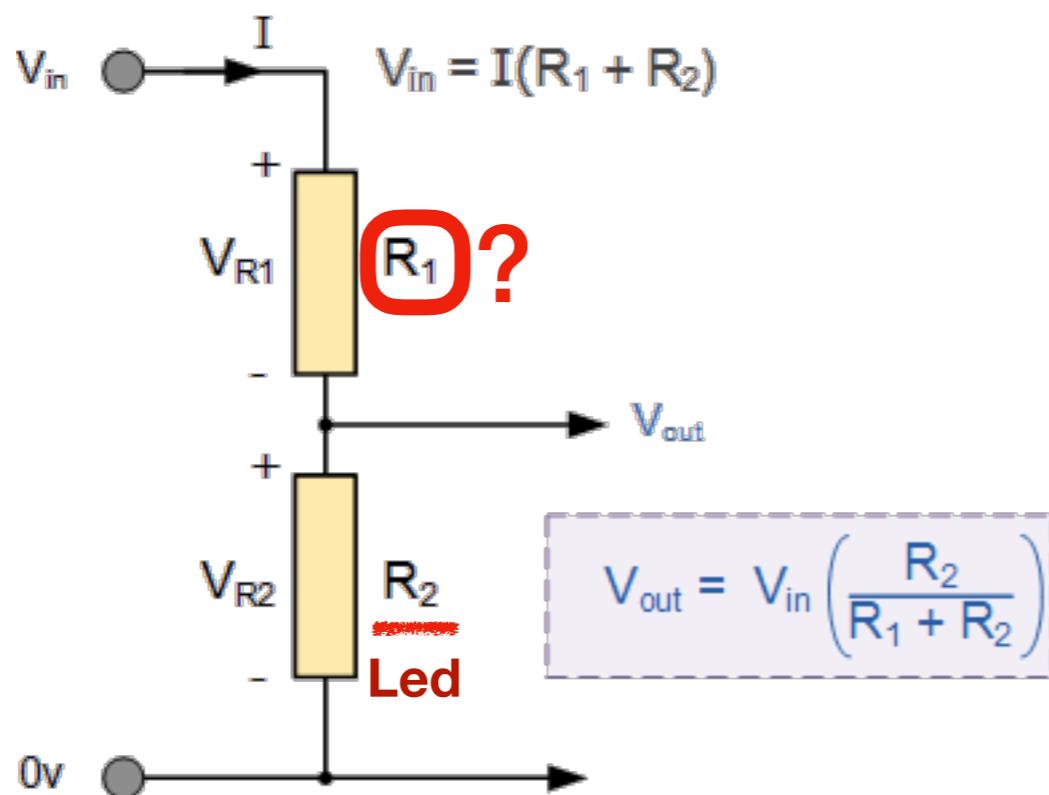



# What resistor to use?

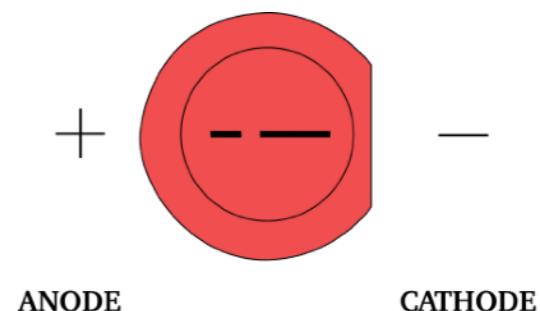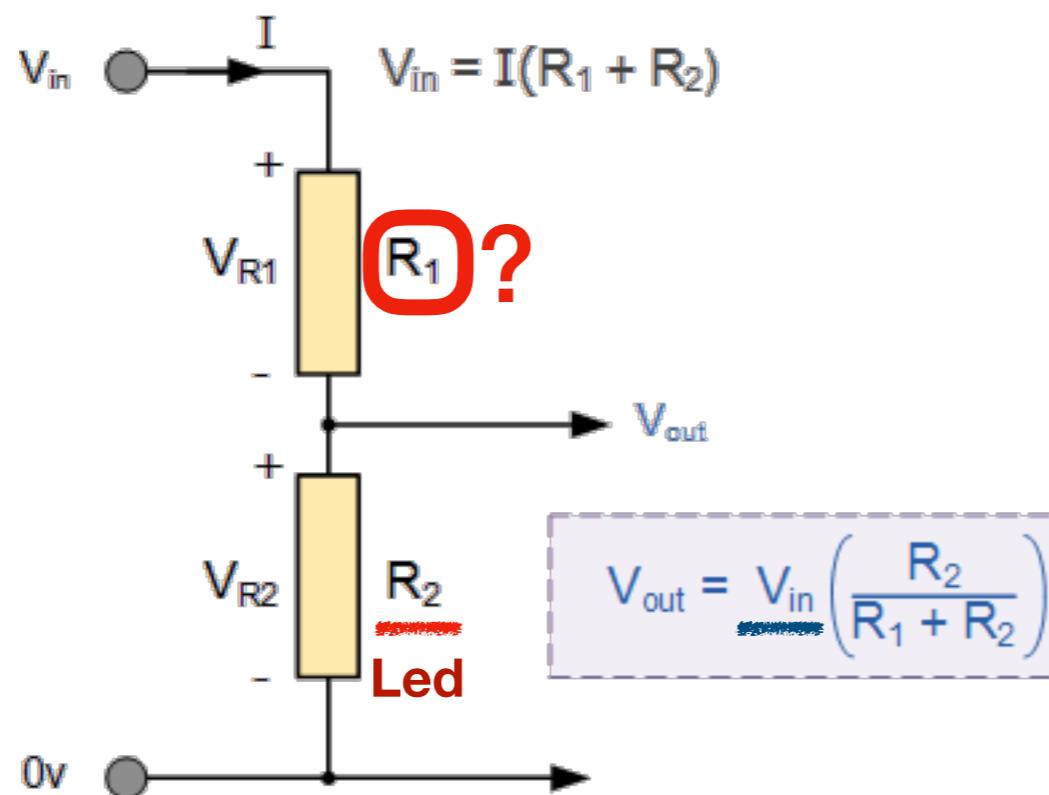





ANODE CATHODE

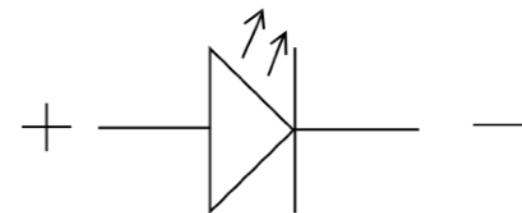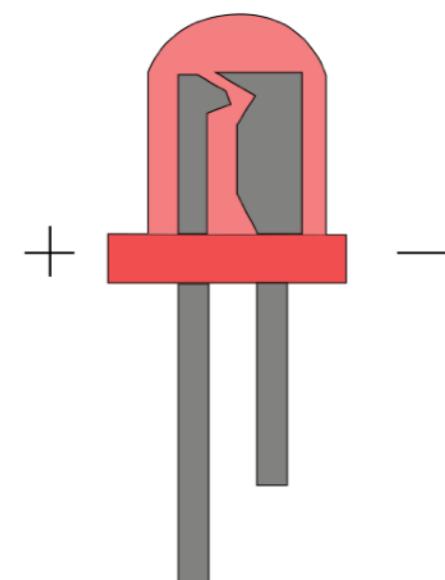





# What resistor to use?

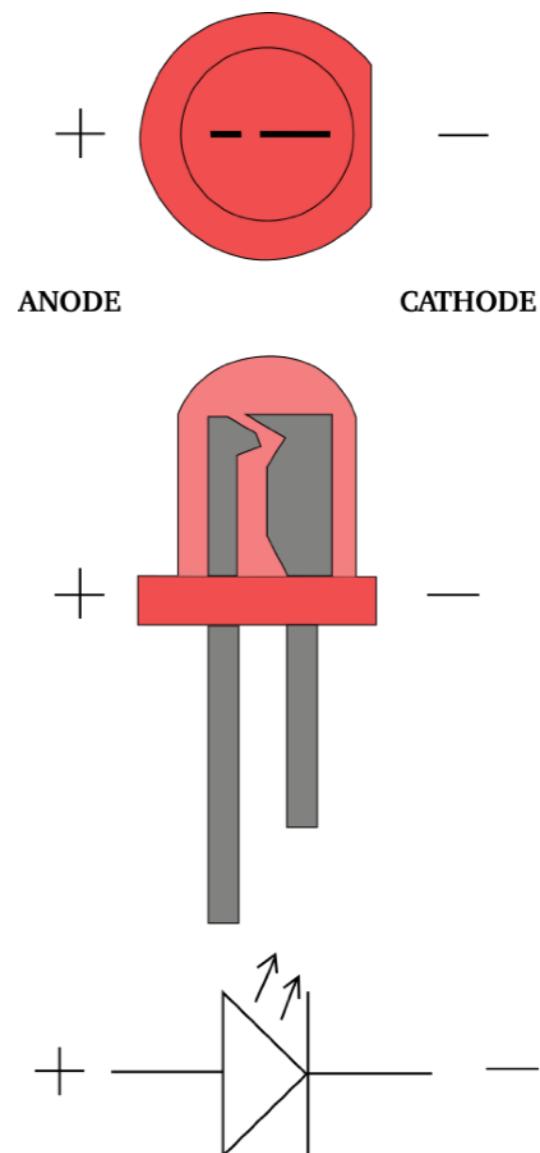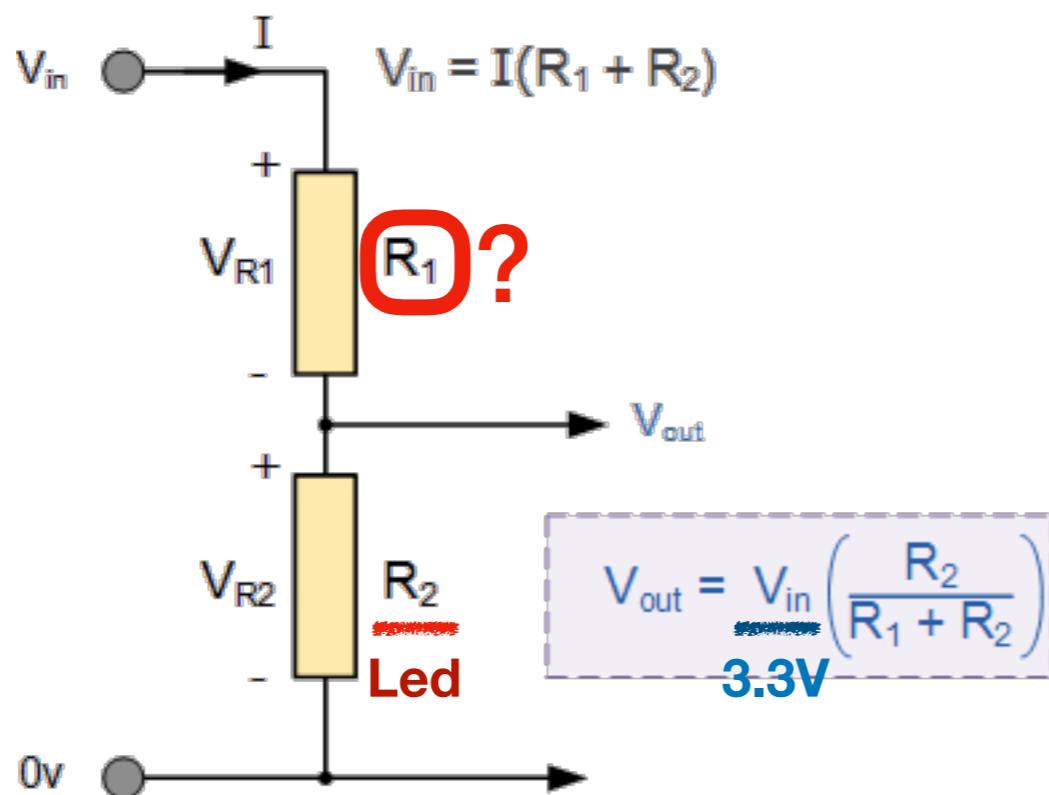

# What resistor to use?

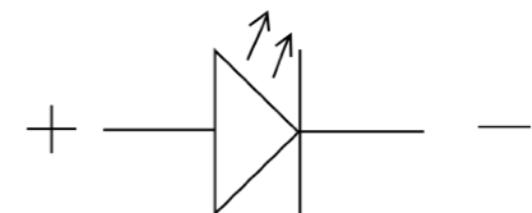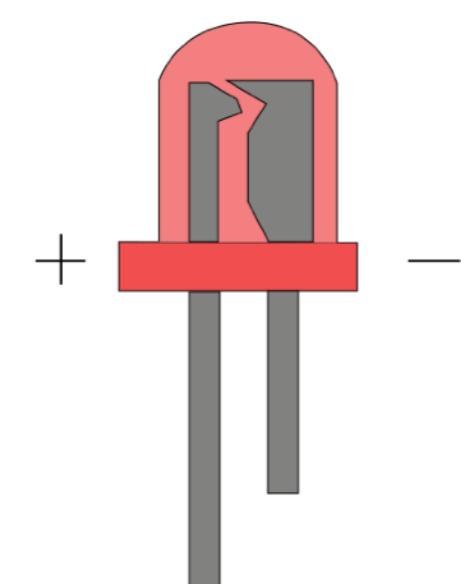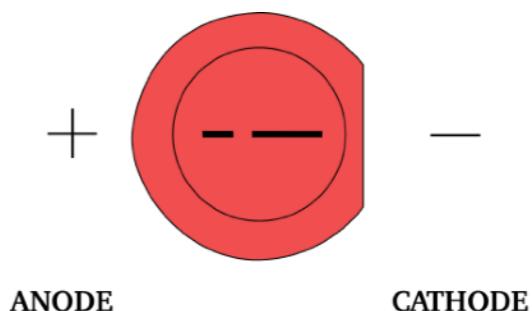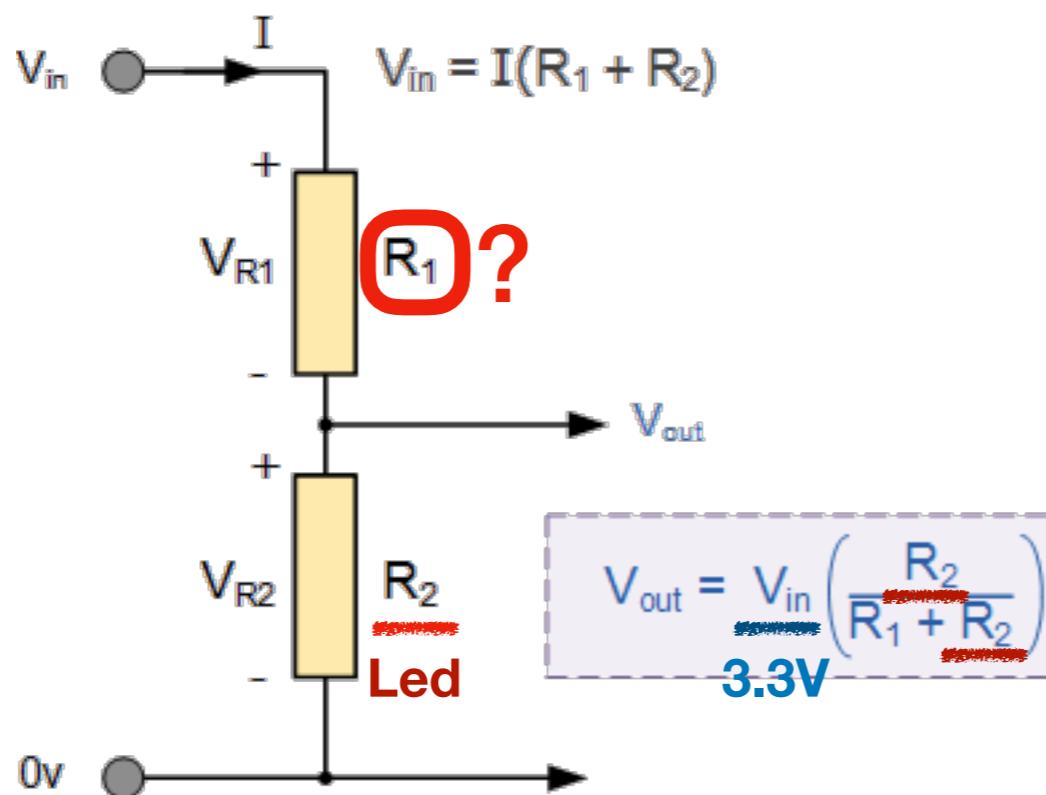

# What resistor to use?

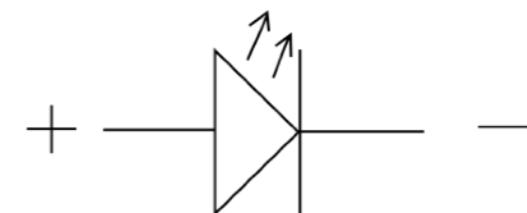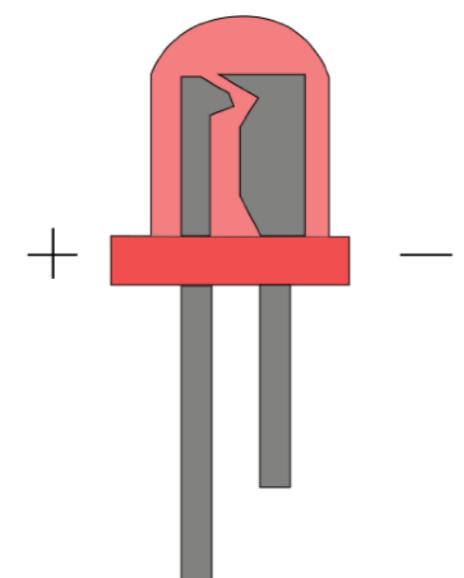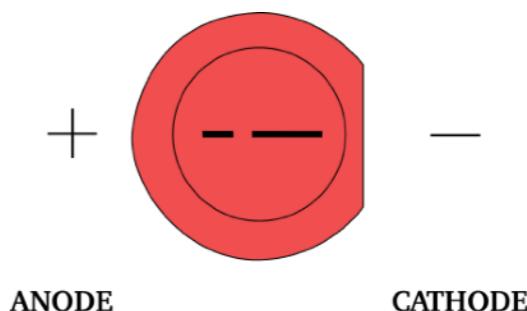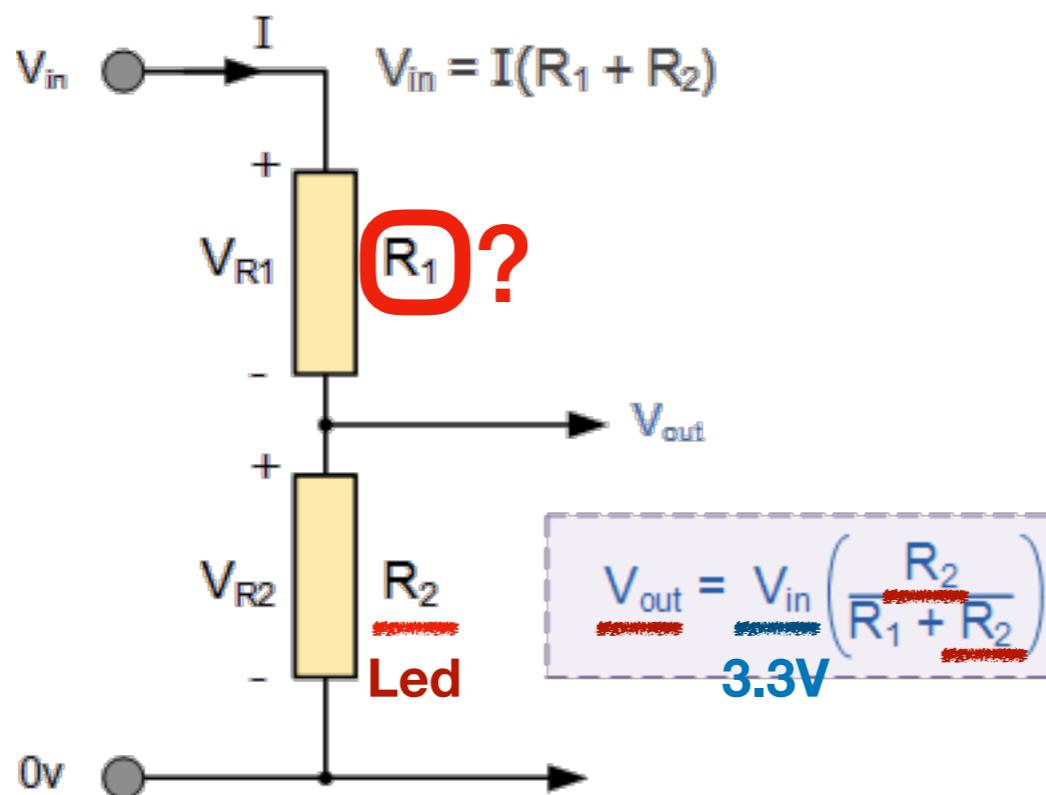

# Led

## LED - Basic Red 5mm

● COM-09590 ROHS ✓ J5 F 3D

\$0.35

Volume sales pricing

- 1 +

ADD TO CART

Quantity discounts available

DESCRIPTION

FEATURES

DOCUMENTS

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Led

## LED - Basic Red 5mm

● COM-09590 ROHS ✓ J5 F 3D

\$0.35

Volume sales pricing

- 1 +

**ADD TO CART**

Quantity discounts available

**DESCRIPTION**

FEATURES

DOCUMENTS

---

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Led

## LED - Basic Red 5mm

COM-09590 ROHS ✓ J5 F 3D

\$0.35

Volume sales pricing

- 1 +

ADD TO CART

Quantity discounts available

DESCRIPTION

FEATURES

DOCUMENTS

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Led

## LED - Basic Red 5mm

COM-09590 ROHS ✓ JST F 3D

\$0.35

Volume sales pricing

- 1 +


**ADD TO CART**

Quantity discounts available


**DESCRIPTION**

FEATURES


DOCUMENTS

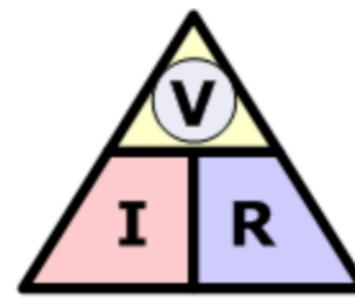

$$\textcircled{V} = I \times R$$

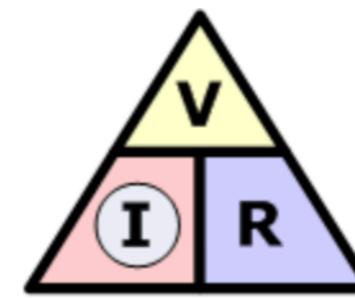

$$\textcircled{I} = \frac{V}{R}$$

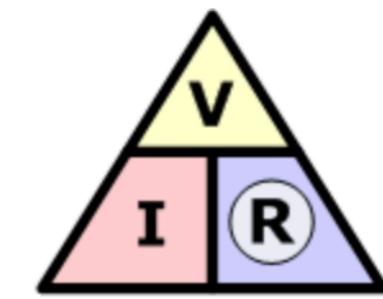


$$\textcircled{R} = \frac{V}{I}$$

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Compute R1

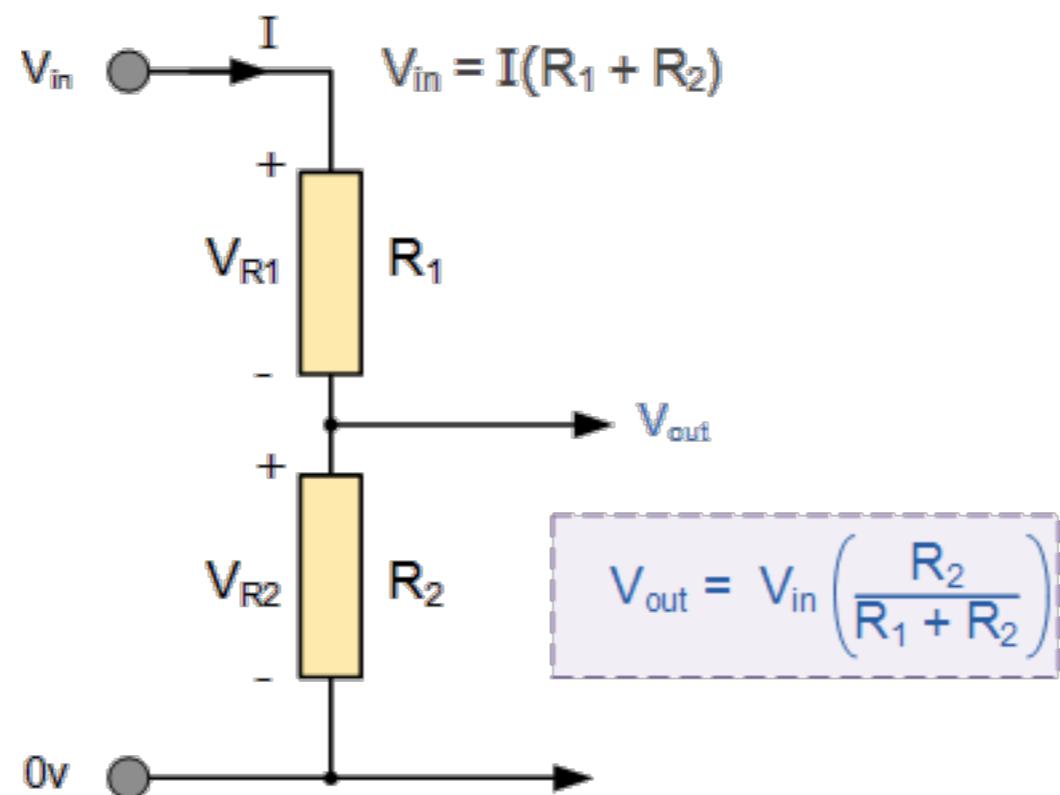

# Compute R1

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

# Compute R1

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

# Compute R1

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

$$R_2 V_{in} = R_1 V_{out} + R_2 V_{out}$$

# Compute R1

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

$$R_2 V_{in} = R_1 V_{out} + R_2 V_{out}$$

$$R_1 = \frac{R_2(V_{in} - V_{out})}{V_{out}}$$

# Compute R1

$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

$$R_2 V_{in} = R_1 V_{out} + R_2 V_{out}$$

$$R_1 = \frac{R_2(V_{in} - V_{out})}{V_{out}}$$



$$\textcircled{\textbf{R}} = \frac{V}{I}$$

# Compute R1


$$V_{out} = V_{in} \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\frac{R_2}{R_1 + R_2} = \frac{V_{out}}{V_{in}}$$

$$R_2 V_{in} = R_1 V_{out} + R_2 V_{out}$$

$$R_1 = \frac{R_2(V_{in} - V_{out})}{V_{out}}$$
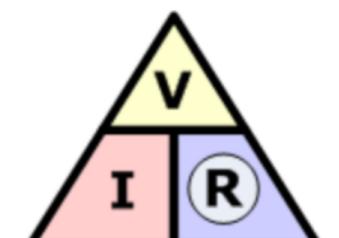
$$R_1 = \frac{\frac{V_{out}}{I_{out}}(V_{in} - V_{out})}{V_{out}}$$



$$\textcircled{\textbf{R}} = \frac{V}{I}$$

# Compute R1

$$R_1 = \frac{V_{in} - V_{out}}{I_{out}}$$

# Compute R1

## LED - Basic Red 5mm

● COM-09590 ROHS ✓   

\$0.35

Volume sales pricing

$$R_1 = \frac{V_{in} - V_{out}}{I_{out}}$$

- 1 +

**ADD TO CART**

Quantity discounts available

**DESCRIPTION**

FEATURES

DOCUMENTS

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Compute R1

## LED - Basic Red 5mm

● COM-09590 ROHS ✓   

\$0.35

Volume sales pricing

$$R_1 = \frac{V_{in} - V_{out}}{I_{out}} = \frac{3.3V - 2V}{0.020A} = 65\Omega$$

- 1 +

**ADD TO CART**

Quantity discounts available

**DESCRIPTION**

FEATURES

DOCUMENTS

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

# Compute R1

## LED - Basic Red 5mm

● COM-09590 ROHS ✓   

\$0.35

Volume sales pricing

$$R_1 = \frac{V_{in} - V_{out}}{I_{out}} = \frac{3.3V - 2V}{0.020A} = 65\Omega$$

- 1 +

**ADD TO CART**

Quantity discounts available

**DESCRIPTION**

FEATURES

DOCUMENTS

LEDs - those blinky things. A must have for power indication, pin status, opto-electronic sensors, and fun blinky displays.

This is a very basic 5mm LED with a red lens. It has a typical forward voltage of 2.0V and a rated forward current of 20mA.

<http://www.ohmslawcalculator.com/led-resistor-calculator>

# Input


J8			
3.3V	1	2	5V
BCM2	3	4	5V
BCM3	5	6	Ground
BCM4	7	8	BCM14
Ground	9	10	BCM15
BCM17	11	12	BCM18
BCM27	13	14	Ground
BCM22	15	16	BCM23
3.3V	17	18	BCM24
BCM10	19	20	Ground
BCM9	21	22	BCM25
BCM11	23	24	BCM8
Ground	25	26	BCM7
	27	28	
BCM5	29	30	Ground
BCM6	31	32	BCM12
BCM13	33	34	Ground
BCM19	35	36	BCM16
BCM26	37	38	BCM20
Ground	39	40	BCM21

- In this case we are measuring  $V_{out}$
- Represented on one bit.


# Input

	J8		
3.3V	1	2	5V
BCM2	3	4	5V
BCM3	5	6	Ground
BCM4	7	8	BCM14
Ground	9	10	BCM15
BCM17	11	12	BCM18
BCM27	13	14	Ground
BCM22	15	16	BCM23
3.3V	17	18	BCM24
BCM10	19	20	Ground
BCM9	21	22	BCM25
BCM11	23	24	BCM8
Ground	25	26	BCM7
	27	28	
BCM5	29	30	Ground
BCM6	31	32	BCM12
BCM13	33	34	Ground
BCM19	35	36	BCM16
BCM26	37	38	BCM20
Ground	39	40	BCM21

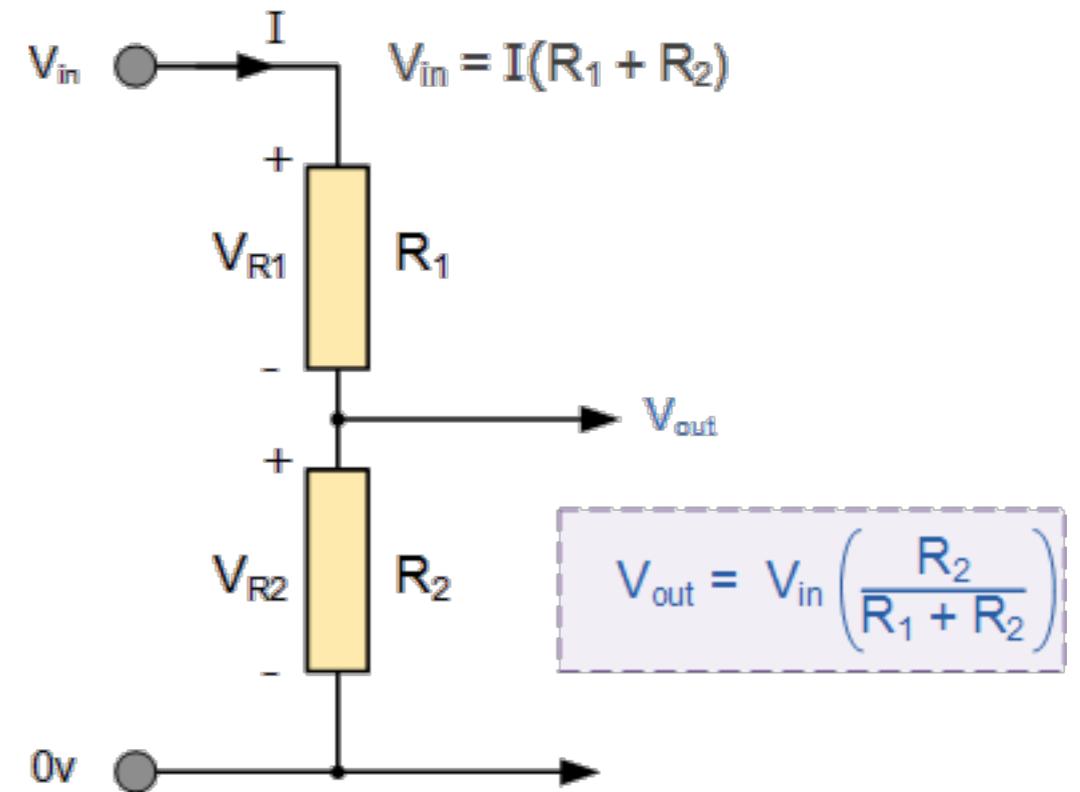- In this case we are measuring  $V_{out}$
- Represented on one bit.



# I/O Pinouts

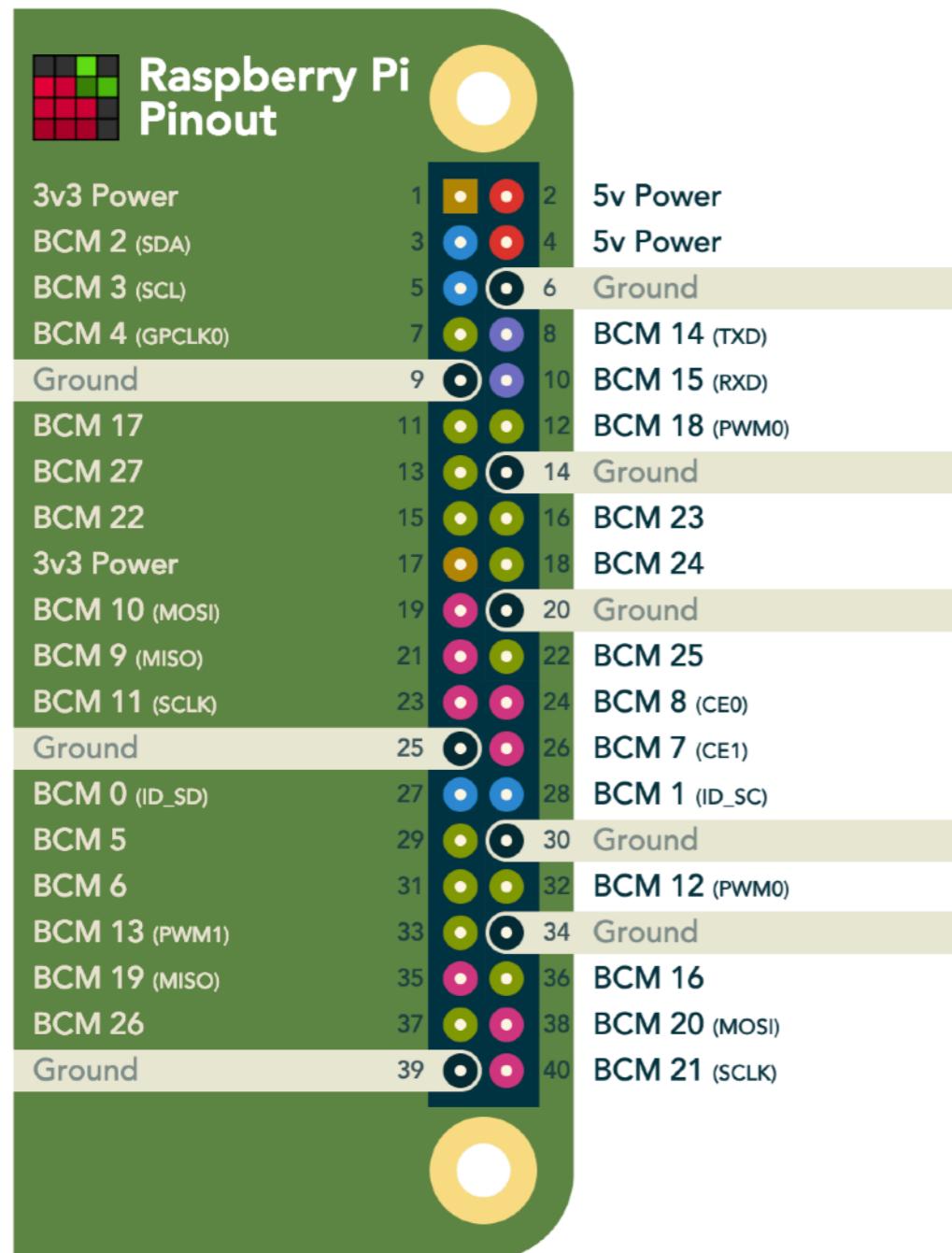

Ground    DPI    GPCLK    JTAG    1-WIRE    PCM    SDIO    I2C    SPI    UART    WiringPi

Browse more HATs, pHATs and add-ons »

**Arcade Bonnet**  
Connect joystick, buttons and speakers to your Pi

**MotoZero**  
Control 4 motors from your Raspberry Pi

**XBee Shield**  
Use XBee modules with the Raspberry Pi

**Score:Zero**  
A super-simple and stylish soldering kit - makes an NES-style games controller when assembled.

## Ground

The Ground pins on the Raspberry Pi are all electrically connected, so it doesn't matter which one you use if you're wiring up a voltage supply.


Generally the one that's most convenient or closest to the rest of your connections is tidier and easier, or alternatively the one closest to the supply pin that you use.

For example, it's a good idea to use Physical Pin 17 for 3v3 and Physical Pin 25 for ground when using the SPI connections, as these are right next to the important pins for SPI0.

### Details

- 1 pin header
- Uses 8 GPIO pins


# Pulse Width Modulation PWM

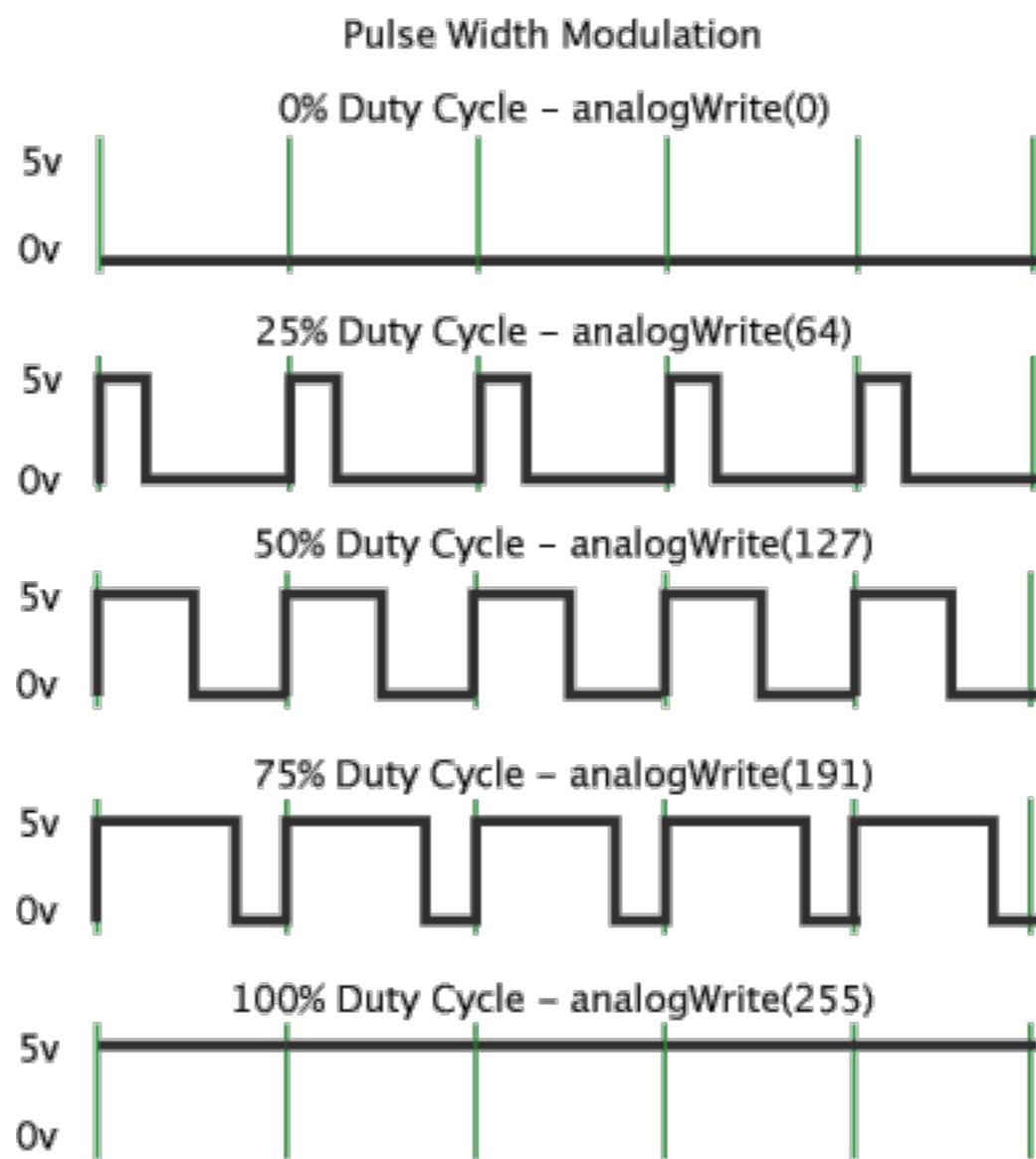

# Pulse Width Modulation
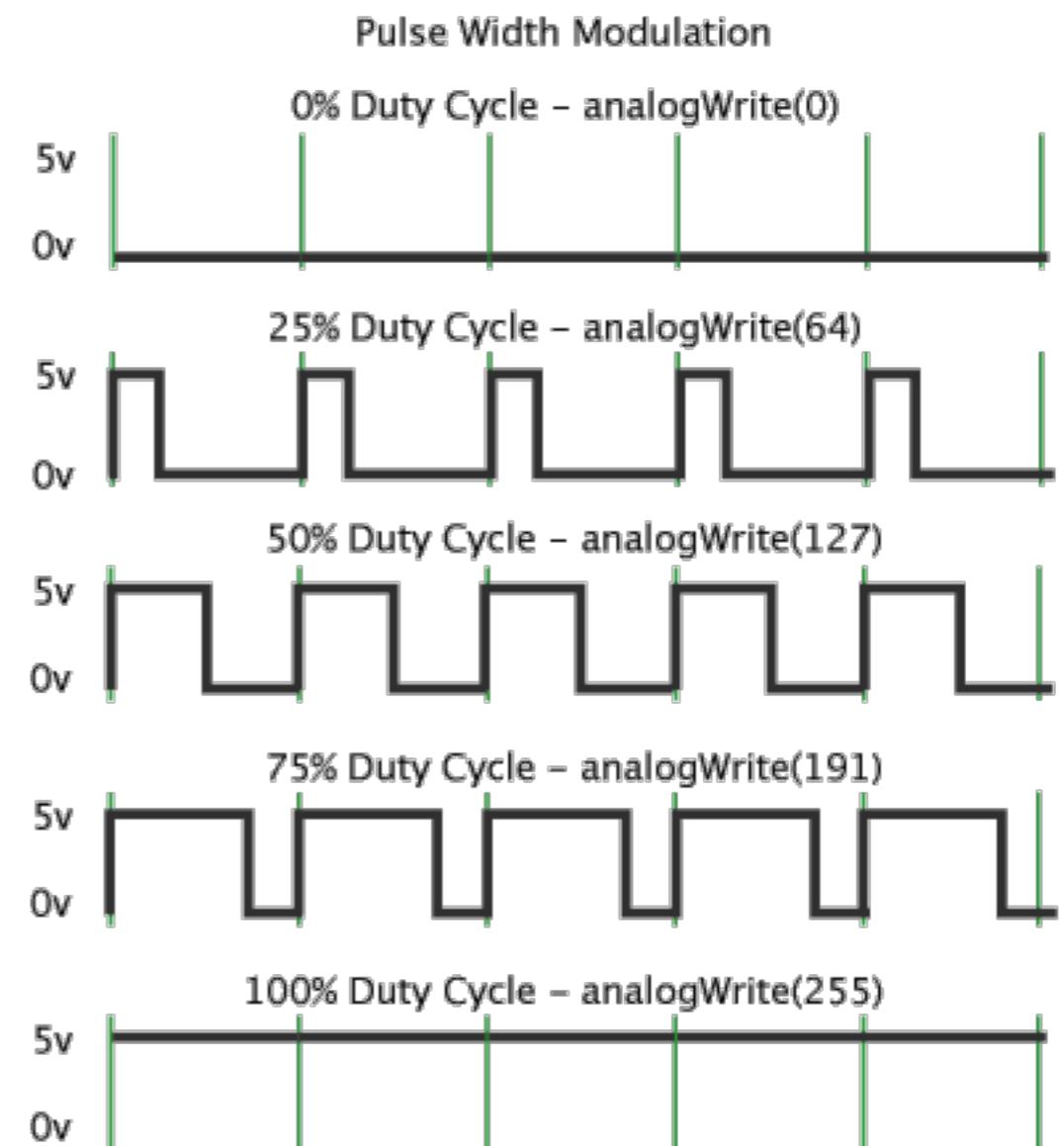
## PWM


- PWM Pins
  - Capable to generate square wave signals.
- We control the % of the duty cycle:
  - 0 - 0%
  - 255 - 100% (check hardware specs)
- Possible usage:
  - Led dimming.
  - Control a servo motor.



# Pulse Width Modulation
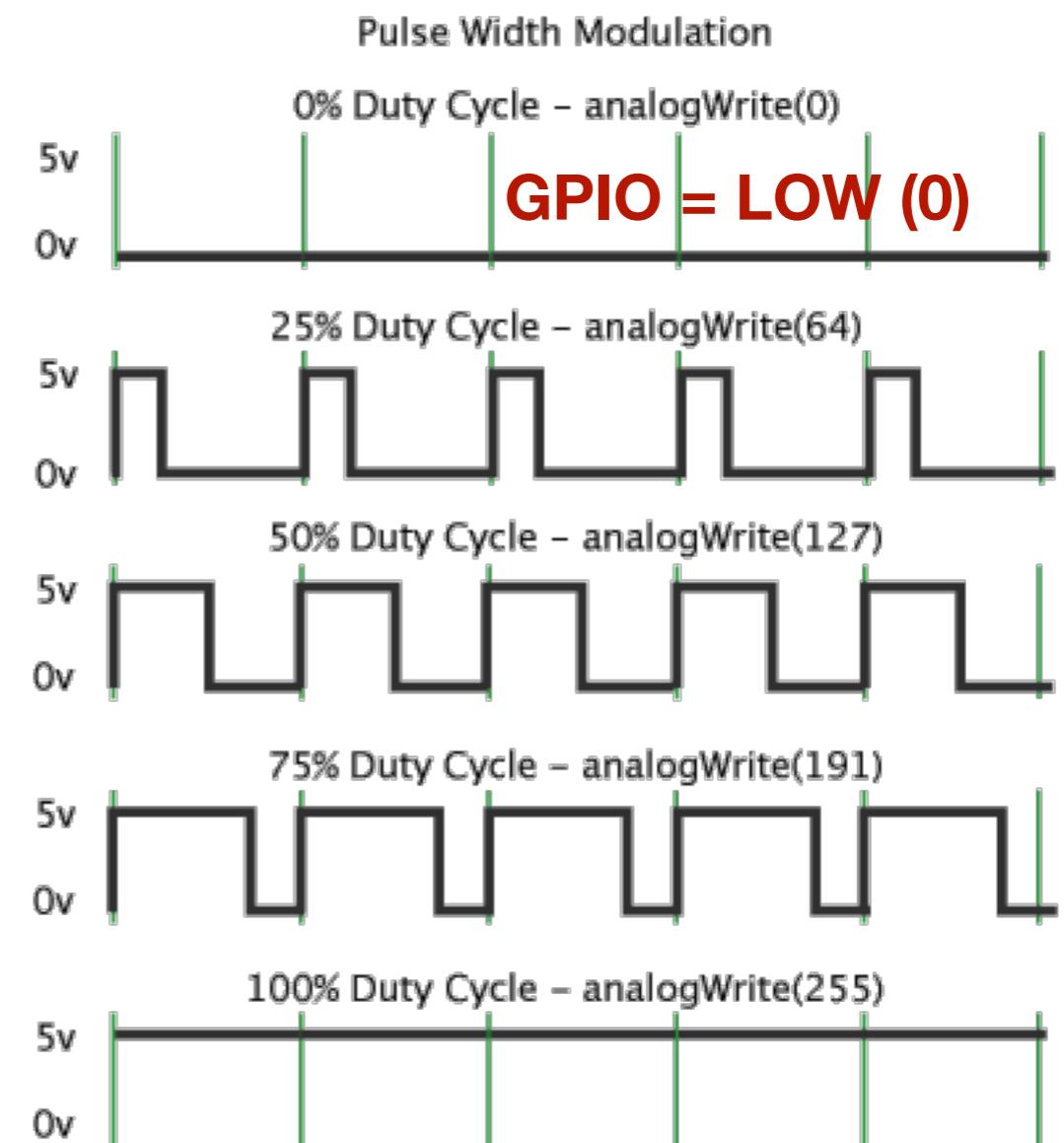
## PWM


- PWM Pins
  - Capable to generate square wave signals.
- We control the % of the duty cycle:
  - 0 - 0%
  - 255 - 100% (check hardware specs)
- Possible usage:
  - Led dimming.
  - Control a servo motor.



# Pulse Width Modulation
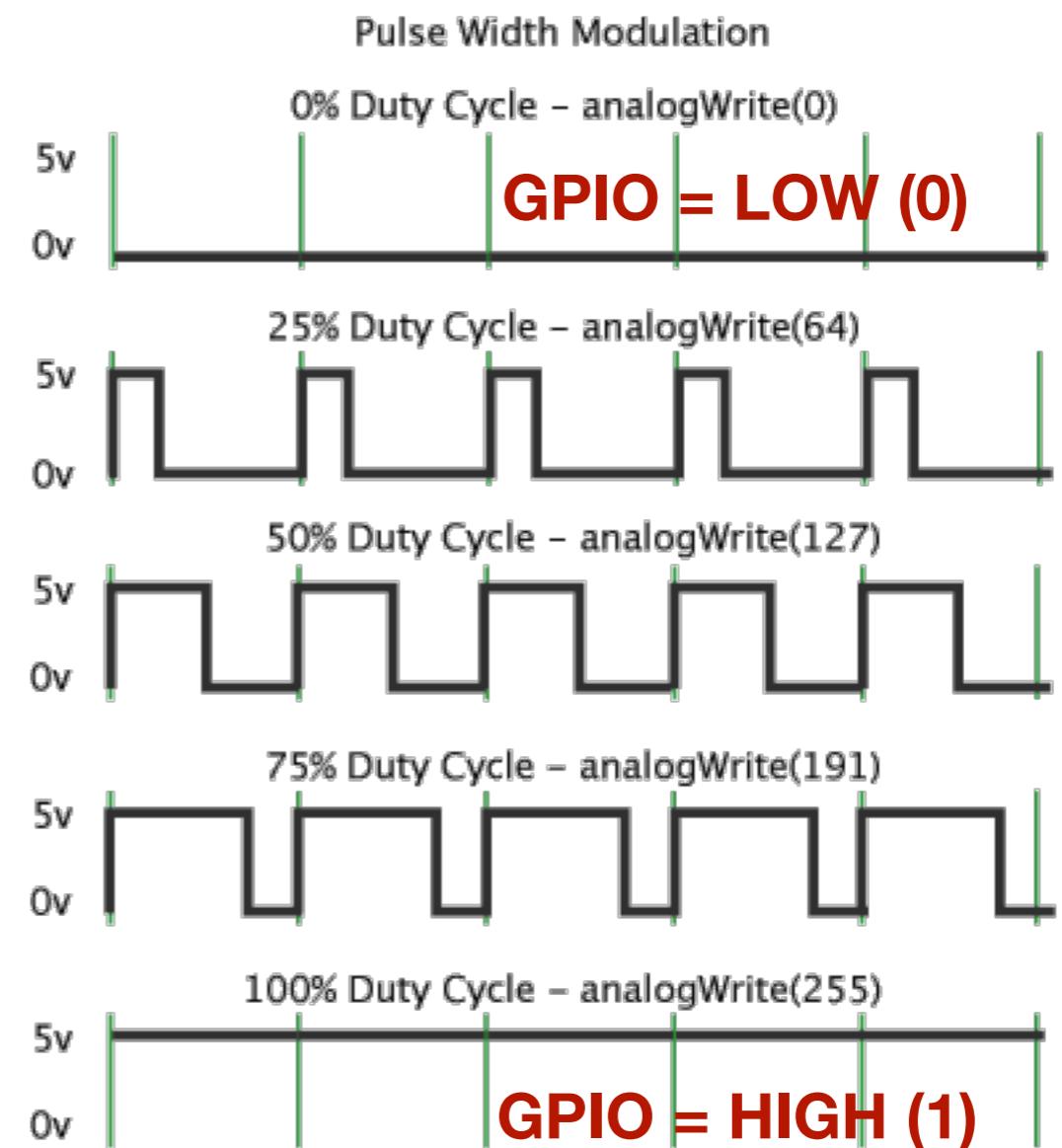
## PWM

- PWM Pins
  - Capable to generate square wave signals.
- We control the % of the duty cycle:
  - 0 - 0%
  - 255 - 100% (check hardware specs)
- Possible usage:
  - Led dimming.
  - Control a servo motor.




# Pulse Width Modulation

## PWM

- PWM Pins
  - Capable to generate square wave signals.
  - We control the % of the duty cycle:
    - 0 - 0%
    - 255 - 100% (check hardware specs)
  - Possible usage:
    - Led dimming.
    - Control a servo motor.

↔ Between 1.1Hz and 19MHz

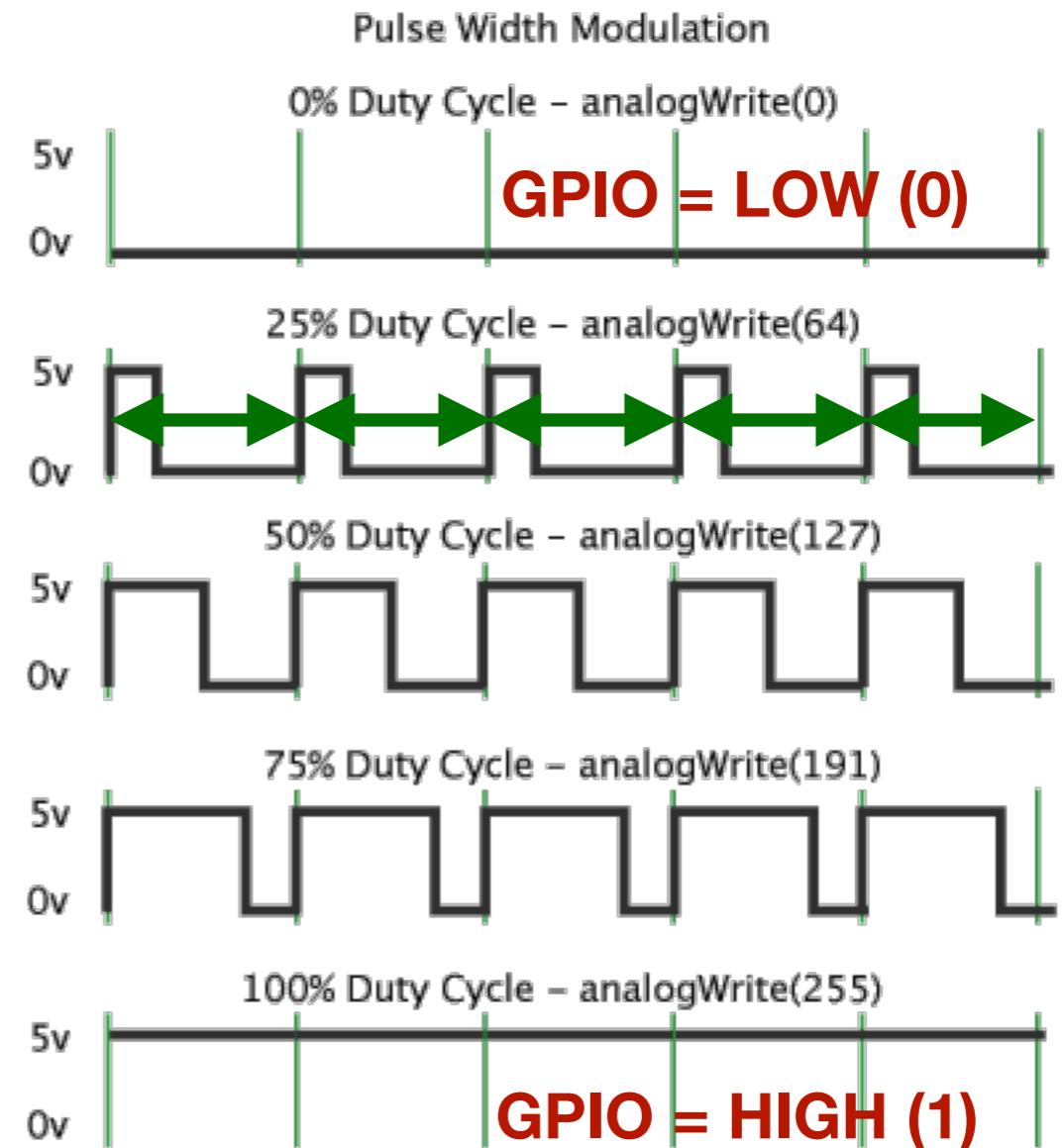

# Analog to Digital Convertors



Ground    DPI    GPCLK    JTAG    1-WIRE    PCM    SDIO    I2C    SPI    UART    WiringPi

Browse more HATs, pHATs and add-ons »

**Arcade Bonnet**  
Connect joystick, buttons and speakers to your Pi

**MotoZero**  
Control 4 motors from your Raspberry Pi

**XBee Shield**  
Use XBee modules with the Raspberry Pi

**Score:Zero**  
A super-simple and stylish soldering kit - makes an NES-style games controller when assembled.

## BCM 18 (PWM0)


Alt0	Alt1	Alt2	Alt3	Alt4	Alt5
PCM CLK	SMI SD10	DPI D14	I2CSL SDA / MOSI	SPI1 CE0	PWM0

- Physical pin 12
- BCM pin 18
- Wiring Pi pin 1

The PWM0 output of BCM 18 is particularly useful, in combination with some fast, direct memory access trickery, for driving tricky devices with very specific timings. The WS2812 LEDs on the [Unicorn HAT](#) are a good example of this in action.


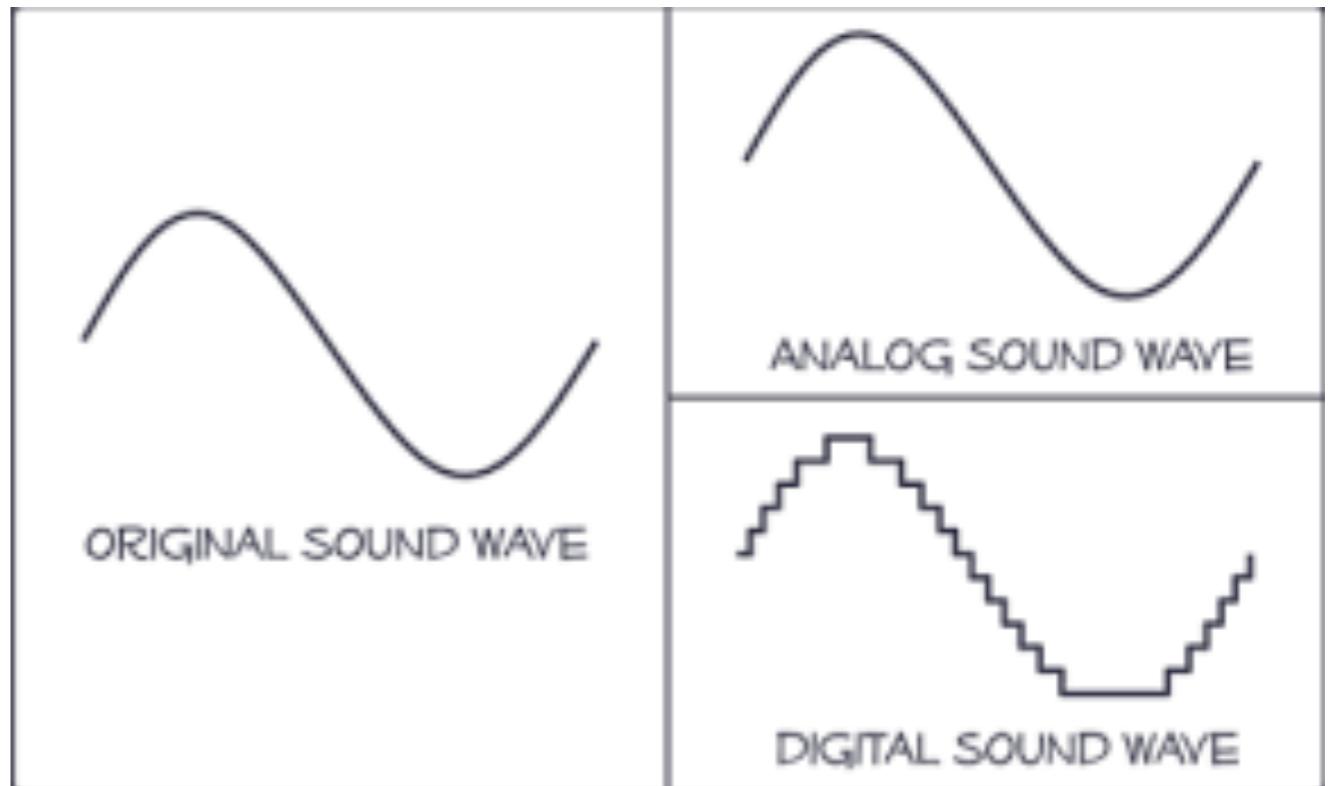
# Analog to Digital Convertors

- When reading or writing digital signals we need to establish values for:
  - Bits per sample.
    - 1 bit - GPIO Input.
    - $n$  bits -  $0..2^n - 1$
  - Sampling rate.


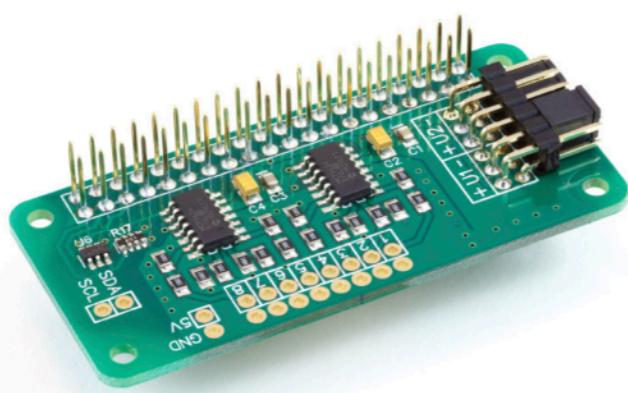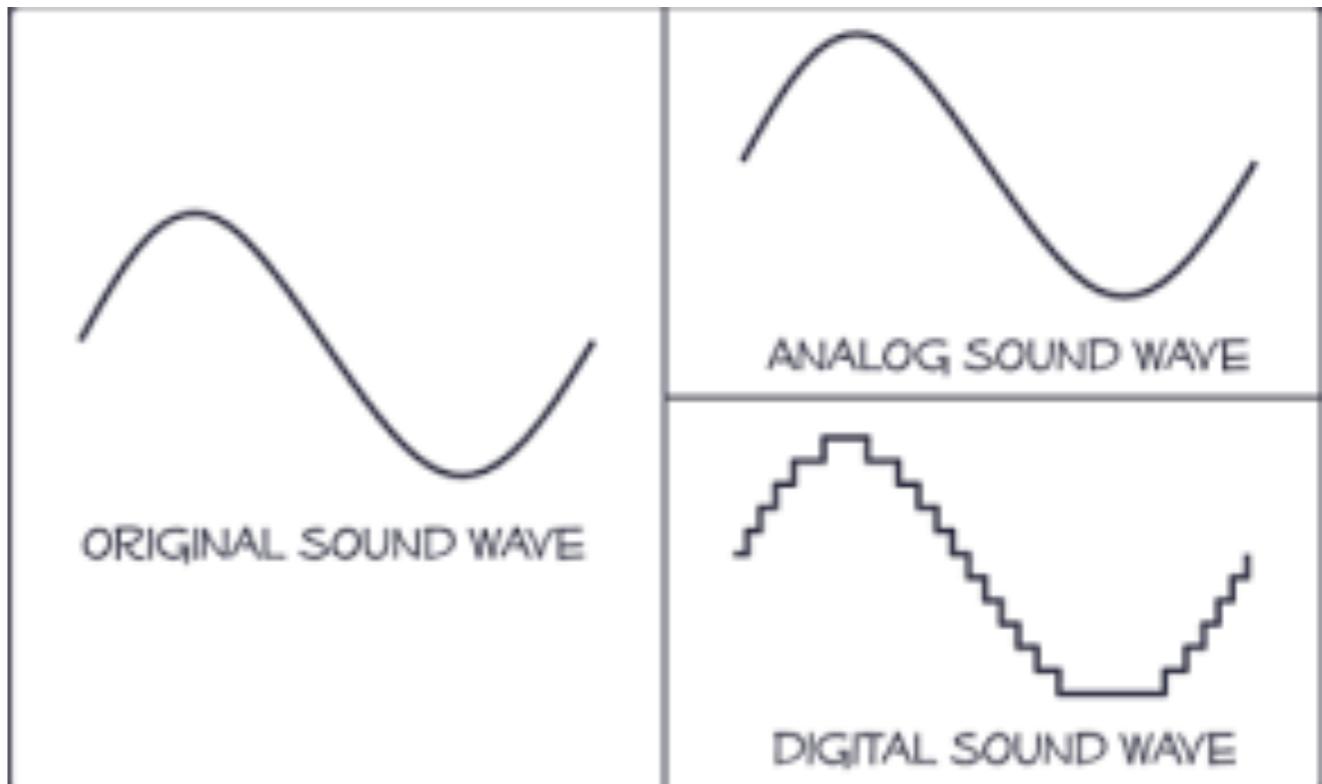
# Analog to Digital Convertors

- When reading or writing digital signals we need to establish values for:
  - Bits per sample.
    - 1 bit - GPIO Input.
    - $n$  bits -  $0..2^n - 1$
  - Sampling rate.  
ADC Pi



# Analog to Digital Convertors

## Features


- 8 x 17-bit 0 to 5V Single Ended Inputs
- Control via the Raspberry Pi I2C port
- Stack up to 4 ADC Pi boards on a single Raspberry Pi
- ...

# Analog to Digital Convertors

## Features

- 8 x 17-bit 0 to 5V Single Ended Inputs
- Control via the Raspberry Pi I2C port
- Stack up to 4 ADC Pi boards on a single Raspberry Pi
- ...

ADC Pi

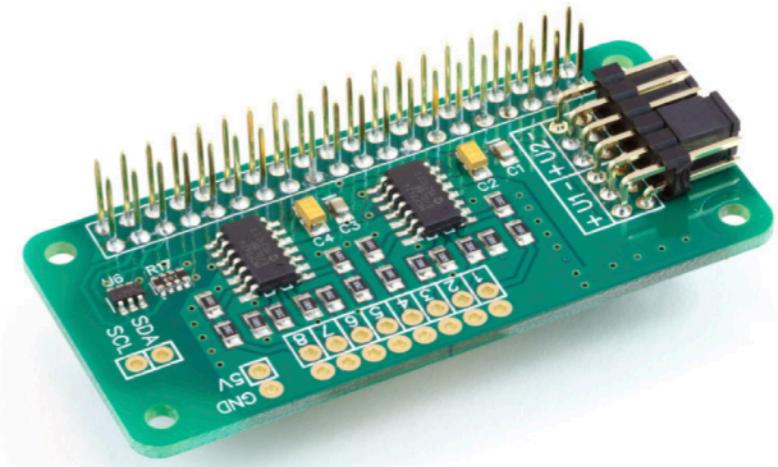


# Setup



Image source: <https://rehoff.me>

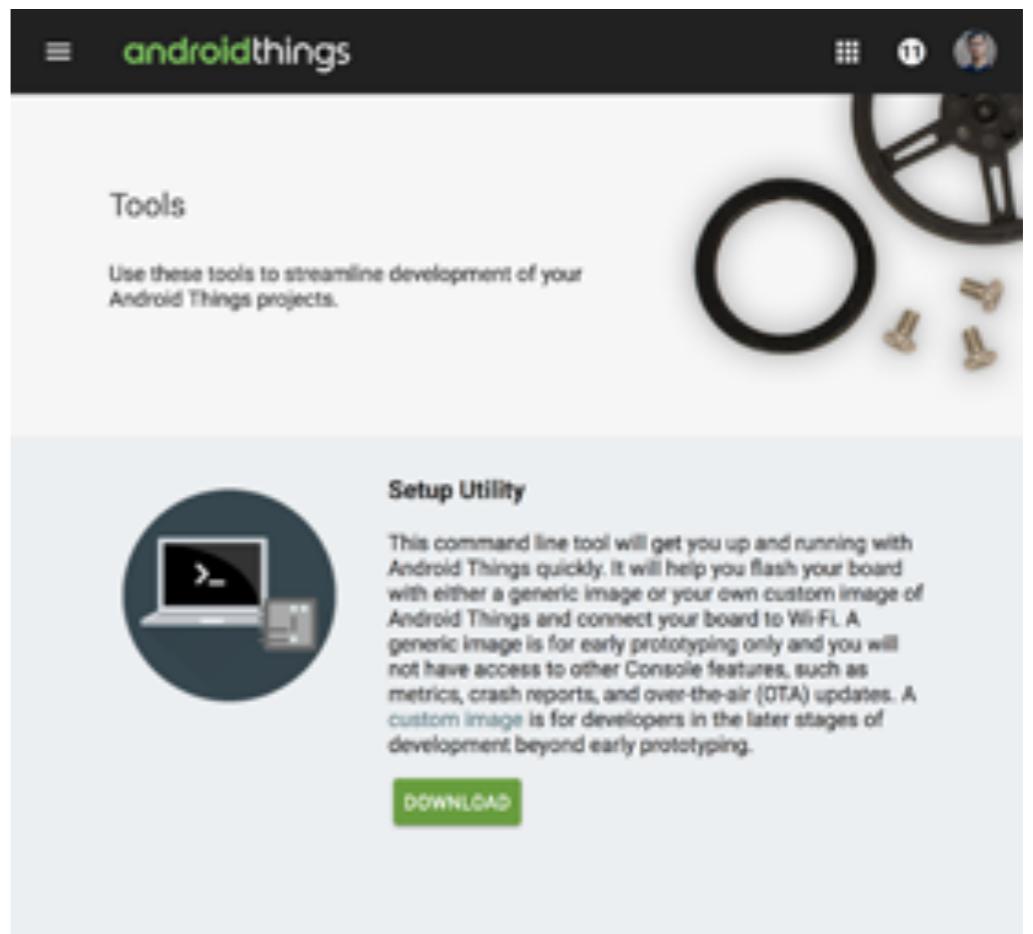
# Flashing the Image

- Prerequisite:
  - Micro-USB cable.
  - Ethernet cable.
  - MicroSD card reader.
  - 8GB or larger microSD card.
- Optional items:
  - HDMI cable.
  - HDMI-enabled display.



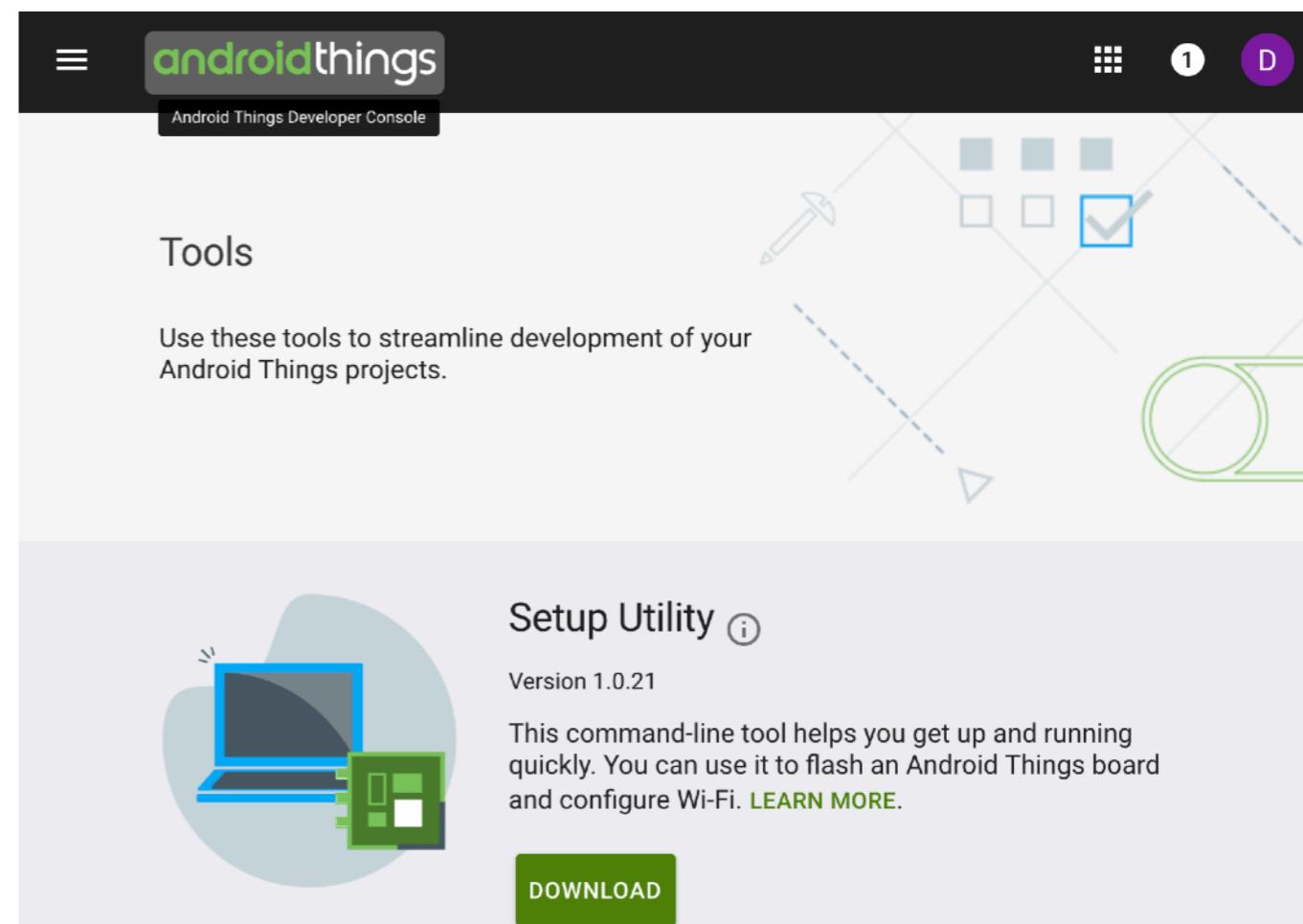
# Step 1

- Download the Android Things Setup Utility.
  - <https://partner.android.com/things/console/#/tools>
- Using the setup utility:
  - Select the option to install Android Things and optionally set up Wi-Fi.
  - Insert the microSD card into the microSD slot on the underside of the Raspberry Pi.


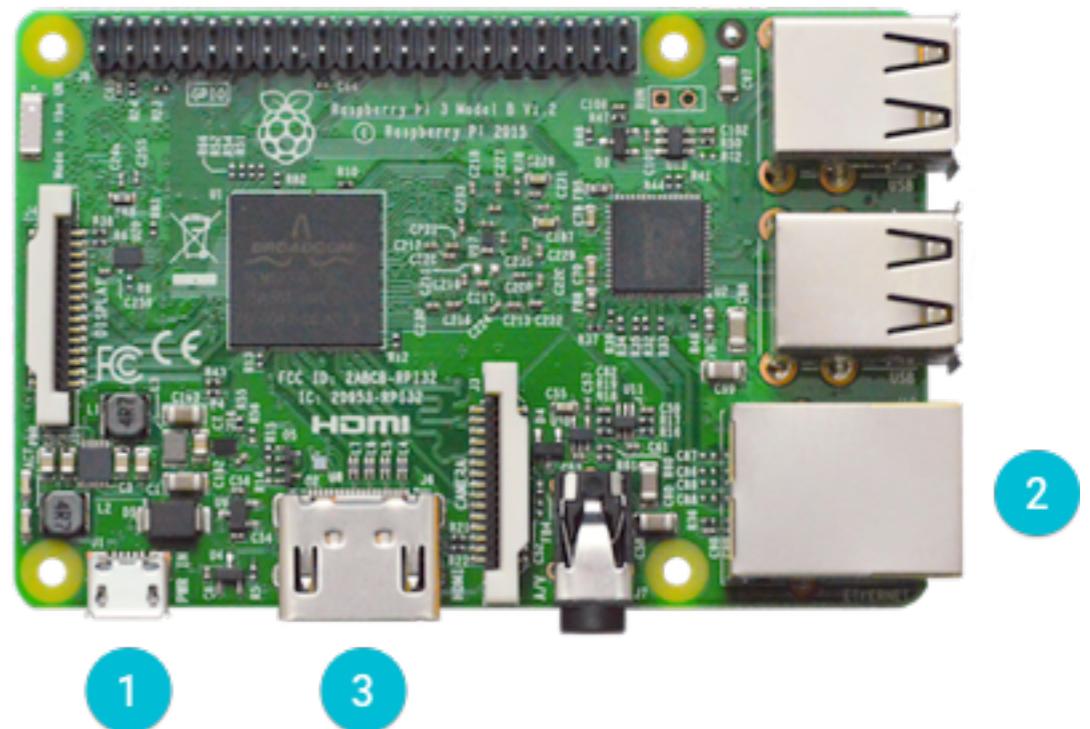
# Step 2

- Connect a USB cable to J1 for power.
- Connect an Ethernet cable to your local network.
- (Optional) Connect an HDMI cable to an external display.
- Verify that Android is running on the device.
  - Connect to the IP address using the adb tool:
    - `adb connect <ip-address>`



connected to <ip-address>:5555

# Lecture outcomes

- Understand how to establish the needed components.
- How to establish the hardware characteristics for the needed components.
- How to use the available pins for input and output.
- Setup the development platform.

